



ULTIMATE KCET


CRASH COURSE 2026

PHYSICS

Lecture : 01

ALTERNATING CURRENT AND ELECTROMAGNETIC WAVES

By – AK SIR

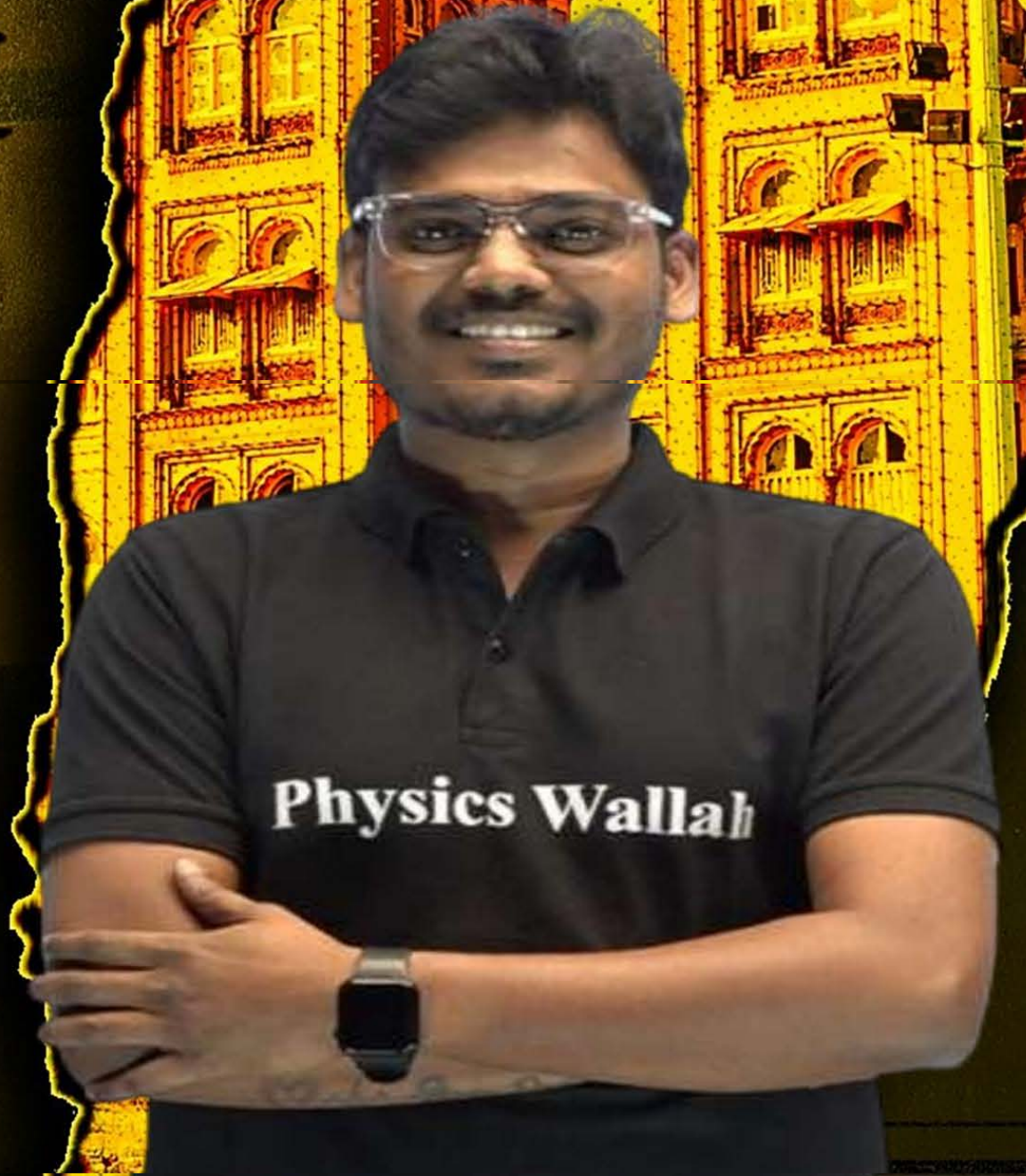

Recap *of previous lecture*

- 1** TORQUE ON A CURRENT CARRYING COIL IN A MAGNETIC FIELD
- 2** CONVERSION OF A GALVANOMETER INTO AMMETER AND VOLTMETER
- 3** BAR MAGNET AND MAGNETIC FIELD LINES
- 4** QUESTIONS



Topics *to be covered*

- 1 RMS VALUES OF AC & AC AND DC
- 2 DIFFERENT TYPES OF AC CIRCUIT
- 3 LCR-RESONANT CIRCUIT
- 4 ELECTROMAGNETIC WAVES





KCET analysis of chapter – Marks weightage

Year	Topic
2025 (2Q)	RMS Value of voltage and frequency, Series LCR
2024(3Q)	LCR circuit, Resonance frequency and LCR Graph
2023(3Q)	Quality factor, Transformer and Phase difference in LCR
2022(3Q)	Impedence of LCR, Energy stored in LC and R.M.S current
2021(3Q)	Current in LCR, Oscillating LC (2)



KCET analysis of chapter – Marks weightage

Year	Topic
2020(3Q)	R.M.S values of LCR, Power factor R-L and Resonant frequency of L-C
2019(2Q)	Peak Values of R.M.S and Power dissipated in L-R
2018(5Q)	Graph of inductive reactance, Current through AC, Power dissipated LCR, Transformer and R.M.S Values of AC
2017(3Q)	Time lag-LCR, Inductance and Transformer
2016(4Q)	Average value of AC, Current AC, Source voltage-LCR and Power dissipated in AC
2015(3Q)	Efficiency of transformer, Resonance-LCR and Power dissipated in a pure inductor



RMS VALUES

Root mean square values

From last class: AC Generator.

RMS Values

In India

↳ 220V
↳ $f = 50\text{Hz}$ } AC

$$e = e_0 \sin \omega t$$

$$v = v_0 \sin \omega t$$

$$I = \frac{v}{R} = \frac{v_0 \sin \omega t}{R}$$

$$I = I_0 \sin \omega t$$

$$v_0 = NAB\omega$$

$$I_0 = \frac{NAB\omega}{R}$$

*
$$V_{\text{rms}} = \frac{v_0}{\sqrt{2}}$$


*
$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

v_0, I_0 - peak value of voltage & current



AC and DC

Alternating Current (AC)

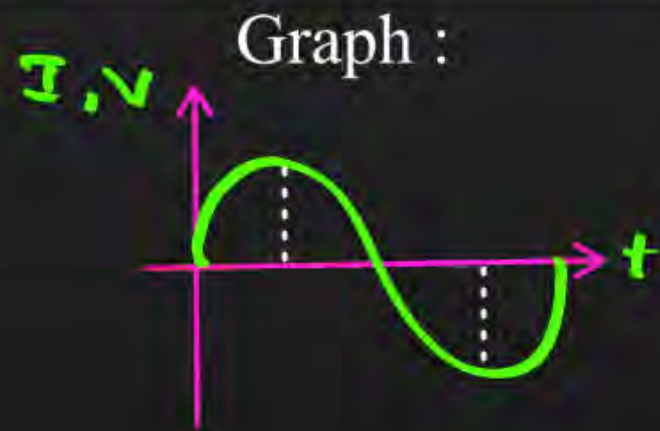


Can be Generated by using AC Generator.

Inverter converts DC into AC.

Can be controlled using Transformer.

Direct current

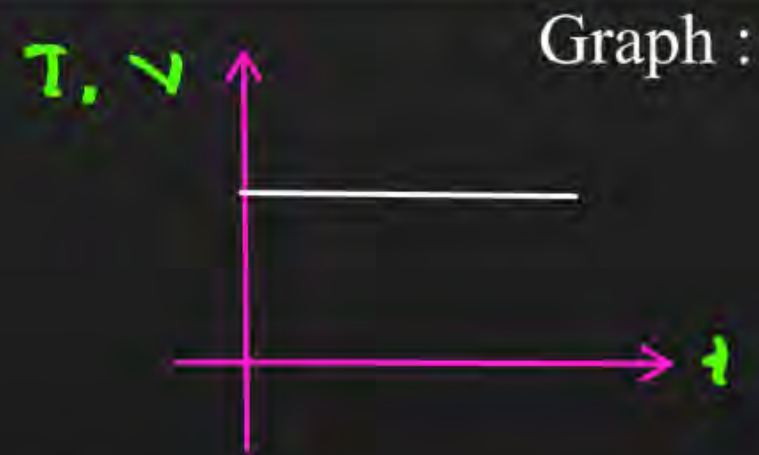

Can be Generated by using DC Generator, Battery, solar panels.

Rectifier converts AC into DC.

Cannot be controlled using Transformer

Question



In Karnataka, the normal domestic power supply AC is 220 V, 50 Hz. Here, 220 V and 50 Hz refer to

- A** peak value of voltage and frequency
- B** rms value of voltage and frequency
- C** mean value of voltage and frequency
- D** peak value of voltage and angular frequency

Question



A multimeter reads a voltage of a certain AC source as 100 V . What is the peak value of voltage of AC source?

A 200 V

B 100 V

C 141.4 V

D 400 V

$$V_{\text{rms}} = 100 \text{ V}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$


$$V_0 = \sqrt{2} \times V_{\text{rms}} = 1.41 \times 100$$

$$V_0 = 141 \text{ V}$$

$$y = A \sin(\omega t \pm \phi)$$



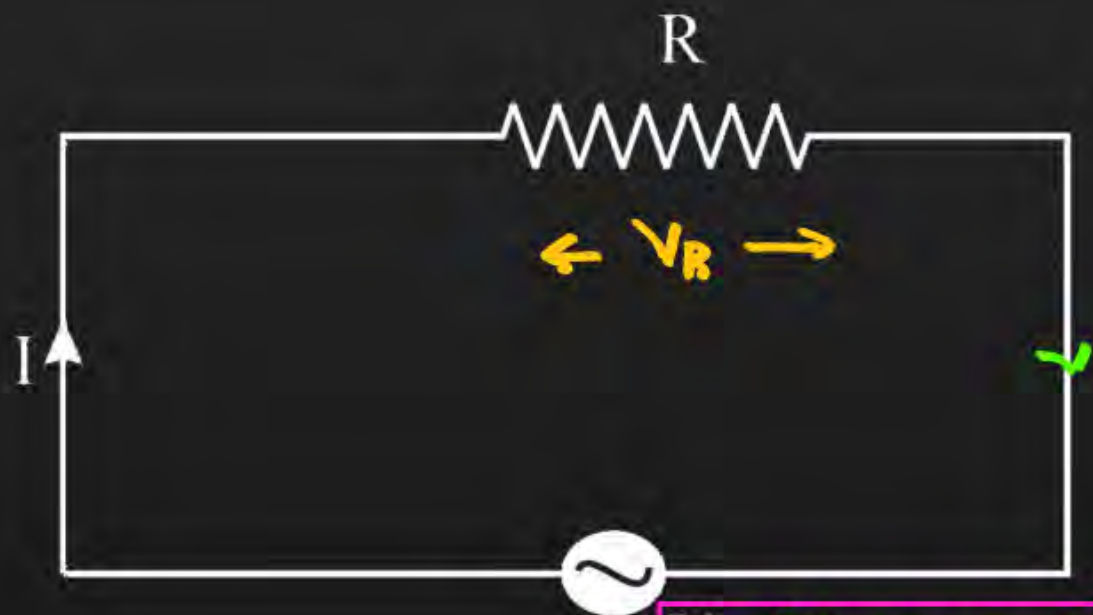AC Voltage applied to pure Resistance (R)




$$V = V_0 \sin \omega t$$

$$I = \frac{V}{R}$$

$$I = \frac{V_0 \sin \omega t}{R}$$

$$I = I_0 \sin \omega t$$

V & I both are in phase i.e. $\phi = 0$

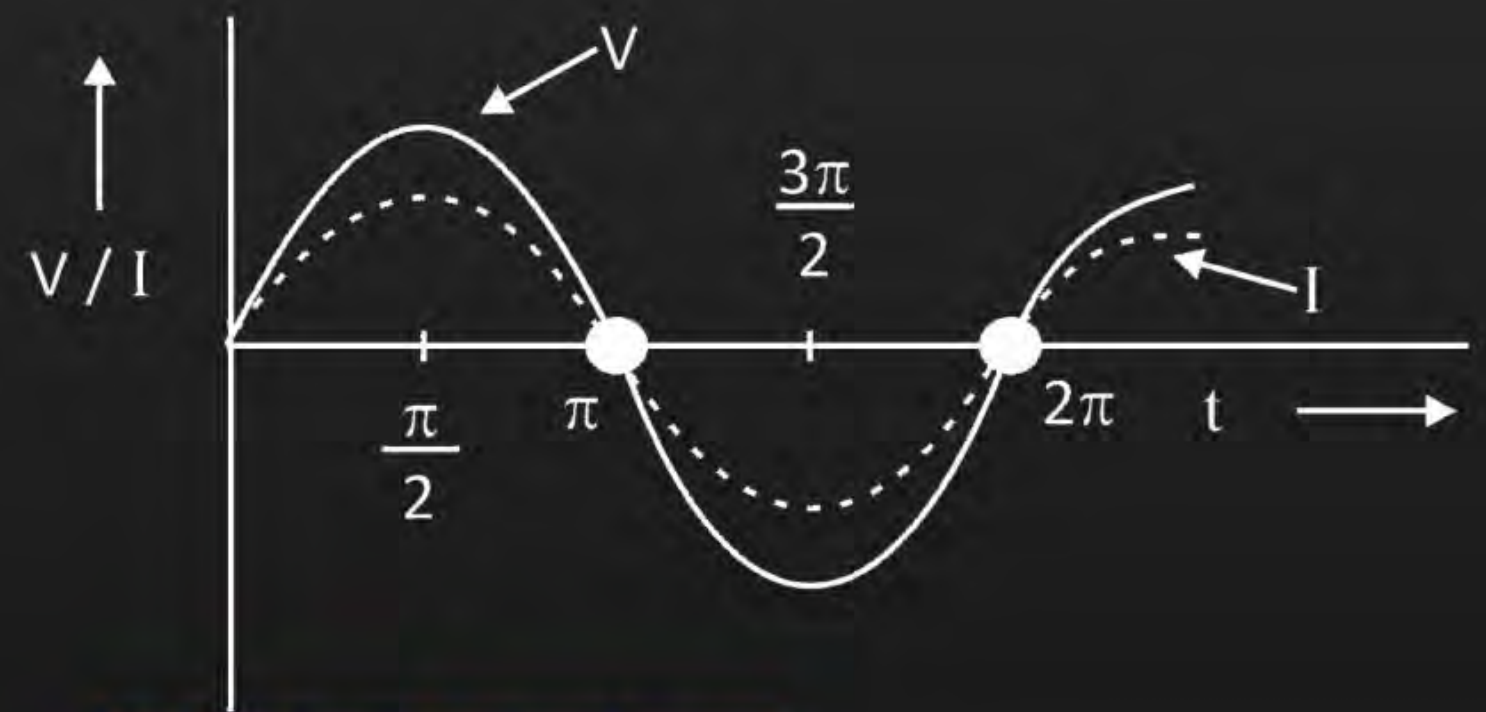


Phasor Diagram






AC Voltage applied to pure Inductor (L)

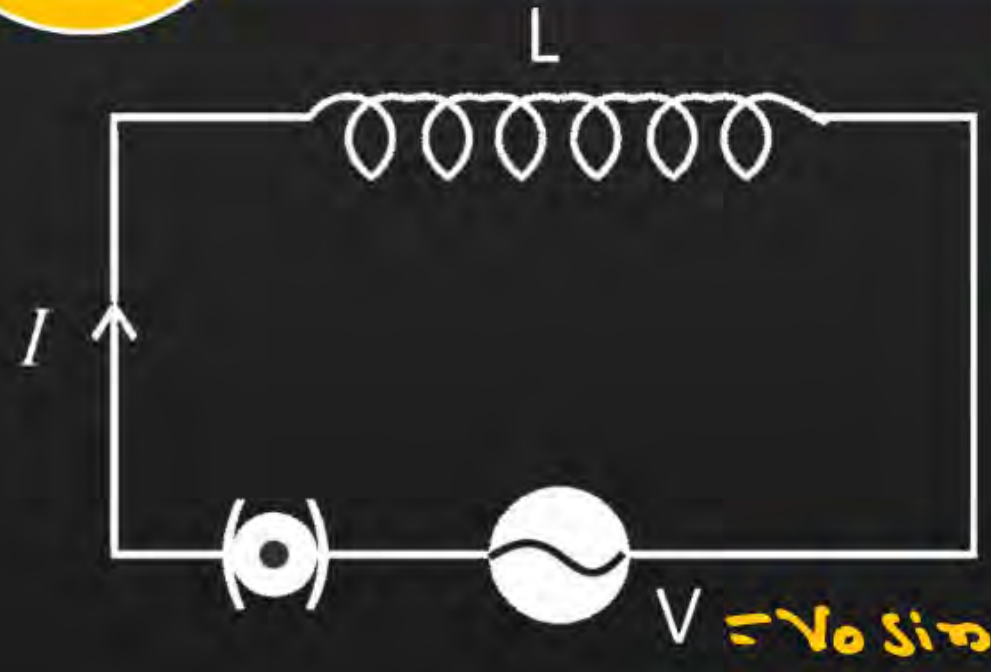


$$I_0 = \frac{V_0}{X_L}$$

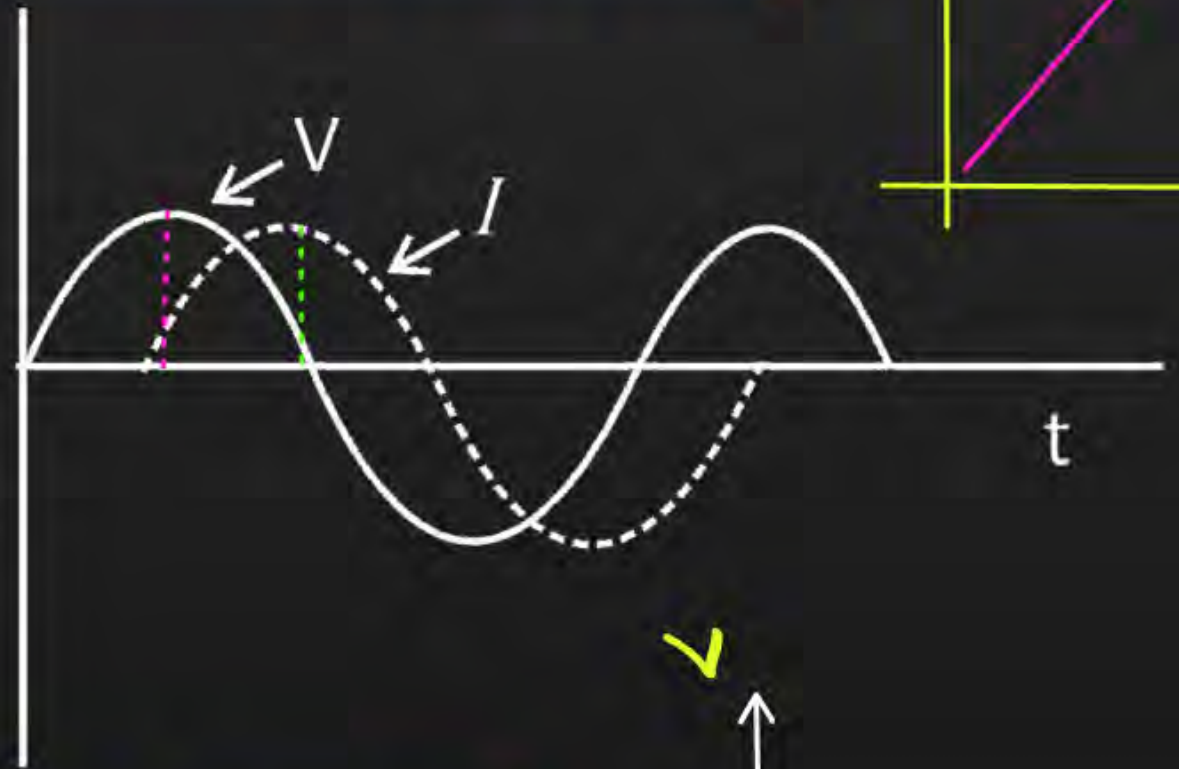V/I
 $X_L \rightarrow$ Inductive Reactance



Phases Diagram

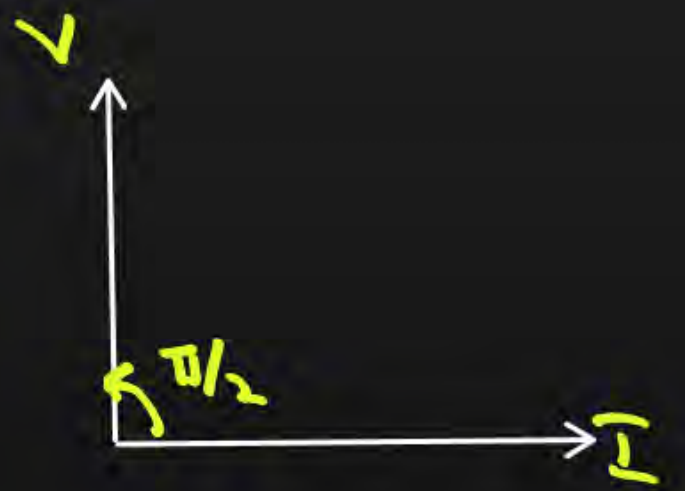

$$I = I_0 \sin(\omega t - \frac{\pi}{2})$$

phase Difference

$\phi = \pi/2$
 $\rightarrow V$ Leads I by $\frac{\pi}{2}$
 $\rightarrow I$ lags V by $\frac{\pi}{2}$.


$$X_L = \omega L = 2\pi fL$$

unit - Ohm.

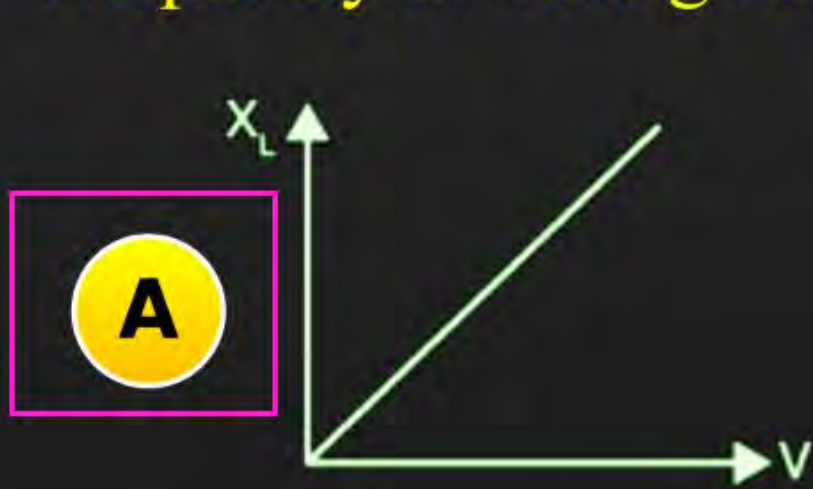Question



Which of the following, represents the variation of inductive reactance (X_L) with the frequency of voltage sources (ν)?



$$\nu = ?$$

ν
 \sim





$$X_L = \omega L$$

$$X_L = 2\pi f L$$

$$X_L \propto f$$

$$X_L \propto \omega$$

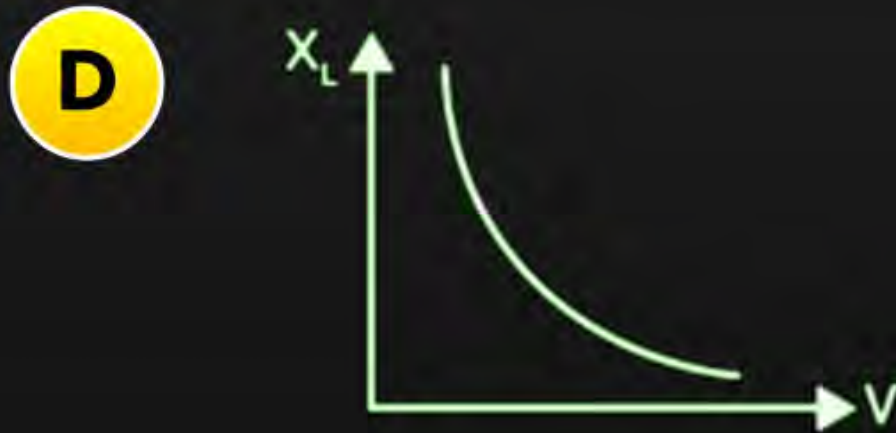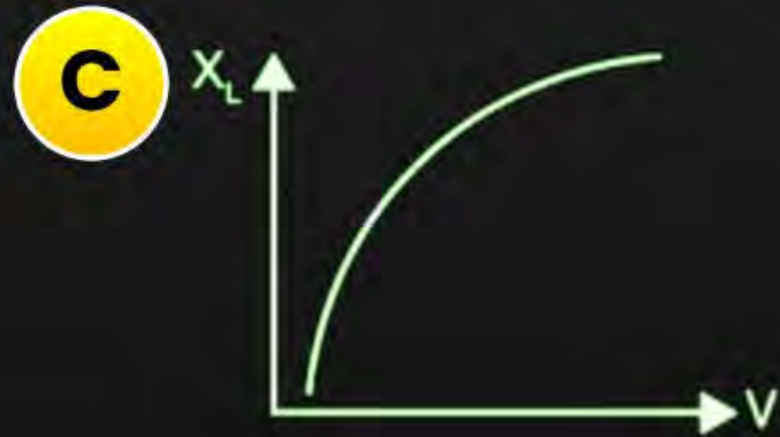

Question

 X_L I_0

What is the inductive reactance of a coil if the current through it is 20 mA and voltage across it is 100 V

 V_0

$$I_0 = \frac{V_0}{X_L} \Rightarrow X_L = \frac{V_0}{I_0}$$

$$X_L = \frac{100}{20 \times 10^{-3}} = 5 \times 10^3$$

$$X_L = 5000 \Omega$$

$$X_L = \frac{V_{rms}}{I_{rms}}$$

Question



$$X_L = \frac{V_{rms}}{I_{rms}} = \frac{V_0}{\sqrt{2}} \times \frac{1}{I_{rms}} = \frac{50\sqrt{2}}{\sqrt{2}} \times \frac{1}{2} = 25\Omega$$

In given circuit applied voltage $V = 50\sqrt{2}\sin(100\pi t)$ volt and ammeter reading is 2A then calculate value of L?

$$v = V_0 \sin \omega t$$

↳ I_{rms}

$$V_0 = 50\sqrt{2} \text{ V} \quad \omega = 100\pi \text{ rad/s}$$

$$I = \frac{V}{R} = \frac{V}{X_L} \Rightarrow X_L = \frac{V}{I} = \frac{V_0}{I_0}$$

$$I_{rms} = \frac{I_0}{\sqrt{2}} \quad I_0 = \sqrt{2} I_{rms} = \sqrt{2} \times 2 \text{ A}$$

$$X_L = \frac{50\sqrt{2}}{2\sqrt{2}} = 25\Omega$$

$$X_L = \omega L = 2\pi f L$$

$$25 = \frac{100\pi}{4} \times L$$


$$L = \frac{1}{4\pi} = \frac{1}{4 \times 3.14} = 0.080 \text{ H} = 80 \text{ mH}$$





AC Voltage applied to pure Capacitor (C)
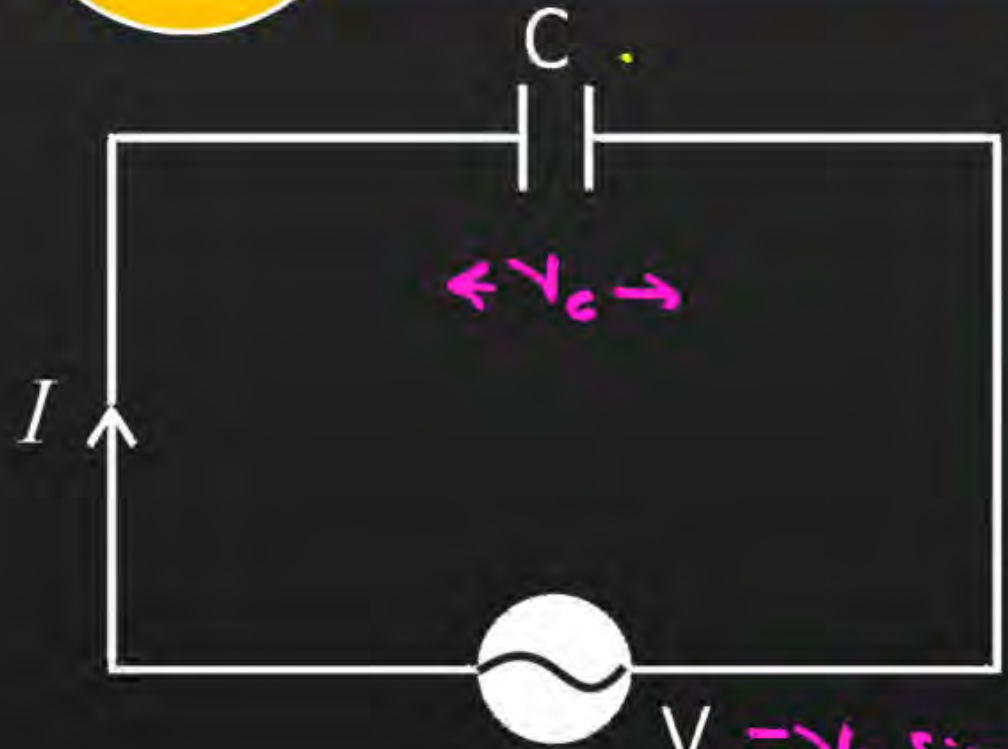
$$X_c \propto \frac{1}{f} \propto \frac{1}{\omega}$$




$$I_0 = \frac{V_0}{X_c}$$

$$X_c = \frac{V_0}{I_0}$$

OR

$$X_c = \frac{V_{rms}}{I_{rms}}$$

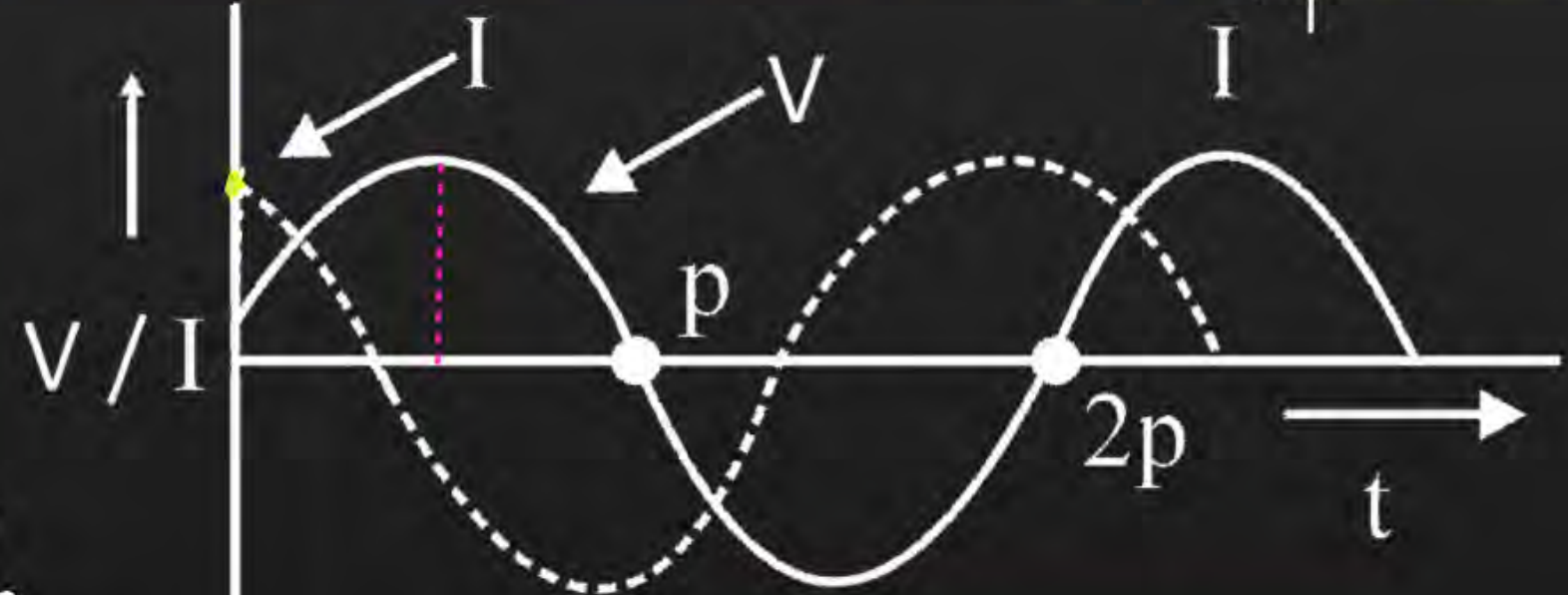

Phase Diagram

$V = V_0 \sin \omega t$
 X_c - Capacitive reactance

$$I = I_0 \sin(\omega t + \frac{\pi}{2})$$


$\rightarrow V$ lags I by $\frac{\pi}{2}$

$\rightarrow I$ leads V by $\frac{\pi}{2}$

$$X_c = \frac{1}{\omega C}$$

$$X_c = \frac{1}{2\pi f C}$$

\Rightarrow Unit Ohm (Ω)

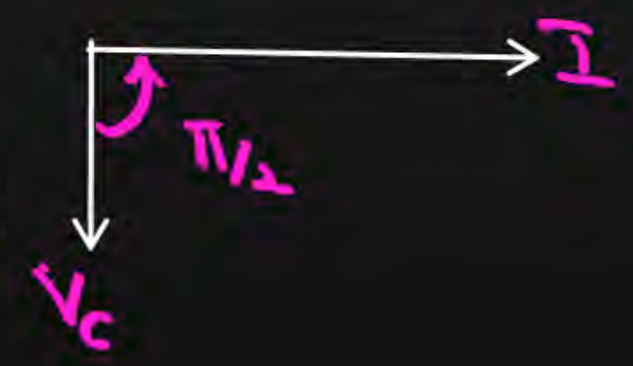

Question



$$p = 10^{-12} \text{ F}$$

A capacitor of 50 pF is connected to an a.c. source of frequency 1kHz. Calculate its reactance.

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_c = \frac{1}{2 \times 3.14 \times 10^3 \times 50 \times 10^{-12}}$$

$$X_c = \frac{1}{314 \times 10^7} = 0.00318 \times 10^9$$

$$X_c = 3.18 \times 10^6 \Omega$$

Question



A capacitor of capacitance $10\mu\text{F}$ is connected to an AC ammeter. If the source voltage varies as $V = 50\sqrt{2}\sin 100t$, the **reading of the ammeter** is

$$I = \frac{V}{R} = \frac{V}{X_c} = \frac{V_{\text{rms}}}{X_c}$$

$$v = V_0 \sin \omega t$$

$$V_0 = 50\sqrt{2} \text{ V}$$

$$\omega = 100 \text{ rad/s}$$

$$C = 10\mu\text{F}$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{50\sqrt{2}}{\sqrt{2}} = 50 \text{ V}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_c} = \frac{50}{10^3} = 50 \times 10^{-3} \text{ A}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_c}$$

$$I_{\text{rms}} = 50 \text{ mA}$$

$$X_c = \frac{1}{\omega C} = \frac{1}{100 \times 10 \times 10^{-6}} = \frac{1}{10^3} \quad \square$$

$$X_c = 10^3 \Omega$$

A 50 mA

B 70.7 mA

C 5.0 mA



D 7.07 mA




Series LCR Circuit

L-C-R series circuit

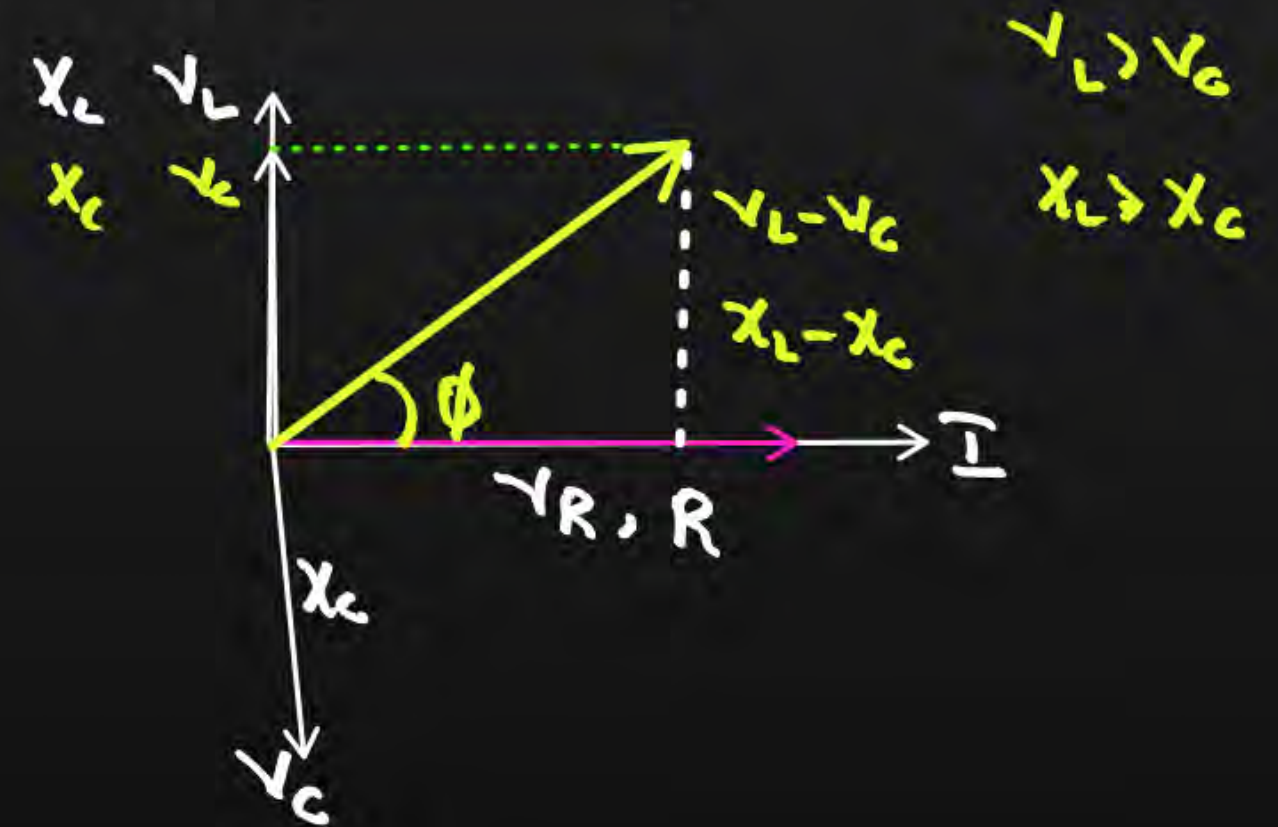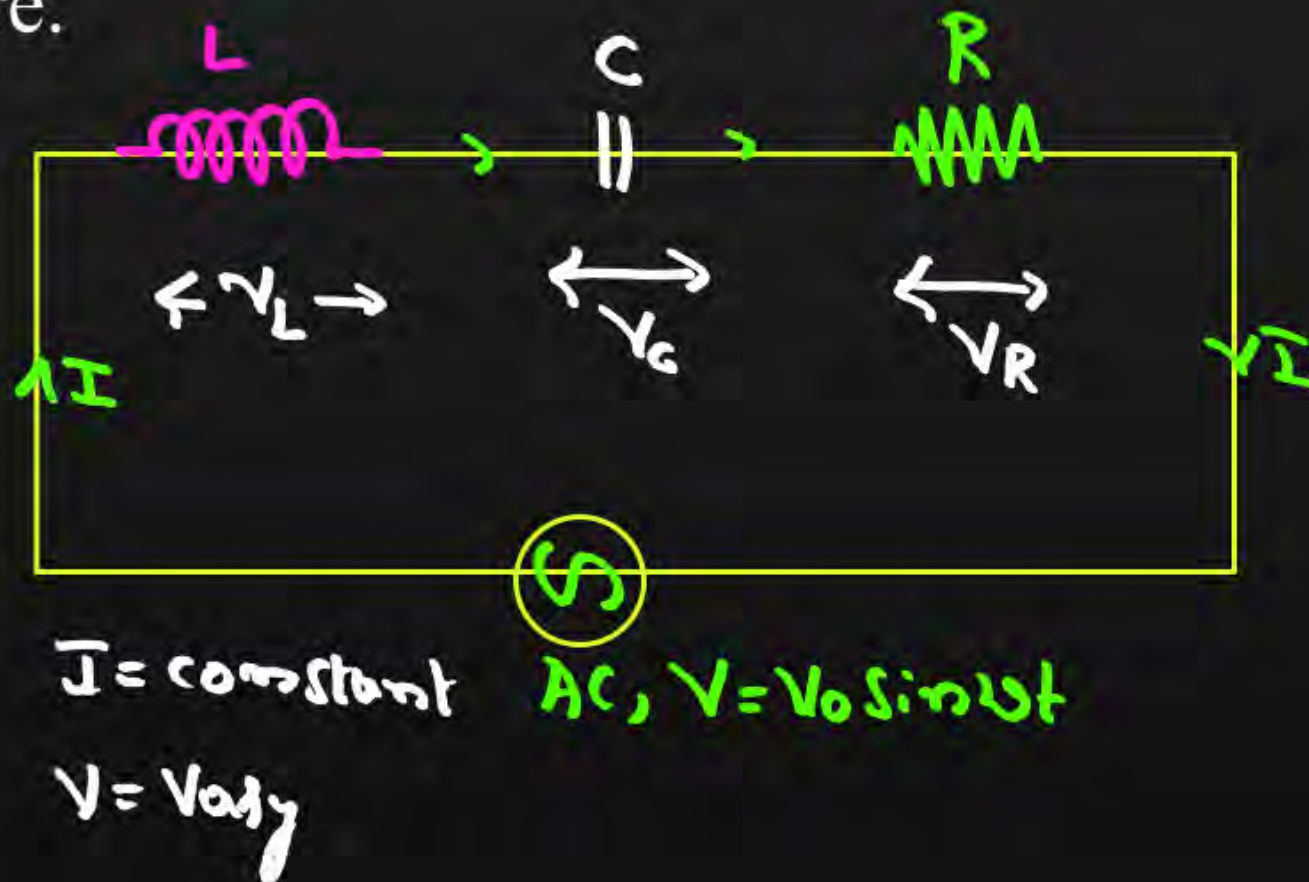
A circuit containing a series combination of an resistance R , a coil of inductance L and a capacitor of capacitance C , connected with a source of alternating e.m.f. of peak value V_0 , as shown in figure.



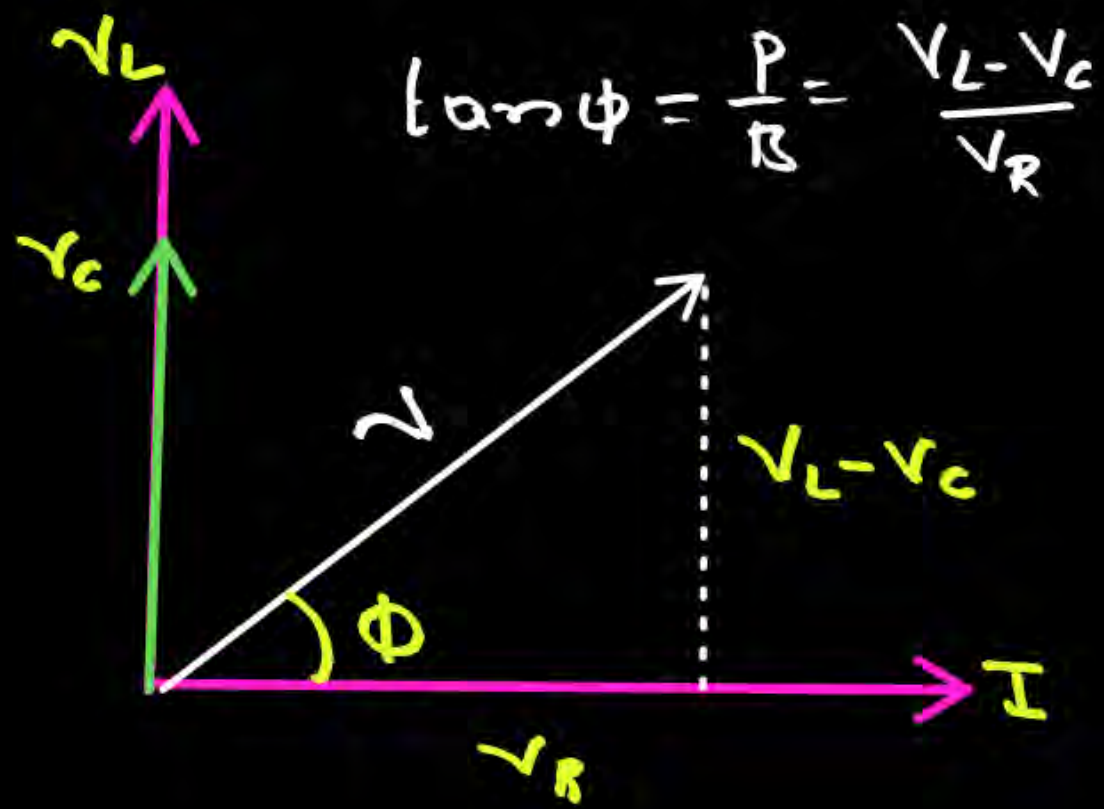

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

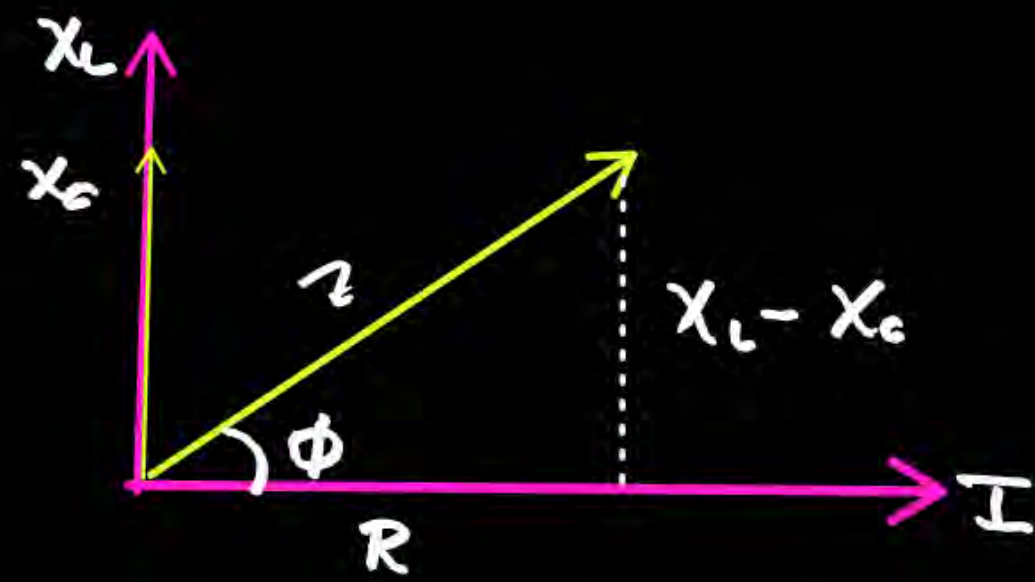

Impedance = Total Resistance

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

POWER Factor

$$\cos \phi = \frac{R}{Z} = \frac{R}{Z}$$

$$\tan \phi = \frac{P}{R} = \frac{X_L - X_C}{R}$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$

$V_L > V_C$
 $X_L > X_C$

Question




For the given LCR-series circuit. Find out applied source voltage of ac.

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = \sqrt{(40)^2 + (50 - 20)^2}$$

$$V = \sqrt{1600 + 900}$$

$$V = \sqrt{2500} = 50V$$

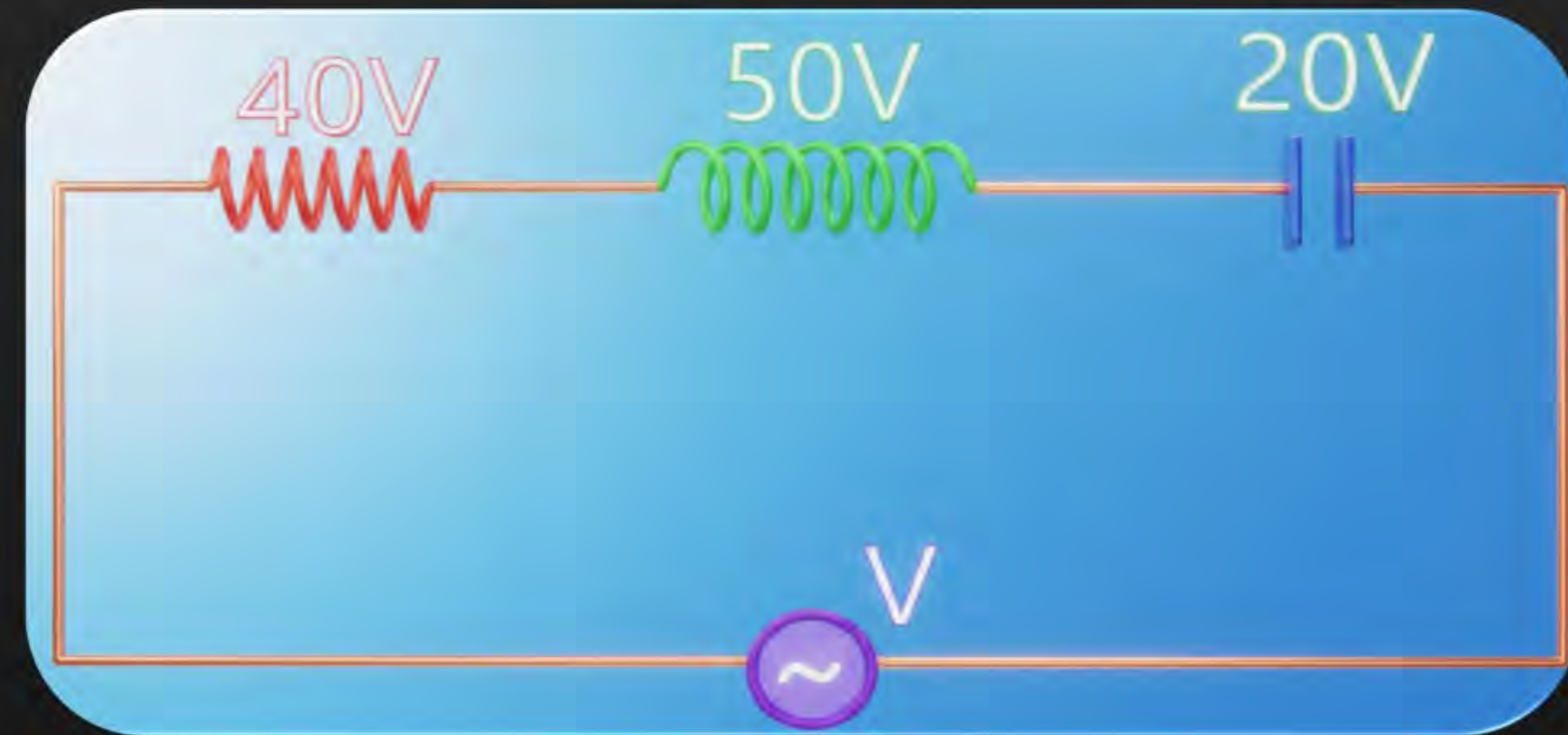

Question



A capacitor, a resistor and an inductor are connected in series to an ac-source of 110 V and frequency 60Hz. Find reading of voltmeter V3 and ammeter in the given LCR-series circuit.


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$110 = \sqrt{V_3^2 + (300 - 300)^2}$$

$$110 = \sqrt{V_3^2} \Rightarrow V_3 = 110V$$

$I = \text{constant}$, I across R
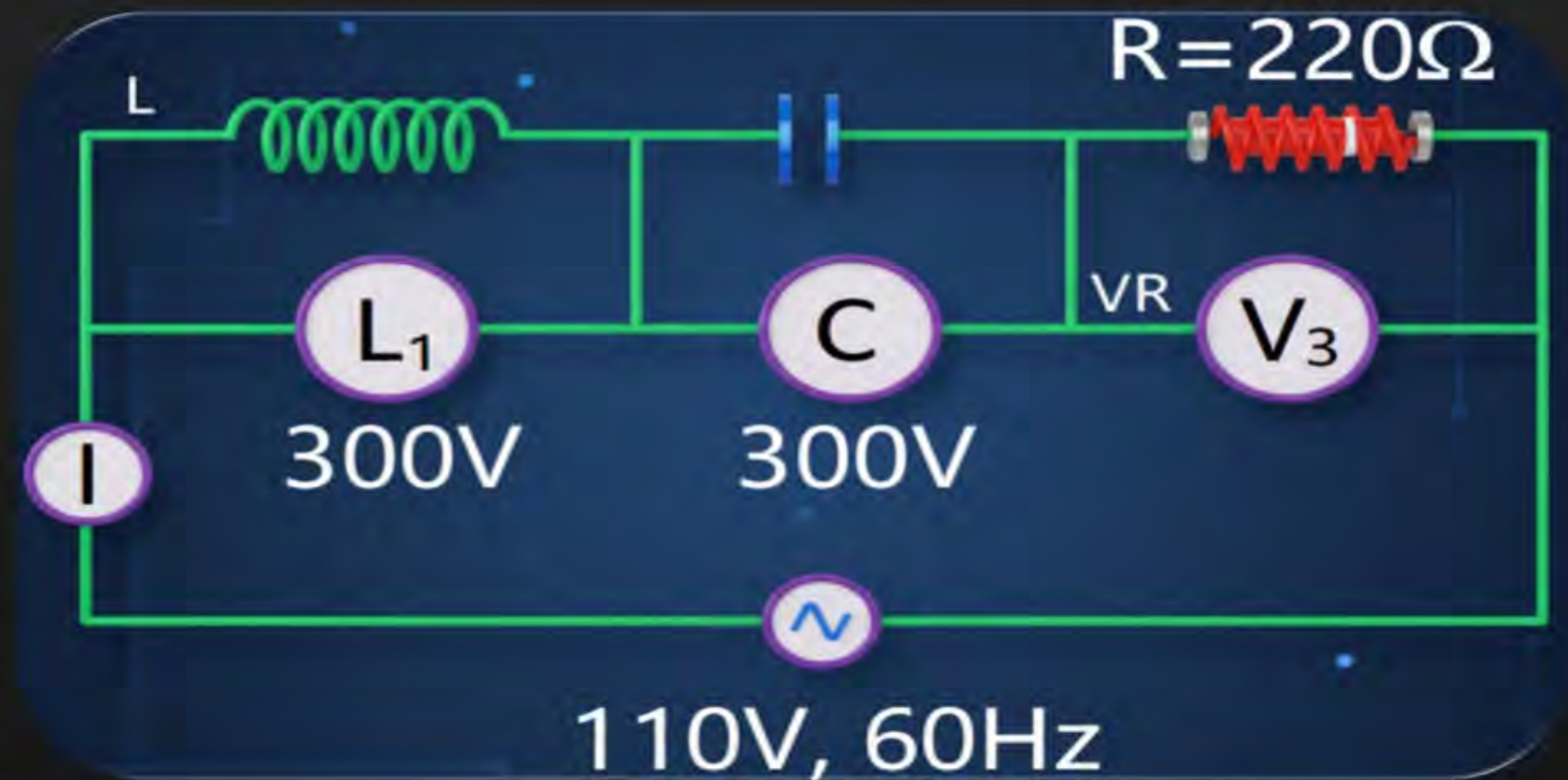
$$I = \frac{V}{R} = \frac{V_3}{R} = \frac{110}{220} = 0.5A$$



Question



Find out the impedance of given circuit.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(4)^2 + (9 - 6)^2}$$

$$Z = \sqrt{16 + 9} = \sqrt{25}$$

$$Z = 5 \Omega$$



Question



Find out reading of A.C. ammeter and also calculate the potential difference across, resistance and capacitor

$$I_{R_{rms}} = \frac{V_{rms}}{Z}$$

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{100}{\sqrt{2}} \text{ V}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(10)^2 + (20 - 10)^2}$$

$$Z = \sqrt{100 + 100}$$


$$Z = 10\sqrt{2} \Omega$$

$$I_{rms} = \frac{100}{\sqrt{2} \times 10\sqrt{2}}$$

$$I_{rms} = \frac{10}{2} = 5 \text{ A}$$

$$v = V_0 \sin \omega t$$
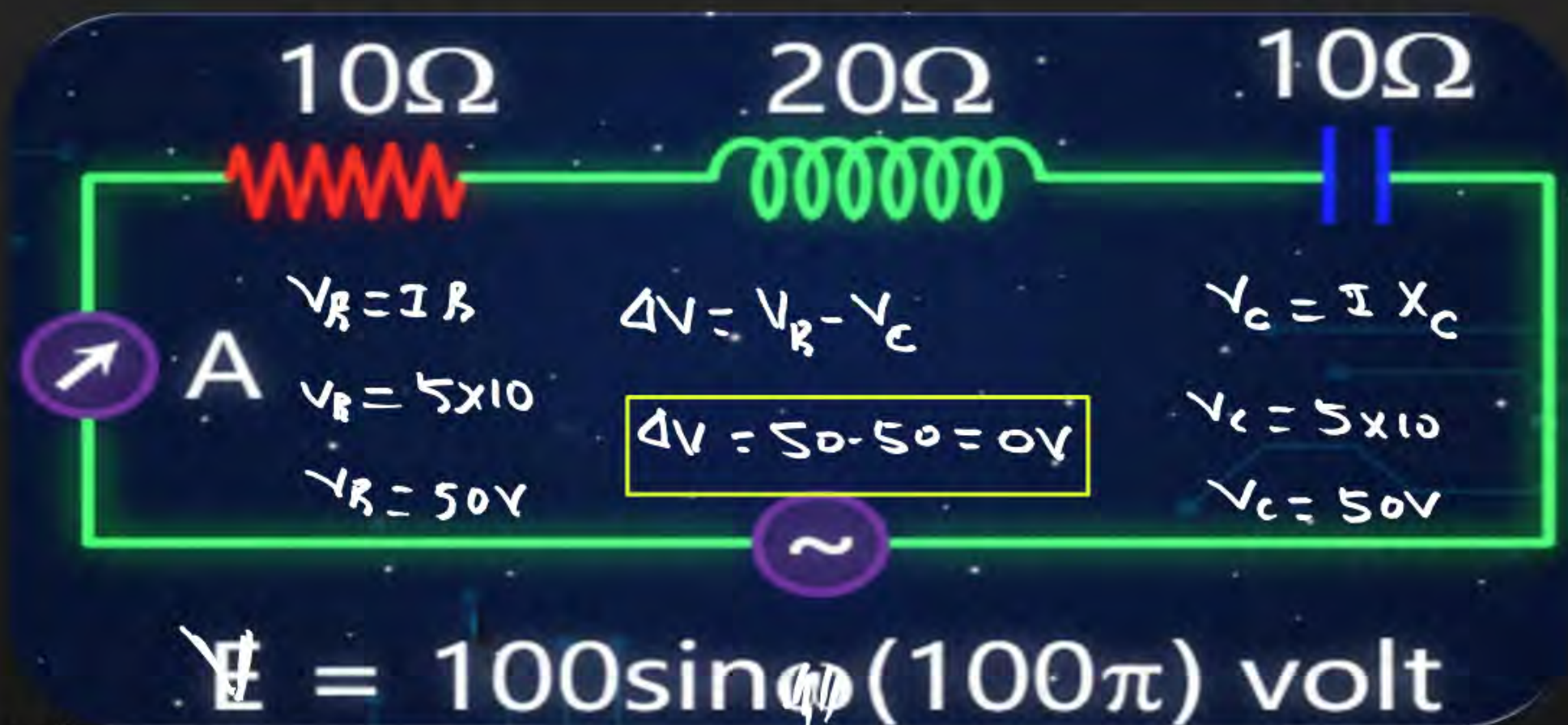
$$V_0 = 100 \text{ V}, \omega = 100\pi \text{ rad/s}$$



Question



In LCR circuit with an AC source $R = 300 \text{ ohm}$, $C = 20 \mu\text{F}$, $L = 1.0 \text{ H}$, $V_{\text{rms}} = 50\text{V}$ and $f = \frac{50}{\pi} \text{ Hz}$. Find RMS current in the circuit.

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = \omega L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_L = 100 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times \frac{50}{\pi} \times 20 \times 10^{-6}} = \frac{1}{2000 \times 10^{-6}}$$

$$X_C = 0.5 \times 10^3 = 500 \Omega$$

$$Z = \sqrt{(300)^2 + (100 - 500)^2}$$

$$Z = \sqrt{90000 + 160000}$$

$$Z = \sqrt{250000}$$

$$Z = 500 \Omega$$

$$I_{\text{rms}} = \frac{50}{500} = \frac{1}{10}$$

$$I_{\text{rms}} = 0.1 \text{ A}$$

$$I_{\text{rms}} = 100 \text{ mA}$$

Question



A sinusoidal voltage produced by an AC generator at any instant t is given by an equation $V = 311 \sin(314t)$. The rms value of voltage and frequency are respectively

$$V = V_0 \sin(\omega t)$$

A 220 V, 50 Hz

B 200 V, 100 Hz

C 220 V, 100 Hz ✗

D 200 V, 50 Hz ✗

$$V_0 = 311 \text{ V}$$
$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{311}{1.414}$$

$$V_{\text{rms}} = 220 \text{ V}$$

$$\omega = 314$$

$$\omega = 2\pi f$$

$$f = \frac{\omega}{2\pi} = \frac{314}{2 \times 3.14} = \frac{100}{2} = 50$$

$$f = 50 \text{ Hz}$$

Question



A series LCR circuit containing an AC source of 100V has an inductor and a capacitor of reactance's 24Ω and 16Ω respectively. If a resistance of 6Ω is connected in series, then the potential difference across the series combination of inductor and capacitor will be

- A** 8 V
- B** 40 V
- C** 80 V
- D** 400 V

$$X_L = 24\Omega$$

$$X_C = 16\Omega$$

$$R = 6\Omega$$

$$I = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{(6)^2 + (24 - 16)^2}$$

$$Z = \sqrt{36 + 64} = \sqrt{100} = 10\Omega$$

$$Z = 10\Omega$$

$$I = \frac{100}{10}$$

$$I = 10A$$

$$V_L = I X_L = 10 \times 24 = 240V$$

$$V_C = I X_C = 10 \times 16 = 160V$$

$$\Delta V = V_L - V_C = 240 - 160$$

$$\Delta V = 80V$$

Question



In a series L - C - R circuit, $R = 300\Omega$, $L = 0.9\text{H}$, $C = 2.0\mu\text{F}$ and $\omega = 1000\text{rad/s}$. then impedance of the circuit is

- A** 900Ω
- B** 500Ω
- C** 400Ω
- D** 1300Ω

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(300)^2 + (900 - 500)^2}$$

$$X_L = \omega L = 1000 \times 0.9$$

$$X_L = 900\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{1000 \times 2 \times 10^{-6}} = \frac{10^3}{2}$$

$$X_C = 500\Omega$$

$$= \sqrt{90000 + 160000}$$

$$= \sqrt{250000}$$

$$Z = 500\Omega$$

Question



In the given circuit the **peak voltage** across C, L and R are $30\text{ V}, 110\text{ V}$ and 60 V , respectively. The rms value of the applied voltage is

A 100 V

B 200 V

C 70.7 V

D 141 V


$$V_0 = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V_0 = \sqrt{(60)^2 + (110 - 30)^2}$$

$$V_0 = \sqrt{3600 + 6400}$$

$$V_0 = \sqrt{10000}$$

$$V_0 = 100\text{ V}$$

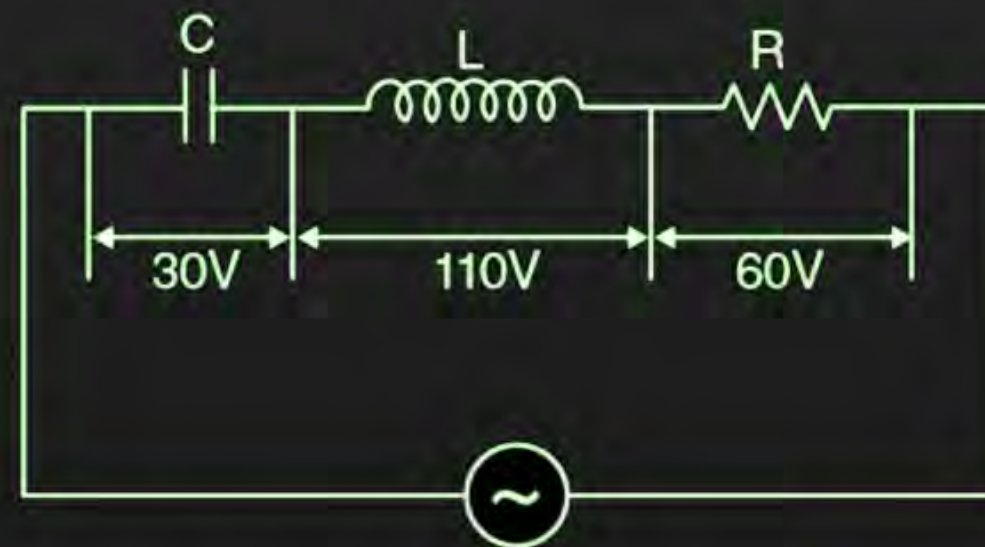

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{100}{\sqrt{2}} = 70.7\text{ V}$$

Question



L

C

An inductance of $\left(\frac{200}{\pi}\right)$ mH, a capacitance of $\left(\frac{10^{-3}}{\pi}\right)$ F and a resistance of 10Ω are connected in series with an AC source 220 V , 50 Hz . The phase angle of the circuit is

A $\frac{\pi}{6}$

B $\frac{\pi}{4}$

C $\frac{\pi}{2}$

D $\frac{\pi}{3}$

$$X_L = \omega L = 2\pi fL$$

$$X_L = 2\pi \times 50 \times \frac{200}{\pi} \times 10^{-3}$$

$$X_L = 20000 \times 10^{-3}$$

$$X_L = 20\Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times \frac{10^{-3}}{\pi}} = 10 = 10\Omega$$

$$\rightarrow \tan\phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$

$$\tan\phi = \frac{20 - 10}{10} = \frac{10}{10}$$

$$\tan\phi = 1$$

$$\tan\phi = \tan 45^\circ = \tan\left(\frac{\pi}{4}\right)$$

$$\phi = \frac{\pi}{4}$$



Series LCR Resonance Circuit

Resonance

A circuit is said to be resonant when the natural frequency of circuit is equal to frequency of the applied voltage.

Note : For resonance both L and C must be present in circuit.*

There are two types of resonance :

- (i) **Series Resonance** – Resonance is a condition where current is maximum in circuit.
- (ii) **Parallel Resonance** - Resonance is a condition where current is minimum in circuit.



Series LCR Resonance Circuit

(a) At Resonance

i. Reactance of 'L' and 'C' $\longrightarrow X_L = X_C$

ii. Voltage across 'L' and 'C' $\longrightarrow V_L = V_C$

iii. Phase difference, $\phi \longrightarrow 0^\circ$

iv. Impedance $\longrightarrow Z_{\min} = R$

v. Current $\longrightarrow I = \frac{V}{Z} = \frac{V}{R}$, $Z_{\min} \rightarrow I_{\max}$

$I = \frac{V}{R}$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{X_L - X_C}{R}$$

$$\phi = 0$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = R$$



Series LCR Resonance Circuit

(b) Resonant frequency

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

Angular
Frequency

$$\omega = 2\pi f$$

$$f_r = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$




Series LCR Resonance Circuit

(c) Variation of 'Z' with 'f'

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$
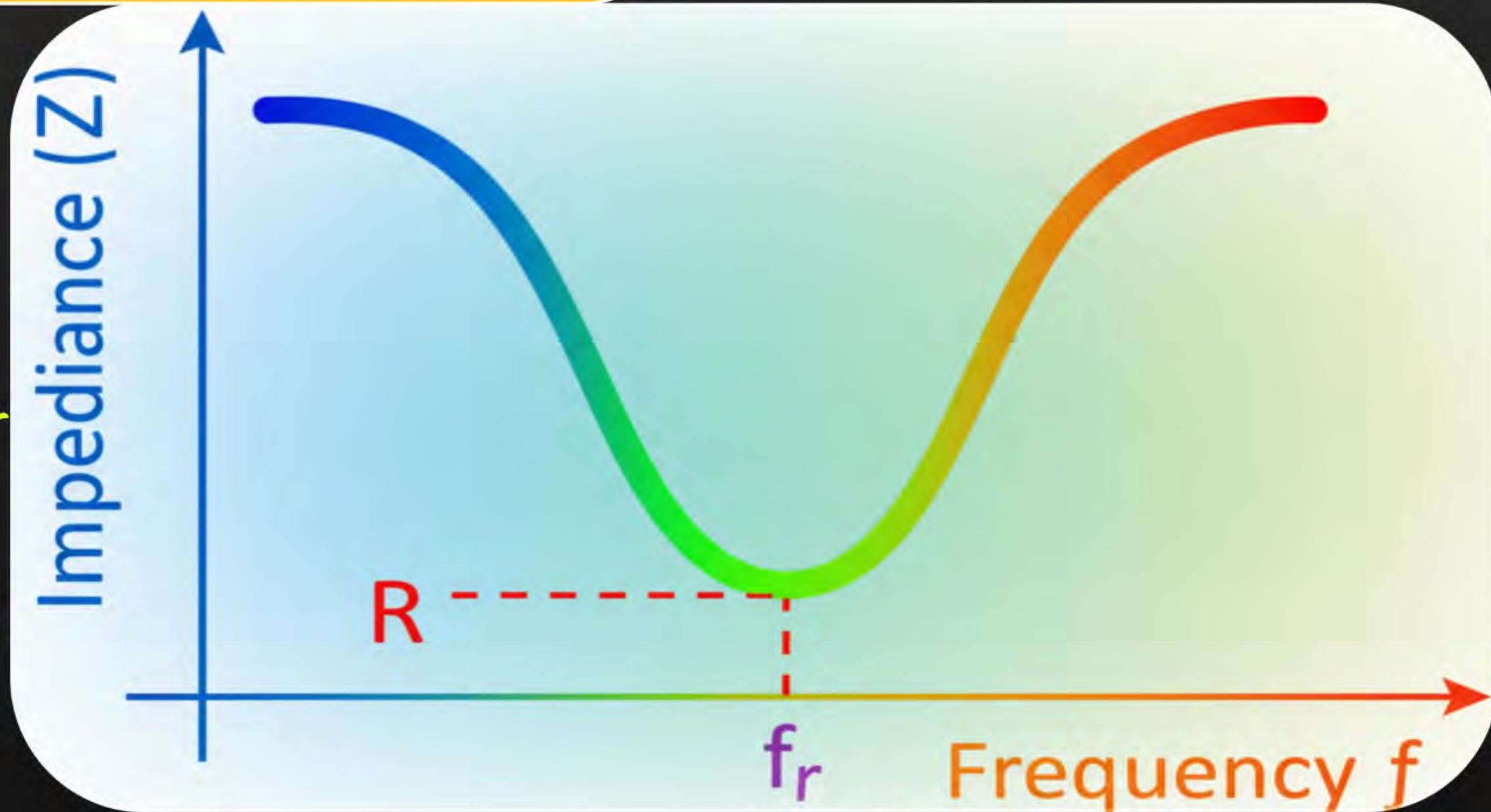
$$Z = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC} \right)^2}$$






Series LCR Resonance Circuit

(d) Variation of 'I' with 'f'

as f increase, Z first decreases then increase
 as f increase, I first increase then decreases

$$I = \frac{V}{Z}$$
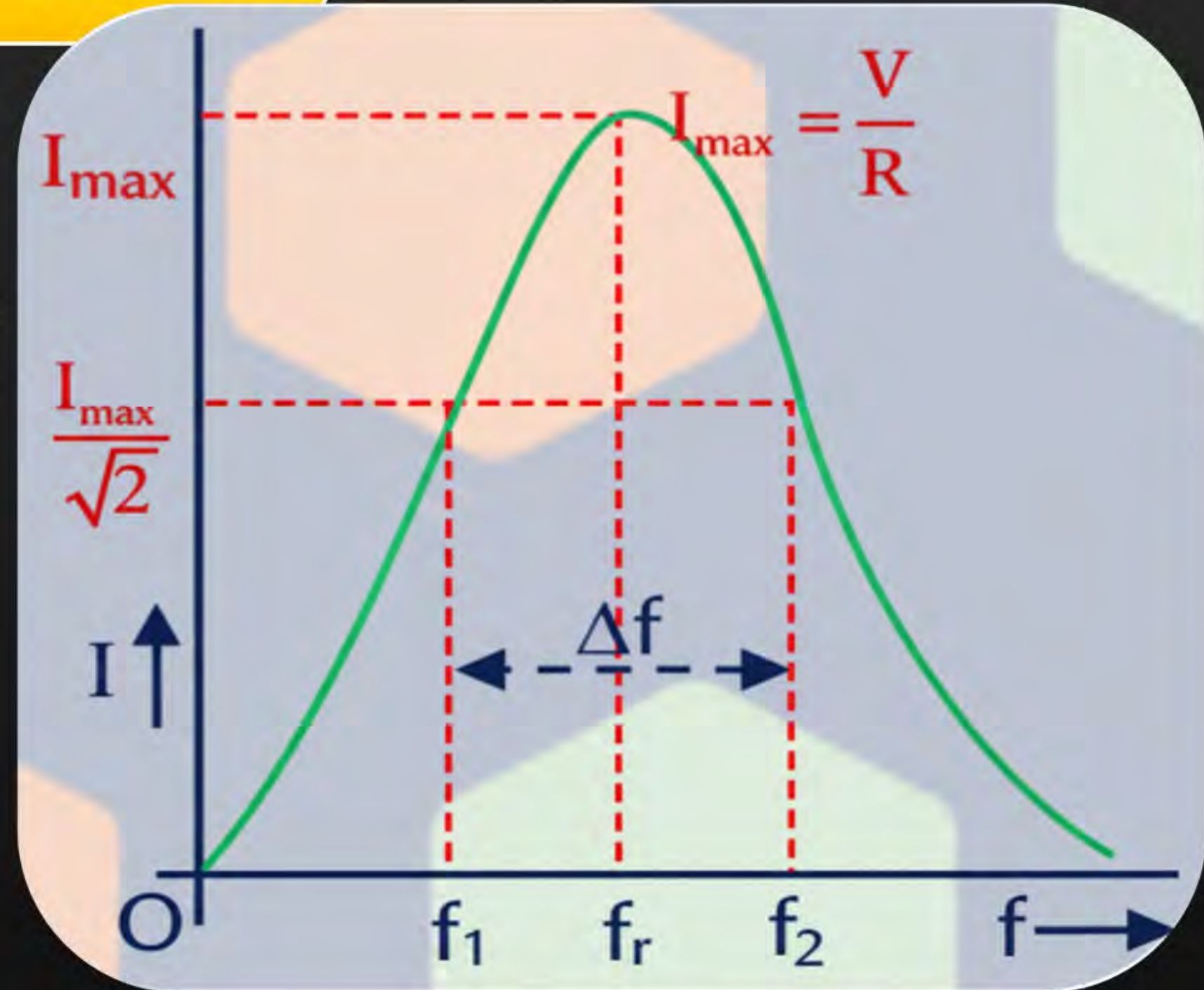
$$Z = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$



Question




For what frequency the voltage across the resistance R will be maximum.

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{\frac{1}{\pi} \times \frac{1}{\pi} \times 10^6}}$$

$$f = \frac{1}{2\pi \times \frac{1}{\pi} \times 10^{-3}} = 0.5 \times 10^3$$

$$f = 500 \text{ Hz}$$

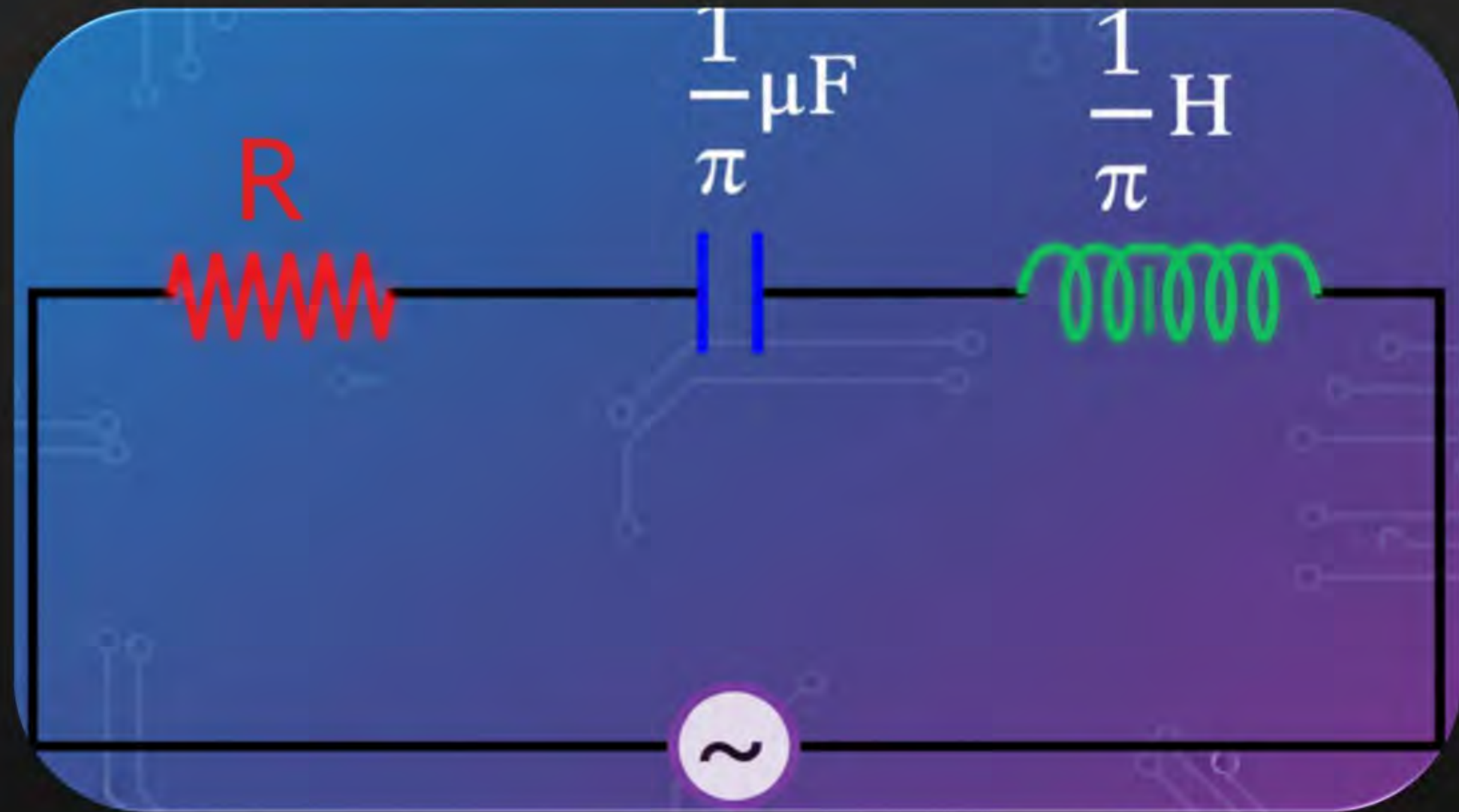

Question



$$P = V \Rightarrow V_{\text{rms}}$$

A light bulb is rated at 100W for a 220 V supply. Find

- the resistance of the bulb;
- the peak voltage of the source; and
- the rms current through the bulb.

(a) Resistance

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{(220)^2}{100}$$

$$R = 484 \Omega$$

$$(b) V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$$

$$V_0 = \sqrt{2} V_{\text{rms}}$$

$$V_0 = 1.414 \times 220$$

$$V_0 = 311 \text{ V}$$

$$(c) I_{\text{rms}} = \frac{V_{\text{rms}}}{R}$$

$$I_{\text{rms}} = \frac{220}{484}$$

$$I_{\text{rms}} = 0.45 \text{ A}$$

Question



In series $L - C - R$ circuit at resonance, the phase difference between voltage and current is

A Zero

B π

C $\frac{\pi}{4}$

D $\frac{\pi}{2}$

Question



A series resonant AC circuit contains a capacitance 10^{-6} F and an inductor of 10^{-4} H. The frequency of electrical oscillations will be

- A** 10 Hz
- B** $\frac{10^5}{2\pi}$ Hz
- C** $\frac{10}{2\pi}$ Hz
- D** 10^5 Hz

$$f = \frac{1}{2\pi \sqrt{LC}}$$

$$f = \frac{1}{2\pi \sqrt{10^{-4} \times 10^{-6}}} = \frac{1}{2\pi \times 10^{-5}}$$

$$f = \frac{10^5}{2\pi} \text{ Hz}$$

Question



In the given circuit, the resonant frequency is

- A** 15.92 Hz
- B** 159.2 Hz
- C** 1592 Hz
- D** 15910 Hz



$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2 \times 3.14 \sqrt{0.5 \times 10^{-3} \times 20 \times 10^{-6}}}$$

$$f = \frac{1}{6.28 \sqrt{10^{-8}}} = \frac{1}{6.28 \times 10^{-4}}$$

$$f = 0.159235 \times 10^4$$

1

$$f = 1592.35 \text{ Hz}$$

Question



In an $L - C - R$ circuit, at resonance

- A** The current is minimum ✗
- B** The current and voltage are in phase ✓
- C** The current leads the voltage by $\frac{\pi}{2}$ ✗
- D** The impedance is maximum ✗



Power in AC

$$P = IV = VI$$

Power in ac-circuit

The rate of doing work or the amount of energy transferred by a circuit per unit time is known as power in AC circuits.

It is used to calculate the total power required to supply a load.

Types

1. Instantaneous power ✓
2. Average power ✓
3. RMS Power ✓



Average power

power factor.

$$\cos\phi = \frac{R}{Z}$$

$$P = V_{\text{rms}} I_{\text{rms}} \cos\phi$$

AC circuit

$$P = \frac{V_0}{\sqrt{2}} \cdot \frac{I_0}{\sqrt{2}} \cdot \cos\phi$$

(i) $R \Rightarrow \phi = 0 \quad P = V_{\text{rms}} I_{\text{rms}} \neq 0$

(ii) $L \Rightarrow \phi = 90^\circ, \quad P = 0$


(iii) $C \Rightarrow \phi = 90^\circ \quad P = 0$

$$P = \frac{V_0 I_0}{2} \cdot \cos\phi$$



RMS Power

$$P_{rms} = V_{rms} I_{rms}$$

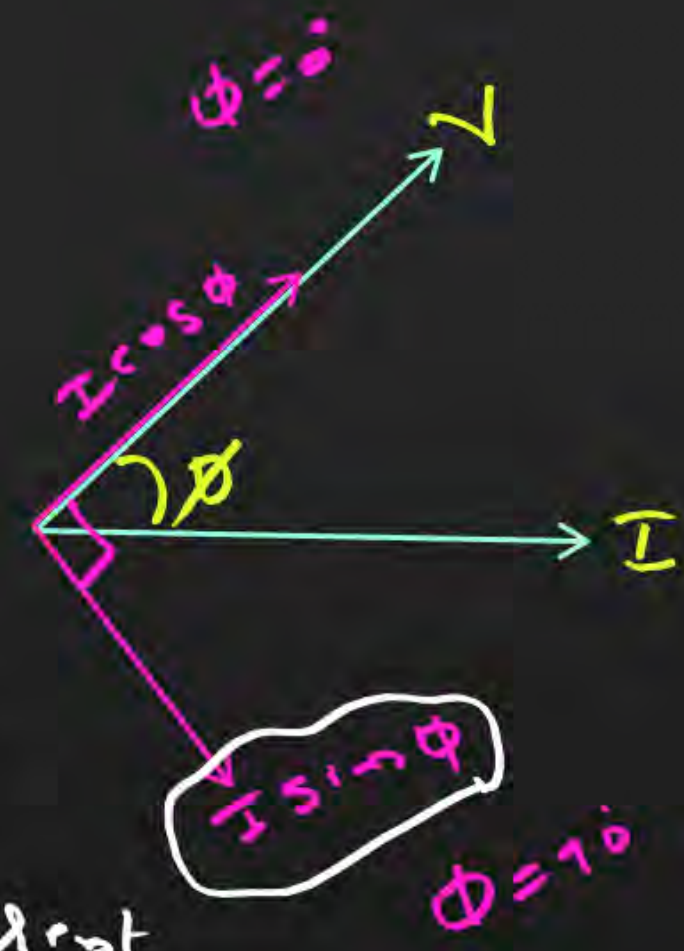

$I \cos \phi \rightarrow$ Watt current

$I \sin \phi \rightarrow$ Wattless current

Wattless current: That component of current in ac-circuit which is not active.

Note: $I \cos \phi$ is the activity component of current because it is in phase with applied voltage. But $I \sin \phi$ is the component which is inactive, called as wattless current because it is in $\frac{\pi}{2}$ phase with applied voltage.



Power factor

$$\cos \phi = \frac{R}{Z}$$

1. **Watt full Power:** Average power is also known as watt full power
2. **Wattless Power :** That component of current in ac-circuit which is not active.

Question

$$\begin{aligned}\cos \phi &= \cos 0 \\ &= 1 \rightarrow \text{unity}\end{aligned}$$



In an A.C. circuit V and I are given by $V = 100 \sin(100 t)$ V and $I = 100 \sin(100t + \pi/3)$ mA

Find power dissipated in the circuit ?

$$\hookrightarrow P = \frac{V_0 I_0}{2} \cos \phi$$

$$\phi = \frac{\pi}{3} = 60^\circ$$

$$P = \frac{100 \times 100 \times 10^{-3}}{2} \times \cos 60^\circ$$

$$P = \frac{10}{2} \times \frac{1}{2} = \frac{5}{2}$$

$$P = 2.5 \text{ W}$$

Question



A series R - L - C ($R = 10\Omega$, $X_L = 20\Omega$, $X_C = 20\Omega$) circuit is supplied by $V = 10 \sin \omega t$ V.

Find power dissipation in circuit.

$$I = \frac{V_0}{Z} = \frac{V_0}{R} = \frac{10}{10} = 1$$

$$X_L = X_C \Rightarrow \text{Resonant } \phi = 0$$

$$P = \frac{V_0 I_0}{2} \cos \phi$$

$$P = \frac{10 \times I_0}{2} \times \cos 0$$

$$P = 5I_0$$

$$P = 5 \times 1 = 5 \text{ W}$$

Question



In the series L-C-R circuit, the power dissipation is Through

- A** R
- B** L ✗
- C** C ✗
- D** Both L and C ✗

Question



In an AC circuit, V and I are given by $V = 150\sin(150t)$ volt and $I = 150\sin\left(150t + \frac{\pi}{3}\right)$ amp. The power dissipated in the circuit is

$$\phi = \frac{\pi}{3} = 60^\circ$$

$$P = \frac{I_0 V_0}{2} \cos \phi$$

$$P = \frac{150 \times 150}{2} \times \cos 60^\circ$$

$$P = \frac{150 \times 150}{2 \times 2} = 5625 \text{ W}$$

A 106 W

B 150 W

C 5625 W


D zero



Transformers


Transformer - It is device to increase or decrease the AC voltage.

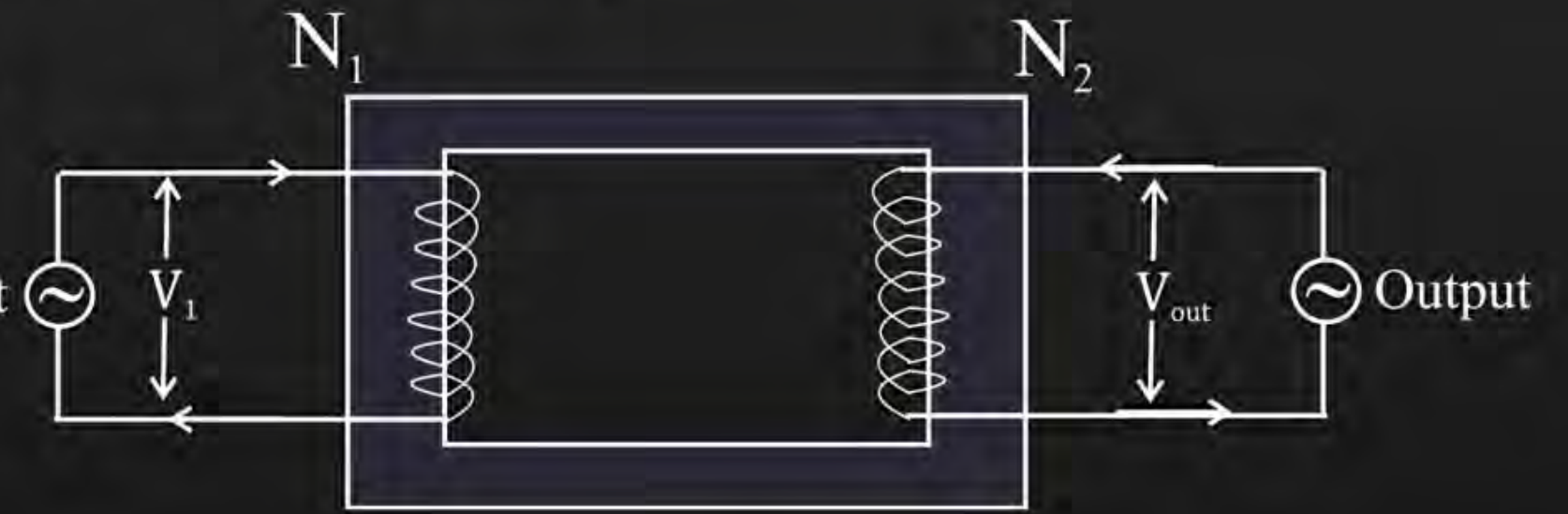- Types -**
- (i) Step up Tx $\Rightarrow V \uparrow$
 - (ii) Step down Tx $\Rightarrow V \downarrow$



Working Principle - Mutual Induction

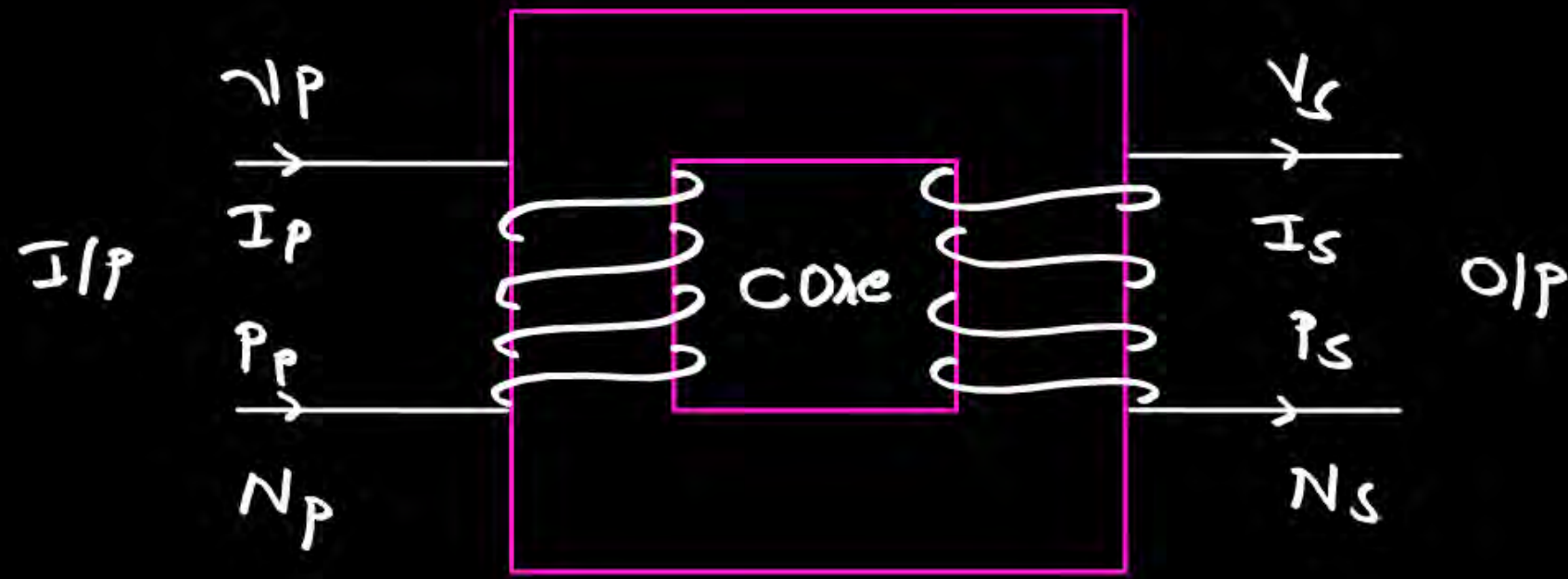It consist of two coils wound over soft iron core as shown in the figure. When current in the primary coil is changed the flux linked to the secondary coil also changes. Consequently, an emf is induced in the secondary coil due to Faraday law of EMI.



$\eta < 100\%$ $\eta < 1$

practical transformer

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s} = \eta$$

$$\eta = \frac{P_o}{P_i} = \frac{P_s}{P_p}$$

$$e = -N \frac{d\phi}{dt}$$

$$P = VI$$

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$$

Ideal transformer.

$$\eta = 100\%$$

$$\eta = 1$$


$$P_i = P_o$$

$$P_p = P_s$$



Transformers

Step Up Transformer

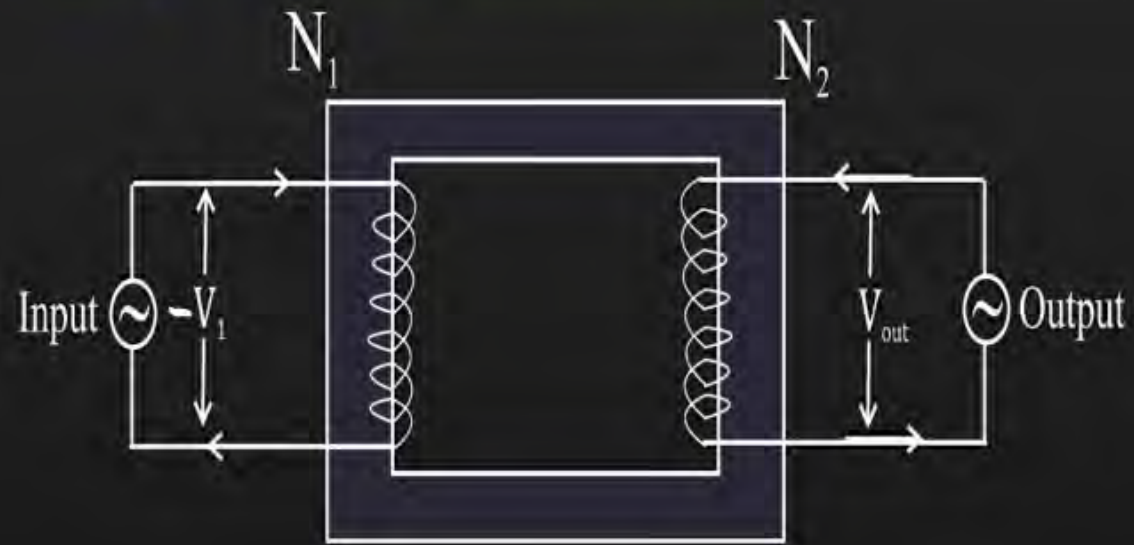


$$V_s > V_p$$

$$N_s > N_p$$

$$I_p > I_s$$

$$\eta = \frac{N_s}{N_p} > 1$$

Step down Transformer

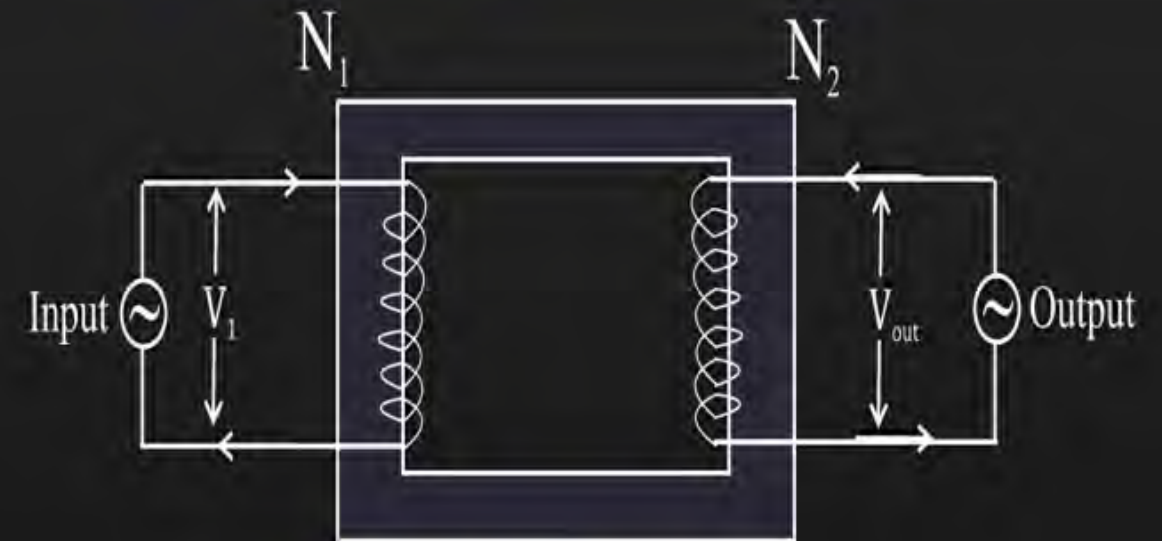

$$N_s < N_p$$

$$V_s < V_p$$

$$I_s > I_p$$

$$\eta = \frac{N_s}{N_p} < 1$$



Energy loss in Transformers

- (i) **Flux Leakage:** There is always some flux leakage; that is, not all of the flux due to primary passes through the secondary, It is due to poor design of the core or the air gaps in the core. It can be reduced by **winding the primary and secondary coils one over the other.**
- (ii) **Resistance of the windings:** The wire used for the windings has some resistance and so, energy is lost due to heat produced in the wire (I^2R). In high current, low voltage windings, these are minimised by using **thick wire**. $R = \rho \frac{l}{A}$ $R \propto \frac{1}{A}$ $A \uparrow R \downarrow$
- (iii) **Eddy currents:** The alternating magnetic flux induces eddy currents in the iron core and causes heating. The effect is reduced by using a **laminated core.**

Question



An ideal transformer has a turns ratio of 10 . When the primary is connected to 220 V , 50 Hz as source, the power output is

- A** 10 times the power input
- B** $\frac{1}{10}$ th the power input
- C** equal to power input
- D** zero

Question



A step-up transformer operates on a 230 V line and a load current of 2 A. The ratio of primary and secondary windings is 1:25. Then, the current in the primary is

 V_p I_s

$$\frac{N_p}{N_s} = \frac{1}{25}$$

 I_p

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} = \frac{I_p}{I_s}$$

$$\frac{N_s}{N_p} = \frac{I_p}{I_s} \Rightarrow \frac{25}{1} = \frac{I_p}{2}$$

$$I_p = 50 \text{ A}$$

A 25 A

B 50 A

C 15 A

D 12.5 A

Question



The output of a step down transformers is measured to be 48 V when connected to a 12 W bulb. The value of **peak current** is

A $\frac{1}{\sqrt{2}} A$

B $\sqrt{2} A$

C $\frac{1}{2\sqrt{2}} A$

D $\frac{1}{4} A$

$$V = 48V$$

$$P = 12W$$

$$P = IV$$

$$I = \frac{P}{V}$$

$$I_{rms} = \frac{12}{48} = \frac{1}{4} A$$

$$I_{rms} = \frac{I_0}{\sqrt{2}}$$

$$I_0 = \sqrt{2} \times I_{rms} = \sqrt{2} \times \frac{1}{4}$$

$$I_0 = \sqrt{\frac{2}{16}} = \frac{1}{\sqrt{8}} = \frac{1}{\sqrt{4 \times 2}} = \frac{1}{2\sqrt{2}}$$

$$I_0 = \frac{1}{2\sqrt{2}} A$$

Question



A step down transformer has 50 turns on secondary and 1000 turns on primary winding. If a transformer is connected to 220 V, 1 A AC source, what is output current of the transformer

A $\frac{1}{20} A$

B $20 A$

C $100 A$

D $2 A$

N_s N_p

V_p I_p I_s

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = \frac{I_p}{I_s}$$

$$\frac{50}{1000} = \frac{1}{I_s}$$

$$I_s = 20 A$$

Question



For a transformer, the turns ratio is 3 and its efficiency is 0.75. The current flowing in the primary coil is 2 A and the voltage applied to it is 100 V. Then the voltage and the current flowing in the secondary coil are... Respectively

$$n = \frac{N_s}{N_p} = 3$$

$$\eta = \frac{P_o}{P_i} = \frac{P_s}{P_p} = \frac{V_s I_s}{V_p I_p}$$

$$\frac{N_s}{N_p} = \frac{I_p}{I_s} = \frac{V_s}{V_p}$$

$$3 = \frac{V_s}{100} \Rightarrow V_s = 300 \text{ V}$$

$$0.75 = \frac{V_s I_s}{100 \times 2}$$

$$75 \times 2 = V_s I_s$$

$$V_s I_s = 150$$

$$\Rightarrow I_s = \frac{150}{300} = \frac{1}{2} = 0.5 \text{ A}$$

↳

A 150 V, 1.5 A

B 300 V, 0.5 A

C 300 V, 1.5 A

D 150 V, 0.5 A

Question



A transformer works on the principle of

- A** Self-induction
- B** Electrical inertia
- C** Mutual induction
- D** Magnetic effect of the electrical current



ELECTROMAGNETIC WAVES



KCET analysis of chapter – Marks weightage

Year	Topic
2025 (1Q)	Wavelength range of EMWs
2024(1Q)	Force exerted by an electromagnetic wave
2023(1Q)	Ratio of Magnitude of Electric field and Magnetic field
2022(2Q)	Radiations deflected by Electric Field, Highest wavelength of EMW
2021(2Q)	Properties of EMW and Source of EMW




KCET analysis of chapter – Marks weightage

Year	Topic
2020(1Q)	Intensity and momentum
2019(2Q)	Direction of propagation of EMW and properties of EMW
2018	-
2017(1Q)	Direction of propagation of EMW
2016(2Q)	Uses of EM-Radiation and Magnetic field vector
2015	-



Displacement Current

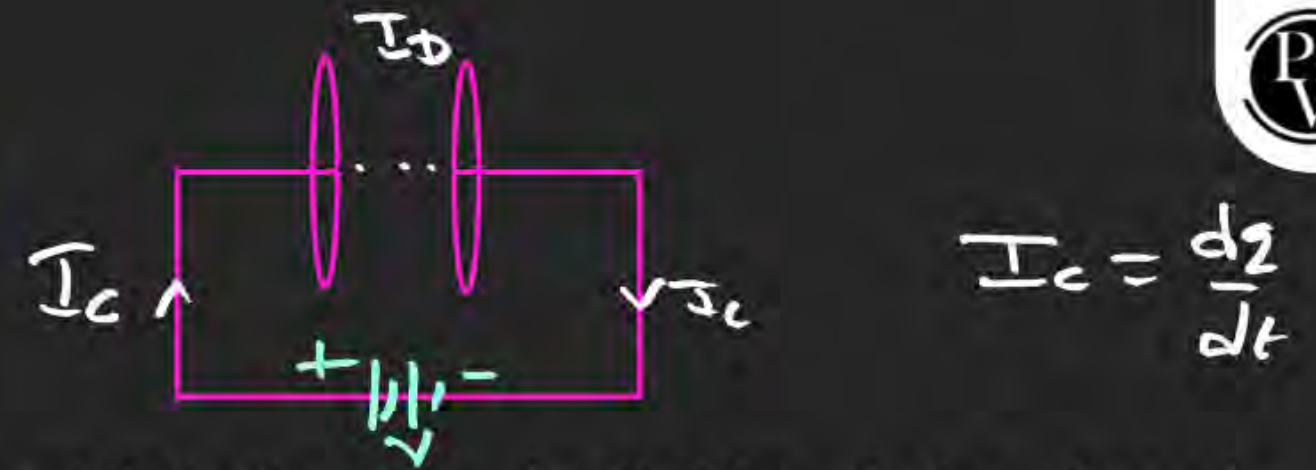

The current which comes into existence in the region in which the electric field and the electric flux is changing with time is known as displacement current. It is expressed by

$$I_D = \epsilon_0 \frac{d\phi_E}{dt}$$

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 (I_c + I_D) = 0$$

I_D

$B \Rightarrow \rightarrow$ No defn

Where ϕ_E is the electric flux and I_D is the displacement current.

Need for Displacement Current

Ampere's circuital law for conduction current during charging of a capacitor was found inconsistent. Therefore, Maxwell modified Ampere's circuital law by introducing the concept of displacement current.



Maxwell's Equation

✓ 1. $\oint \vec{E} \cdot \vec{ds} = \frac{q_{in}}{\epsilon_0}$ - Gauss Law of Electrostatics

✓ 2. $\oint \vec{B} \cdot \vec{ds} = 0$ - Gauss Law of Magnetism

✓ 3. $\int \vec{E} \vec{dl} = - \frac{d\phi_B}{dt}$ - Faraday and Lenz's law


4. $\oint \vec{B} \cdot \vec{dl} = \mu_0 \left(i_C + \epsilon_0 \frac{d\phi_E}{dt} \right)$ - Modified Maxwell's - Ampere's Circuital law



Electromagnetic Waves

An electromagnetic wave is a wave radiated by an **accelerated or oscillatory charge** in which varying magnetic field is the source of electric field and varying electric field is the source of magnetic field. Thus, two fields become source of each other and the wave propagates sinusoidally in a direction perpendicular to both the fields.

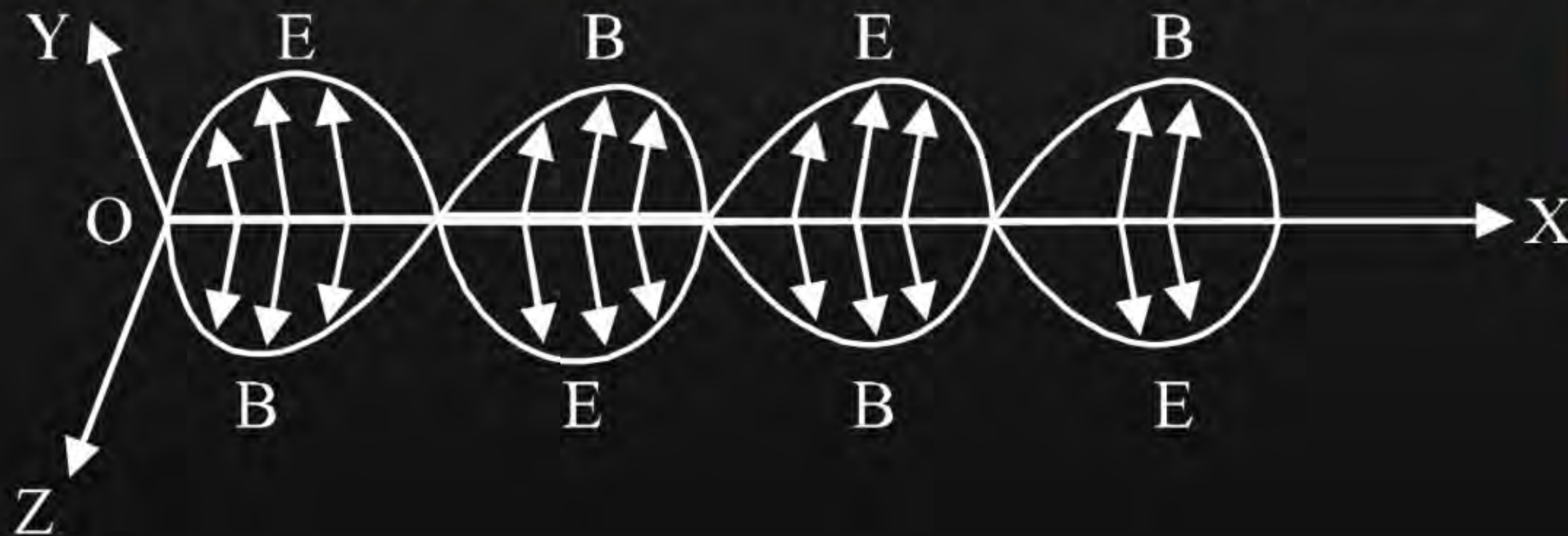Electromagnetic waves are transverse in nature, i.e. electric and magnetic fields are perpendicular to each other and also perpendicular to the direction of wave propagation.



$$\vec{E} \times \vec{B} = \vec{c} = \vec{v}$$

$$\vec{E} \perp \vec{B} \perp \vec{v}$$



Relation between magnitudes of \vec{E} & \vec{B} in a Free space

$$\frac{E}{B} = c \rightarrow \text{Free space}$$

$$\frac{E_0}{B_0} = c$$

$$\frac{E}{B} = v \rightarrow \text{medium}$$

$$\frac{E_0}{B_0} = v$$



Important Characteristics of EMW's

- (i) The electromagnetic waves are produced by accelerated charge. → Transverse
- (ii) These waves do not require any material medium for propagation. → Non-mechanic
- (iii) These waves travel in free space with the speed of light ($3.0 \times 10^8 \text{ ms}^{-1}$), given by the relation

$$c = 1/\sqrt{\mu_0 \epsilon_0}$$


Light waves are electromagnetic.

- (iv) The directions of variations of electric and magnetic fields are perpendicular to each other and also perpendicular to the direction of propagation. Thus, electromagnetic waves are **transverse in nature.** $\vec{E} \perp \vec{B} \perp \vec{v}$

- (v) The variations in electric and magnetic fields occur simultaneously and the fields acquire their maximum values E_0 and B_0 at the same place and at the same time.



Electromagnetic Spectrum

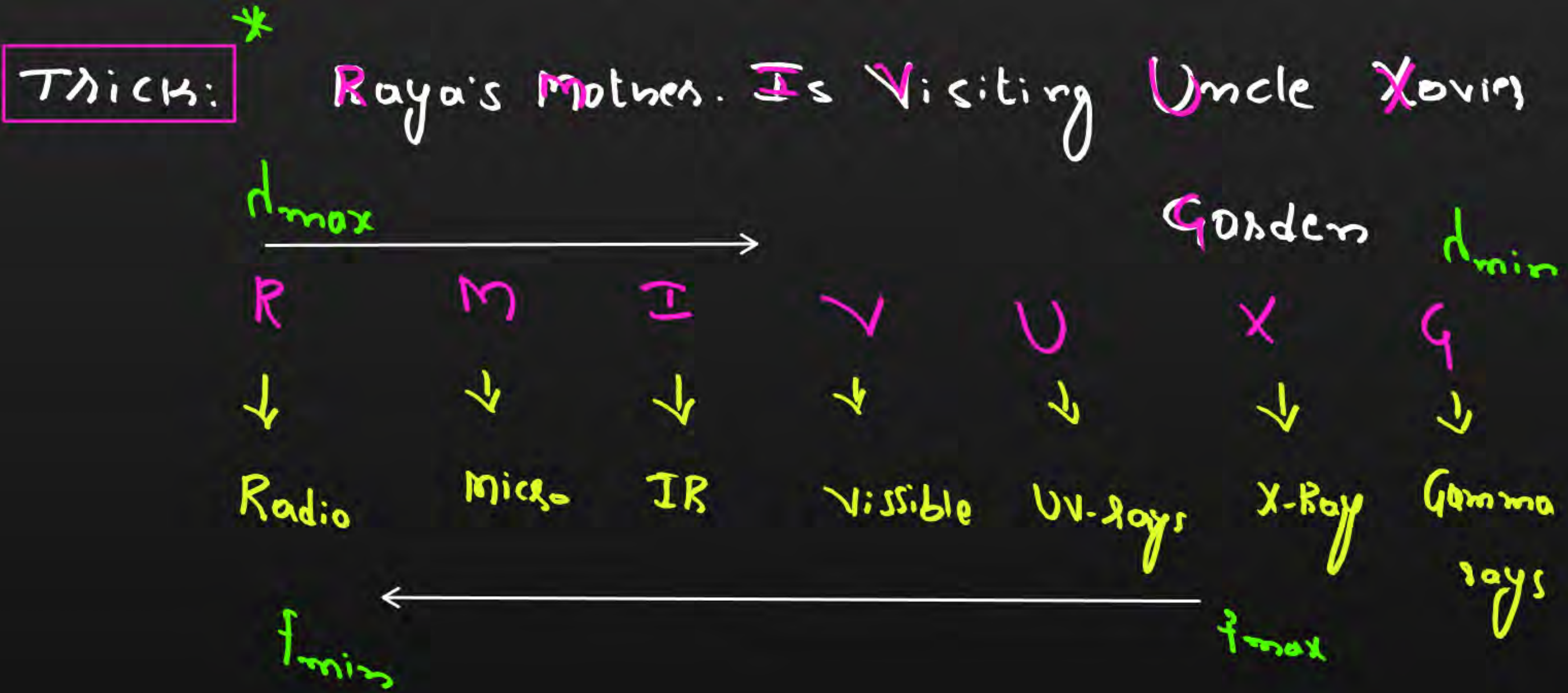

Question



The ratio of the magnitudes of electric field to the magnetic field of an electromagnetic wave is of the order of

$$\frac{E}{B} = c = 3 \times 10^8 \text{ m/s} \rightarrow \text{Free space} \rightarrow c \checkmark$$

- A** 10^{-8} ms^{-1}
- B** 10^5 ms^{-1}
- C** 10^{-5} ms^{-1}
- D** 10^8 ms^{-1}

Question



Which of the following radiations is deflected by electric field?

- A** Neutrons +
- B** γ -rays +
- C** α -particles ✓
- D** X-rays +

All EMWS \rightarrow Electrically Neutral

Question



Which of the following radiations of electromagnetic waves has the highest wavelength?

A UV-rays

B IR-rays

C Microwaves

D X-rays

Question



The source of electromagnetic wave can be a charge

- A** moving with a constant velocity ✗
- B** moving in a circular orbit ✓
- C** at rest ✗
- D** moving parallel to the magnetic field ✓

Question



An electromagnetic wave is travelling in x -direction with electric field vector given by, $E_y = E_0 \sin(kx - \omega t)\hat{j}$. The correct expression for magnetic field vector is

A $B_y = E_0 C \sin(kx - \omega t)\hat{j}$ ✗

B $B_y = E_0 C \sin(kx - \omega t)\hat{k}$

C $B_y = \frac{E_0}{C} \sin(kx - \omega t)\hat{j}$ ✗

D $B_y = \frac{E_0}{C} \sin(kx - \omega t)\hat{k}$

$$\vec{E} \times \vec{B} = \vec{c} = \vec{v}$$


$$\vec{E}_y = E_0 \sin(kx - \omega t)\hat{j}$$

$$\vec{B}_y = B_0 \sin(kx - \omega t)\hat{k}$$

$$E_0 = B_0 C$$

$$B_0 = \frac{E_0}{C}$$
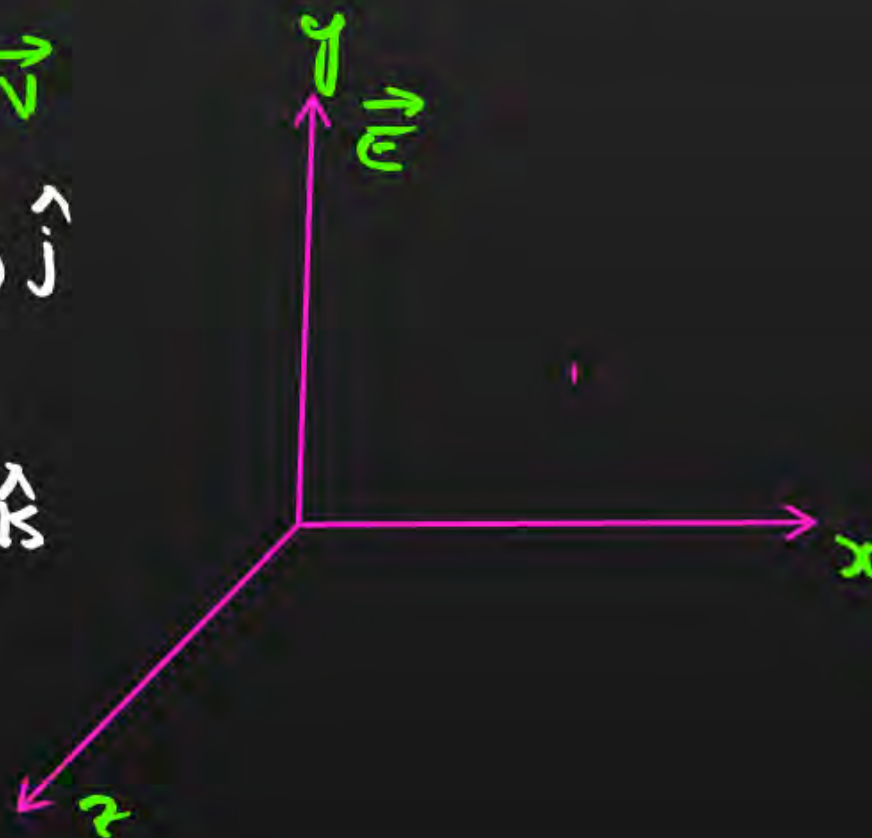
$$\vec{B}_y = \frac{E_0}{C} \sin(kx - \omega t)\hat{k}$$



Question



If E and B represent electric and magnetic field vectors of an electromagnetic wave, the direction of propagation of the wave is along

- A** $E \times B$
- B** $B \times E$
- C** E
- D** B

Question



Electromagnetic radiation used to sterilize milk is

- A** X-rays
- B** γ -rays
- C** UV rays
- D** Radio waves

Question



A plane electromagnetic wave of frequency 20 MHz travels through a space along x -direction. If the electric field vector at a certain point in space is 6 Vm^{-1} , what is the magnetic field vector at that point?

7.2

A $2 \times 10^{-8} \text{ T}$

B $1/2 \times 10^{-8} \text{ T}$

C T

D $1/2 \text{ T}$

$$\frac{E_0}{B_0} = c$$

Question



X-rays, gamma rays and microwaves travelling in **vacuum** have

- ✓ ✗

A same velocity and same frequency
- ✗ ✗

B same wavelengths but different velocities
- ✗ ✗

C same frequency but different velocities
- ✓ ✓

D same velocity but different wavelengths

Question



The speed of electromagnetic wave in **vacuum** depends upon the source of radiation

- A** increases as we move from γ -rays to radio waves
- B** decreases as we move from γ -rays to radio waves
- C** **is same for all of them**
- D** None of the above

Question



If μ_0 is permeability of free space and ϵ_0 is permittivity of free space, the speed of light in vacuum is given by

- A** $\sqrt{\mu_0 \epsilon_0}$
- B** $\sqrt{\mu_0 / \epsilon_0}$
- C** $\sqrt{1 / \mu_0 \epsilon_0}$
- D** $\sqrt{\epsilon_0 / \mu_0}$

Question



All components of the electromagnetic spectrum in **vacuum** have the same

$$\checkmark E = h\nu = hf$$

- A** energy
- B** **velocity**
- C** wavelength
- D** frequency

Thank

You