

# Electricity

# THE GUN SHOT

100% Exam Paper yahi se hoga

### **Learning Outcomes**

- **Electric Current**
- Potential Difference
- Resistance
- Ohm's Law
- Series & Prallel Combination
- **Electric Circuits**
- **Electric Power & Energy**
- Heating Effect Of Current & Joule's Law

Lots Of Numericals

40 + PYQS

#### Charge (Q)



Two types of charge: Positive charge 🛑 & Negative charge 🗕




Unlike charges attract,

S. I. unit of charge: Coulomb (C)

Smallest independent charge: Charge on e (Fundamental charge)/

# Current (I)

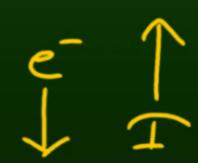

#### Current is rate of flow of positive charge.

Current 
$$T = 0$$
 ) time (s)



(A)

Direction of current: Opposite to the flow of e

(Q)Kyu ayl Thi?



S.I unit of current: Ampere (A)

other popular unit - mA 
$$1 \text{ mA} = 10^{-3} \text{A}$$
  
 $\text{Micro}$   $1 \text{ uA} = 10^{-6} \text{A}$ 

1.An electric source can supply a charge of 500 coulomb. If the current drawn by a device is 25 mA. Find the time in which the electric source will be discharged completely.

- **A** 30,000 s
- **B** 48,000 s
- **C** 60000 s
- 20,000 s

$$Q = 500C$$
  
 $i = 25mA = 25x10^{3}A$   
 $t = ?$ 

$$0 = Tt$$
  
 $500 = 25 \times 10^{-3} \times t$ 

(CBSE 2024)

### **Potential Difference (V)**




$$Q = It$$



Potential difference between two points is amount of work done in moving a unit charge (1 C) from one point to the other.



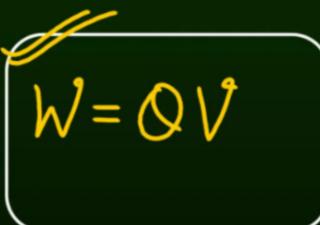V = Potential difference (Volt) W = Work done (joule) Q = Charge (Coulomb)



S.I unit of P.D. is volt (V)

2.Define the term "potential difference" between two points in an electric circuit carrying current. Name and define its S.I. unit. Also express it in terms of S.I. unit of work and charge.

## 3.Calculate the amount of work done by a cell when 20 C of charge is moved through a P.D. of 3V

6.66 J

$$W = ?$$

**B** 66 J

$$Q = 200$$


$$W = QV$$

$$= 20 \times 3$$


$$= 60.5$$



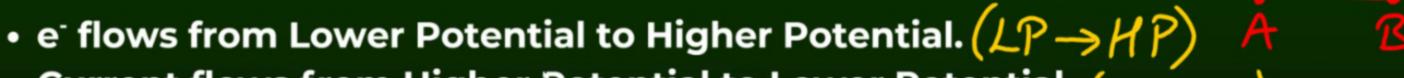
#### Why Current Flows? - Potential Difference (V) [PD]



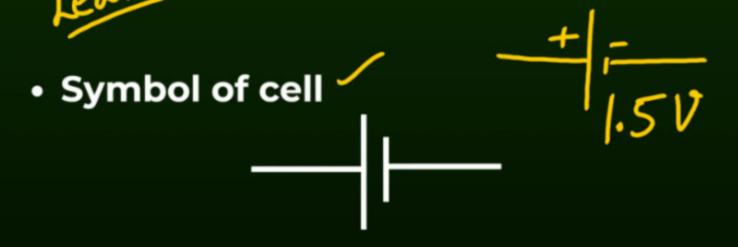• Current flows from Higher Potential to Lower Potential. (ガアー) しょうしゃ



Combination of cells - Battery

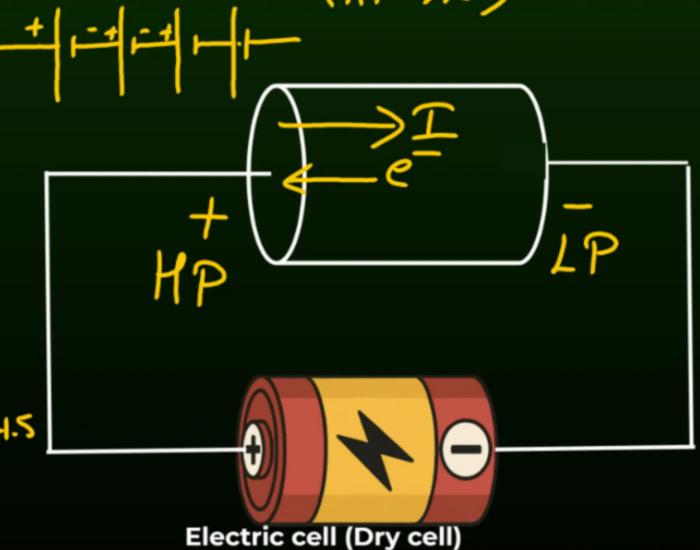

- 4. Assertion (A): Electrons move from lower potential to higher potential in a conductor. /
- Reason (R): A dry cell maintains electric potential difference across the ends of a conductor.
- (a) Both Assertion (A) and Reason (R) are true and Reason (R) is the correct explanation of the Assertion (A).
- (b) Both Assertion (A) and Reason (R) are true, but Reason (R) is not the correct explanation of the Assertion (A).
- (c) Assertion (A) is true, but Reason (R) is false.
- (d) Assertion (A) is false, but Reason (R) is true.

(CBSE 2024)


ローエーシェ

Wータイク. Wywx

### Resistance (R)



Free electron

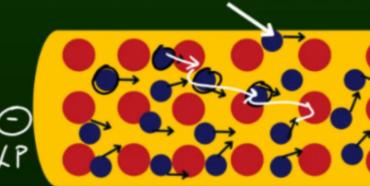

Property of a conductor to oppose the flow of electric current


Factors on which resistance of conductor depends:

1) Length (I) 
$$\mathcal{R} \propto \mathcal{L}$$




Resistivity (p) - property of material

4) Temperature

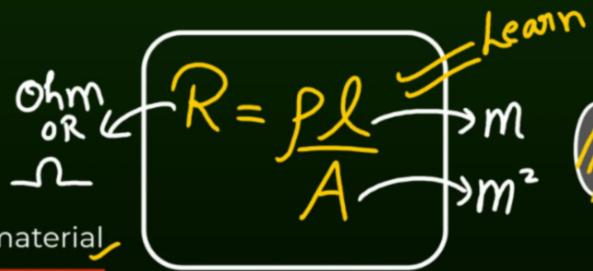



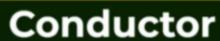




I - length A - Area of cross section

• S.I. unit of R:- Ohm or 
$$\Omega$$

$$MP P = \frac{RA}{l} \rightarrow \underbrace{n}_{m} \rightarrow \underbrace{n}_{m}$$
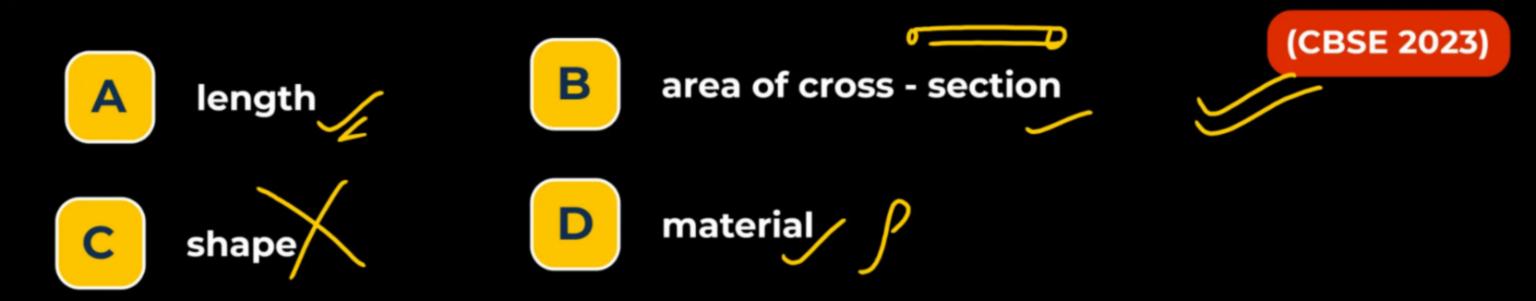
#### 5. The resistance of a wire does not depend on its:



6.Write the relation between resistance R and electrical resistivity  $(\rho)$  of the material of a conductor in the shape of cylinder of length (I) and area of cross-section (A). Hence derive the SI unit of electrical resistivity.

$$R = PL$$
 $P = RA \Rightarrow R$ 

(CBSE 2025, 2024, 2023)

Resistivity (P) only on Matorial R PX R= 12

ullet Resistivity (
ho) is a property of the material. Does not change with shape & size of material (like length, Area, Diameter or radius)

• Resistivity order: Metals < Allo	ys < Insulators
------------------------------------	-----------------

- Copper & aluminium are used for transmission lines.
- Insulators like rubber & glass have high ho Poor conductors
- SI unit of resistivity is Ohm m.

Material	Resistivity (Ω·m)
A Insulator	1017/
B Alloy	44 × 10 <sup>-6</sup> /
C Metal	1.62 × 10-8/

(CBSE 2025)

Potential difference is measured by an instrument->Voltmeter.



Electric Current is measured by an instrument -> Ammeter




7.The resistance of a metal wire of length 3m is  $60~\Omega$ . If the area of cross-section of the wire is 4 x  $10^{-7}~\text{m}^2$ , calculate the electrical resistivity.  $(\rho)$  How will the resistivity of the wire change if the length and diameter of the wire both are doubled? Justify your answer.

$$\begin{array}{lll}
l = 3m & R = pl & \text{(CBSE 2025, 2023, 2022, 2021)} \\
R = 60 \Omega & A & 20 & l \rightarrow 2l \\
A = 4 \times 10^{-7} m^2 & S = RA = 60 \times 4 \times 10^{-7} & \text{old} \rightarrow 2d \\
S = ? & = 80 \times 10^{-7} \Omega \text{ m} & S \rightarrow 2d
\end{array}$$


$$= 8 \times 10^{-6} \Omega \text{ m}$$

Resistivity is a property of the material. Does not change with shape & size of material (like length, Diameter)

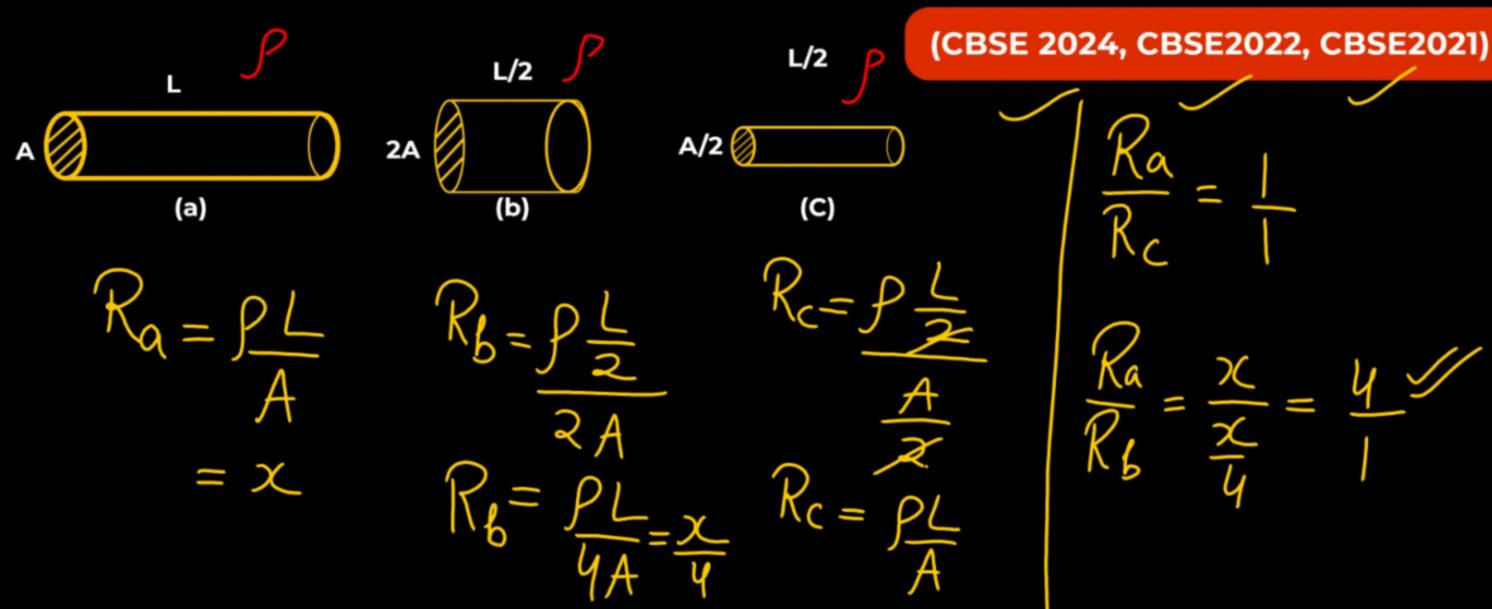8. In the following figure, three cylindrical conductors A, B and C are shown along with their lengths and areas of cross - section. If they are made of same material, find  $R_a/R_b$  &  $R_a/R_c$ .



9. A wire of given material having length (I) and area of cross-section (A) has a resistance of 4N. Find the resistance of another wire of the same material having length I/2 and area of cross - section 2A.

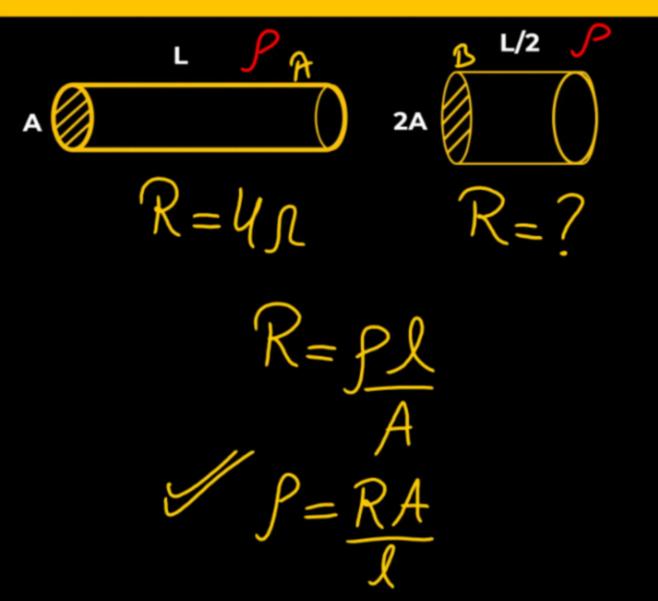

(CBSE 2021)

$$R = I$$

11.The resistance of a wire of 0.01 cm radius is 1000 If the resistivity of the wire 50 x 10<sup>-8</sup>  $\Omega$  m, find the length of this wire.

$$8 = 0.01 \text{ cm} = 0.01 \times 10^{-2} \text{ R} = PL \quad A = 118^{2} \quad \text{CBSE Term 2}$$


$$R = 10 \Omega = \frac{1}{100} \times 10^{-2} \quad A = 118^{2} \quad \text{(2021-2022)}$$

$$9 = 50 \times 10^{-8} \text{ m} \quad 0 = 50 \times 10^{-8} \times 1 = \frac{50 \times 10^{-8} \times 1}{3.14 \times 10^{8}} \quad 1 = \frac{3.14}{5} = 0.62 \text{ m}$$

$$10 = \frac{50 \times 10^{-8} \times 1}{3.14 \times 10^{8}} \quad 1 = \frac{3.14}{5} = 0.62 \text{ m}$$

$$R_a = PL \atop A$$

$$Lengthy R_a = \sqrt{R_b}$$

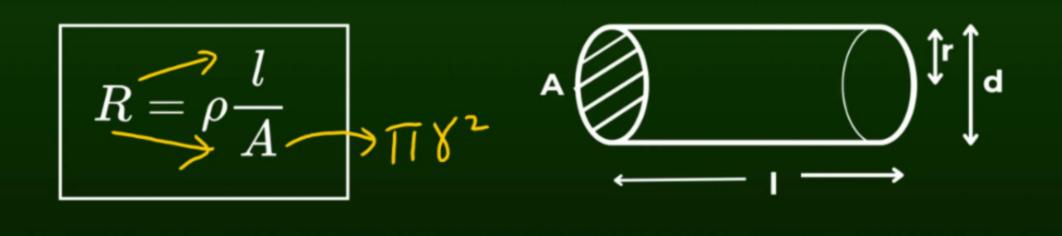

Area of circle , A = 
$$\pi r^2$$

$$R = \rho \frac{l}{\pi r^2} \qquad \begin{array}{c} R \propto l \Rightarrow 2l \quad 2R \stackrel{1}{\searrow} \stackrel{R}{\searrow} \\ R \propto \frac{1}{A} \Rightarrow 2A \stackrel{R}{\searrow} \stackrel{1}{\searrow} \stackrel{2}{\searrow} \\ R \propto \stackrel{1}{\searrow} \Rightarrow 2\chi \stackrel{R}{\searrow} \stackrel{1}{\searrow} \stackrel{1}{\Longrightarrow} \stackrel{1}{$$

r and d are given in mm, cm
$$1 mm = 10^{-3} m$$

$$1 cm = 10^{-2} m$$

10. How much does the resistance change, if the diameter of

the wire is doubled?  $d \rightarrow 2d$ 

**CBSE 2024** 

12. A copper wire has a diameter of 0.2 mm and resistivity of 1.6 x 10-8 m. What will be the length of this wire to make its resistance 14? How much does the resistance change, if the diameter of the wire is doubled?

$$d = 0.2 \text{ mm} = 0.2 \times 10^{-3} \text{m}$$


$$Y = \frac{d}{2} \text{ pr} \quad 1 \Rightarrow ?? \quad R = 142$$

$$|d \Rightarrow 2|$$

$$|d \Rightarrow 2|$$

$$|d \Rightarrow 2|$$

HOMEWORK, COMMENT THE ANSWER

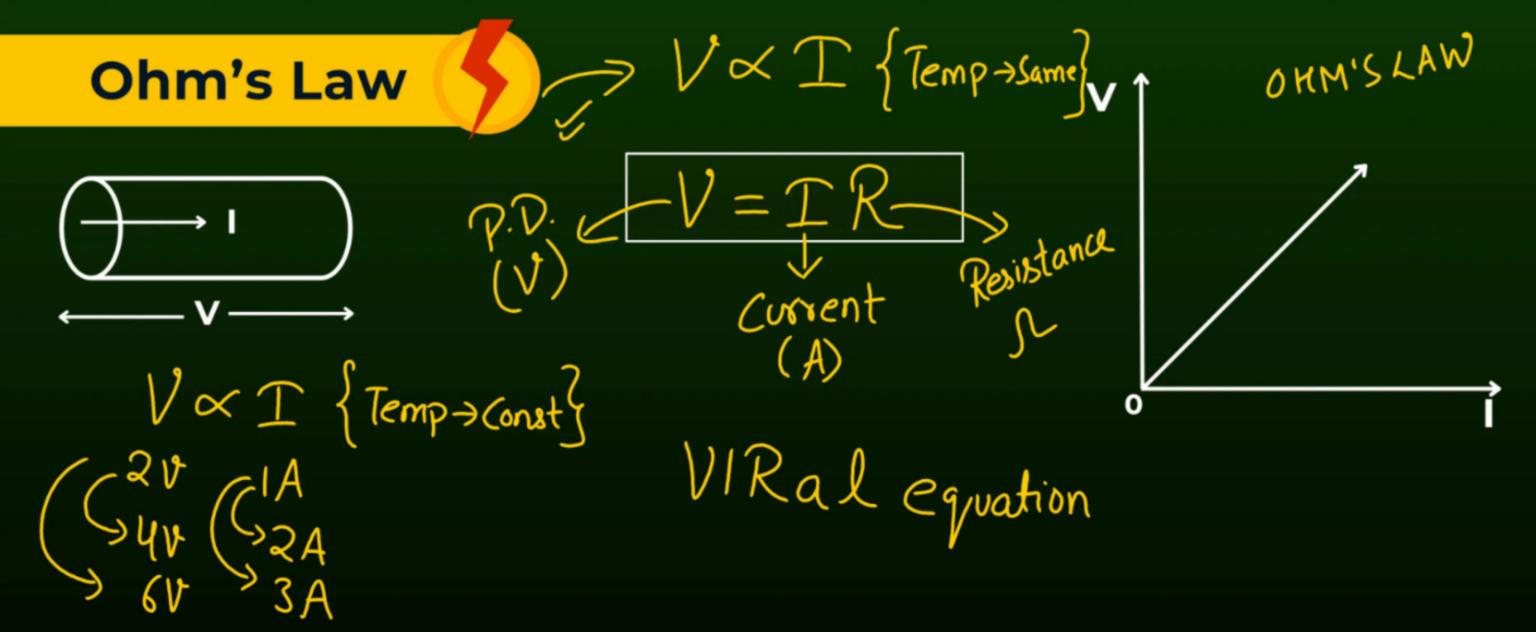


The potential difference V, across the ends of a metallic conductor is directly proportional to the current flowing through it provided its temperature remains the same.

13. The potential difference across the two ends of a circuit component is decreased to one - third of its initial value, while its resistance remains constant. What change will be observed in the current flowing through it? Name & state the law which helps us to answer this answer.

(CBSE 2024, CBSE 2023, CBSE 2020, 2019,2016)

OHM'S LAW

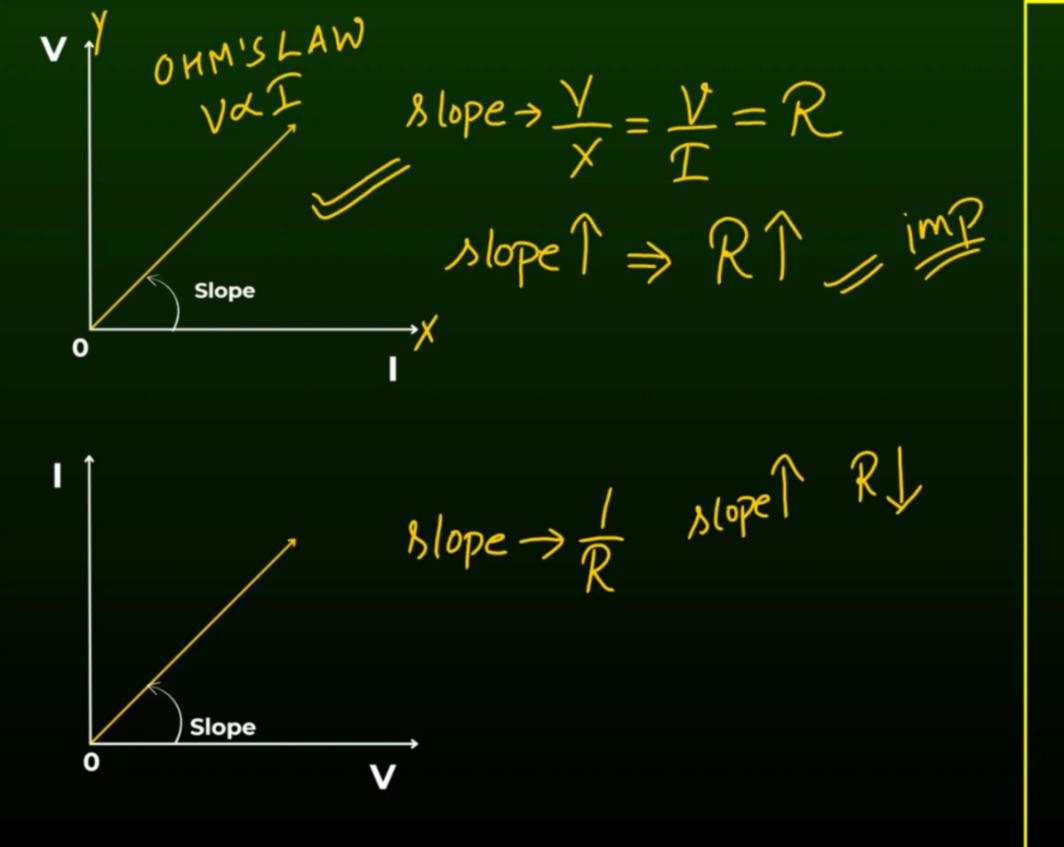OHM'S LAW - The potential difference V, across the ends of a metallic conductor is directly proportional to the current flowing through it provided its temperature remains the same .





$$R_3 > R_1 > R_2$$
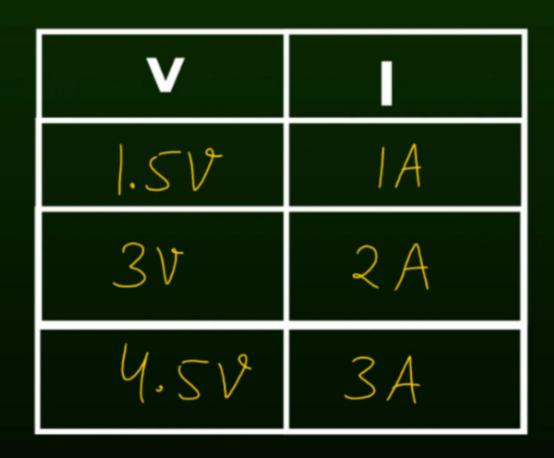
#### Ohm's Law & Experimental setup




CBSE Term 2 (2021-2022) CBSE 2021 ,CBSE 2020




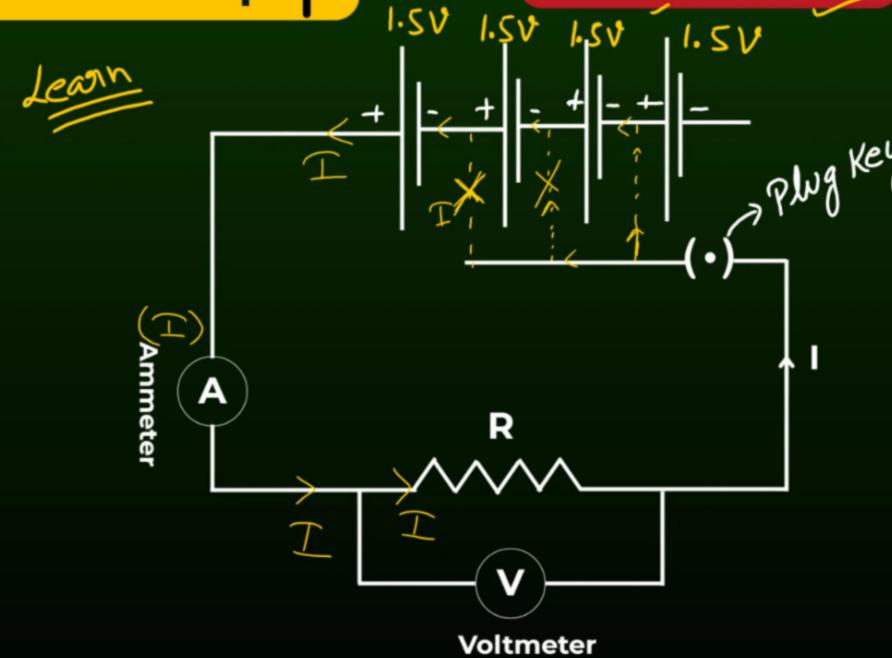


### V=IR


#### **Combination of Resistors**

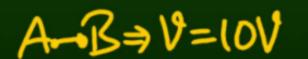

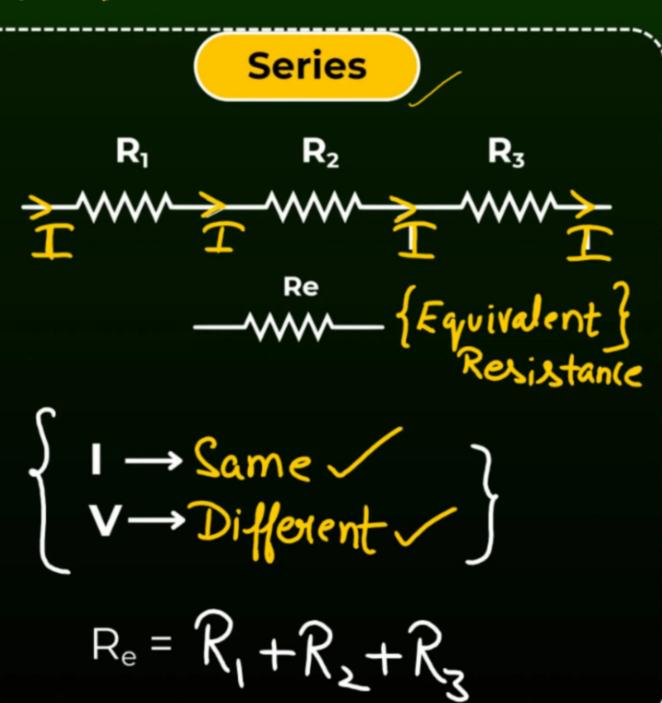

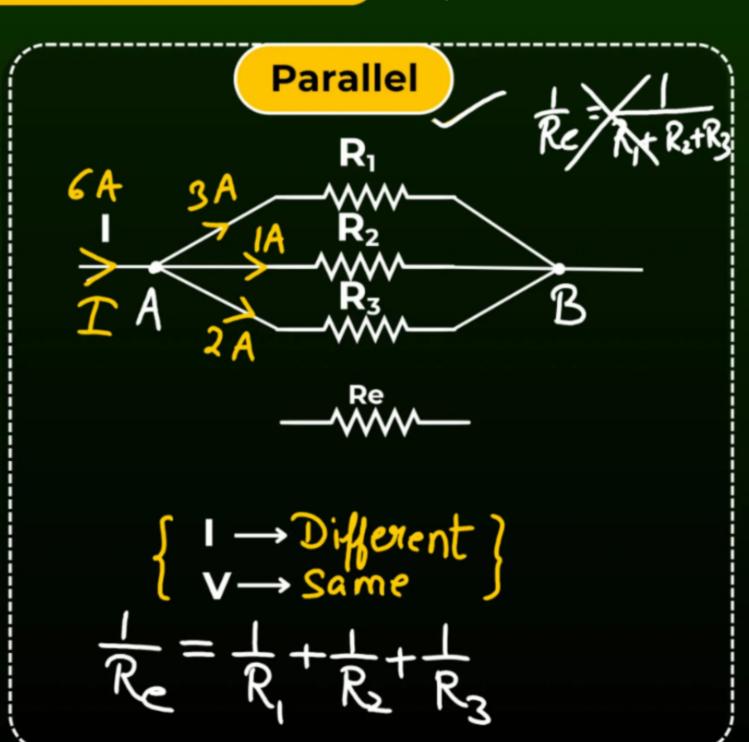
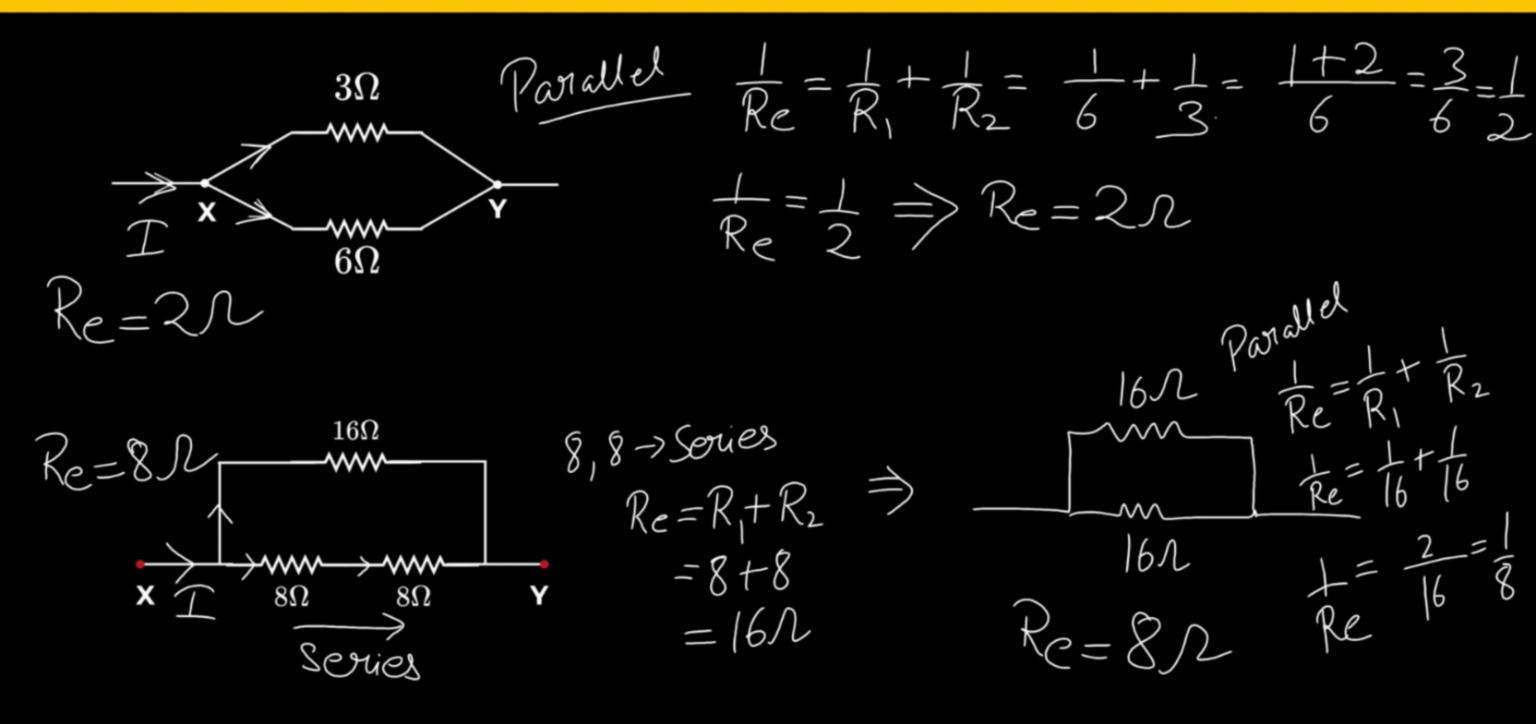
#### 14. Find the equivalent resistance between X and Y.



Re=6
$$\Omega$$


X

 $A\Omega$ 
 $A\Omega$ 

$$f_{Re} = f_{12} + f_{12} = \frac{1+3}{12} = f_{12} = f_{13}$$


$$Re = 3$$



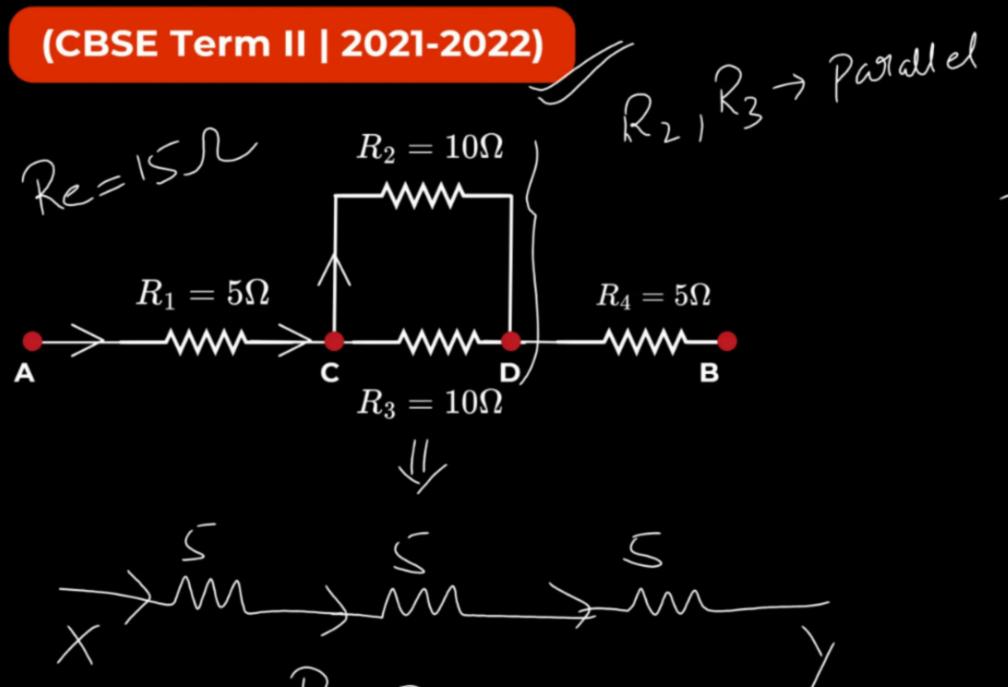

$$\frac{1}{Re} = \frac{1}{10} + \frac{2}{10} = \frac{1}{5}$$
 $\frac{1}{Re} = \frac{1}{5}$ 
 $\frac{1}{Re} = \frac{1}{5}$ 

## 15. Determine the equivalent resistance of the combination between its two ends A and B.

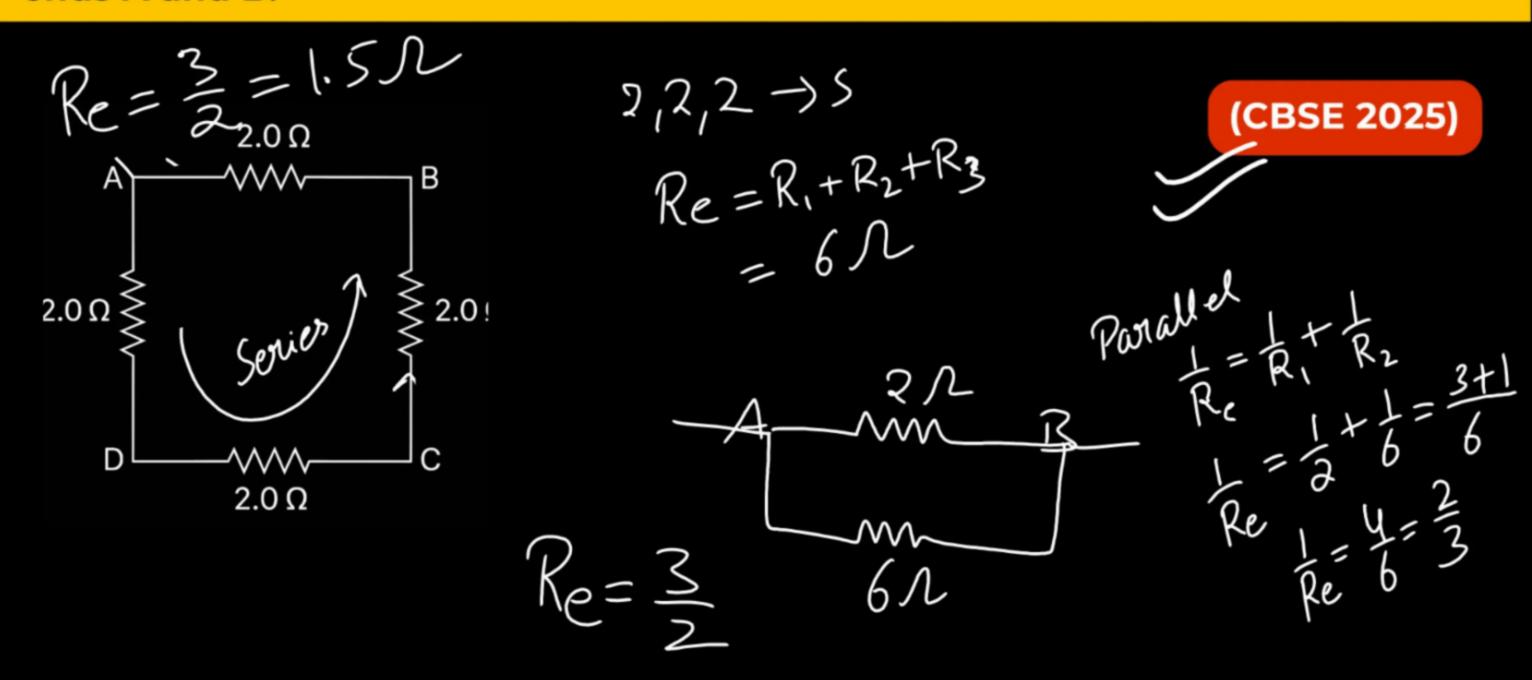


(CBSE 2020) / A > B ey Res

$$6,4 \rightarrow S$$
  $Re = 4+6 = 10 \Omega$ 
 $3,3 \rightarrow S$   $Re = 3+3 = 6 \Omega$ 


Imp Note -> 1) 
$$R_p < R_s$$

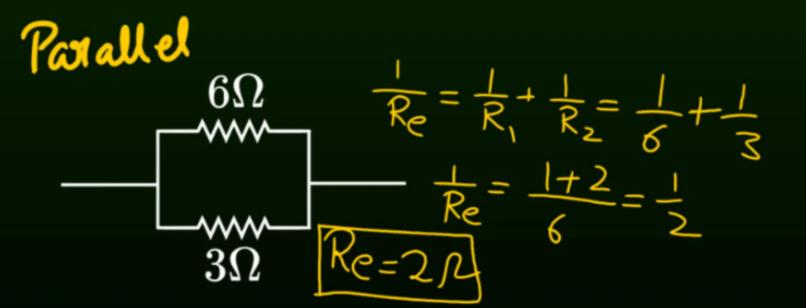-ww-ww- 
$$Re = R_1 + R_2 = 6 + 3 = 9$$
  
 $6\Omega$   $3\Omega$   $Re = 9\Lambda$   
Series



Max Resistance -> Series
Min Resistance -> Parallel

#### Imp Note -> 2)

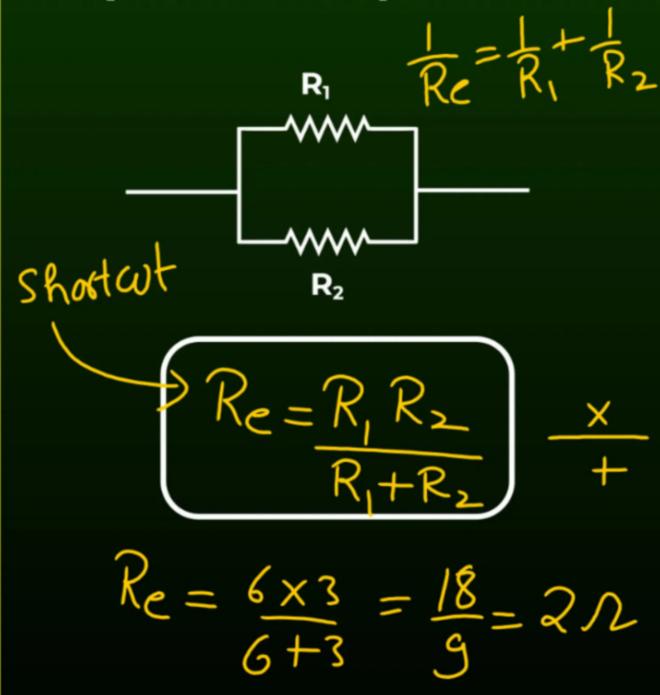

# 16. The maximum & minimum resistance which can be made using four resistors each of 4 $\Omega$ is


Min (CBSE 2025, 2023, 2020)

Win Series

Win Re 
$$\frac{1}{4}$$
  $\frac{1}{4}$   $\frac{1}{4$ 

Imp Note -> 3)
Shoctart

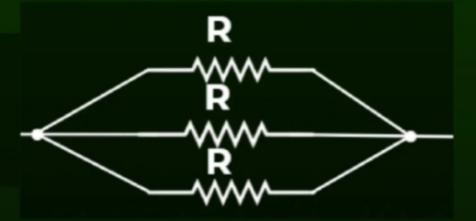
R R R 
$$\rightarrow$$
 W  $\rightarrow$  W  $\rightarrow$  R  $\rightarrow$  R



17. If four identical resistors, of resistance 8 ohm, are first connected in series so as to give an effective resistance  $R_{\rm s}$ , and then connected in parallel so as to give an effective resistance  $R_{\rm p}$ , then the ratio  $R_{\rm s}/R_{\rm p}$  is



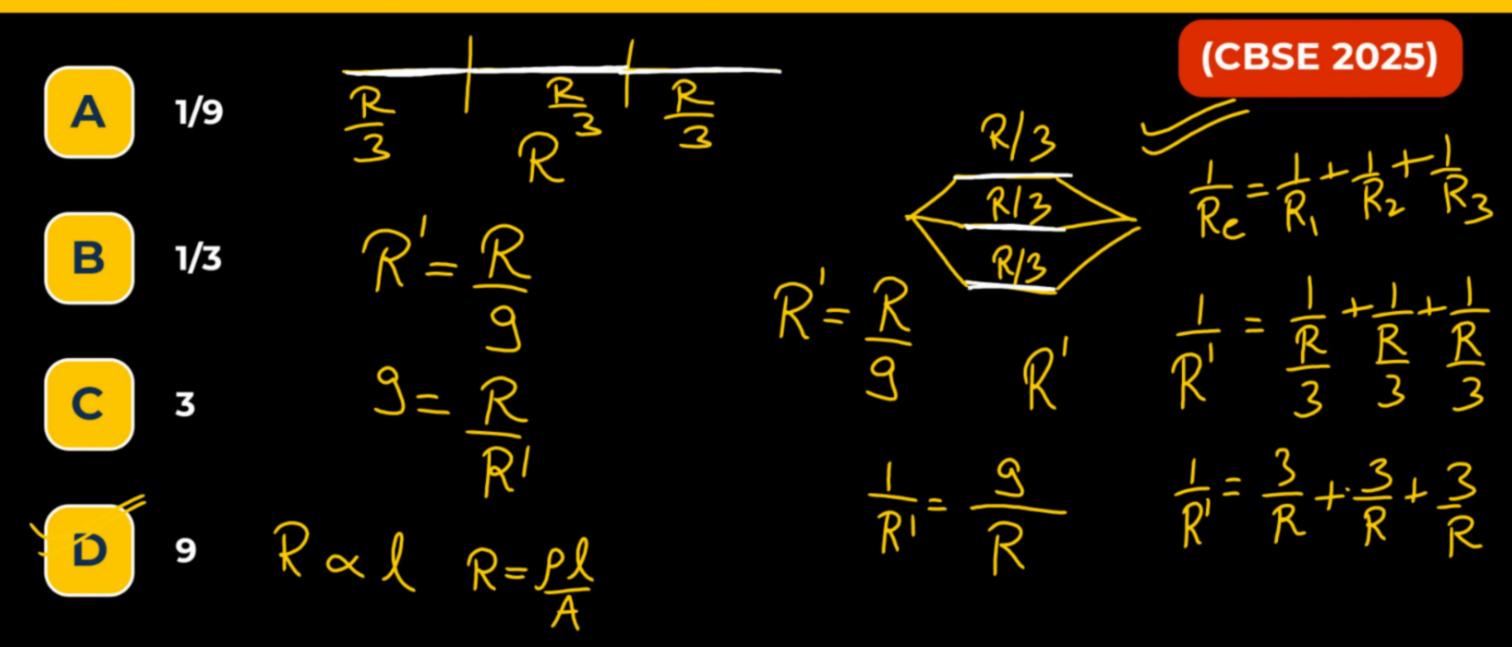18. A piece of wire of resistance 'R' is cut lengthwise into three identical parts. These parts are then connected in parallel. If the equivalent resistance of this combination is R', then the value of R/R' is:



# 19. How you would connect three resistors each of resistance $4\Omega$ , so that the combination has a resistance of $6\Omega$ .

Series 
$$R_e = 4+4+4=12 \Omega$$
  
Parallel  $R_e = \frac{4}{3} = 1.33 \Omega$ 

Mixing 
$$\rightarrow$$
 2p+1s or 2s+1p


4

Y

Tree=4+4=4=1

Re=2+4=6 $\Lambda$ 

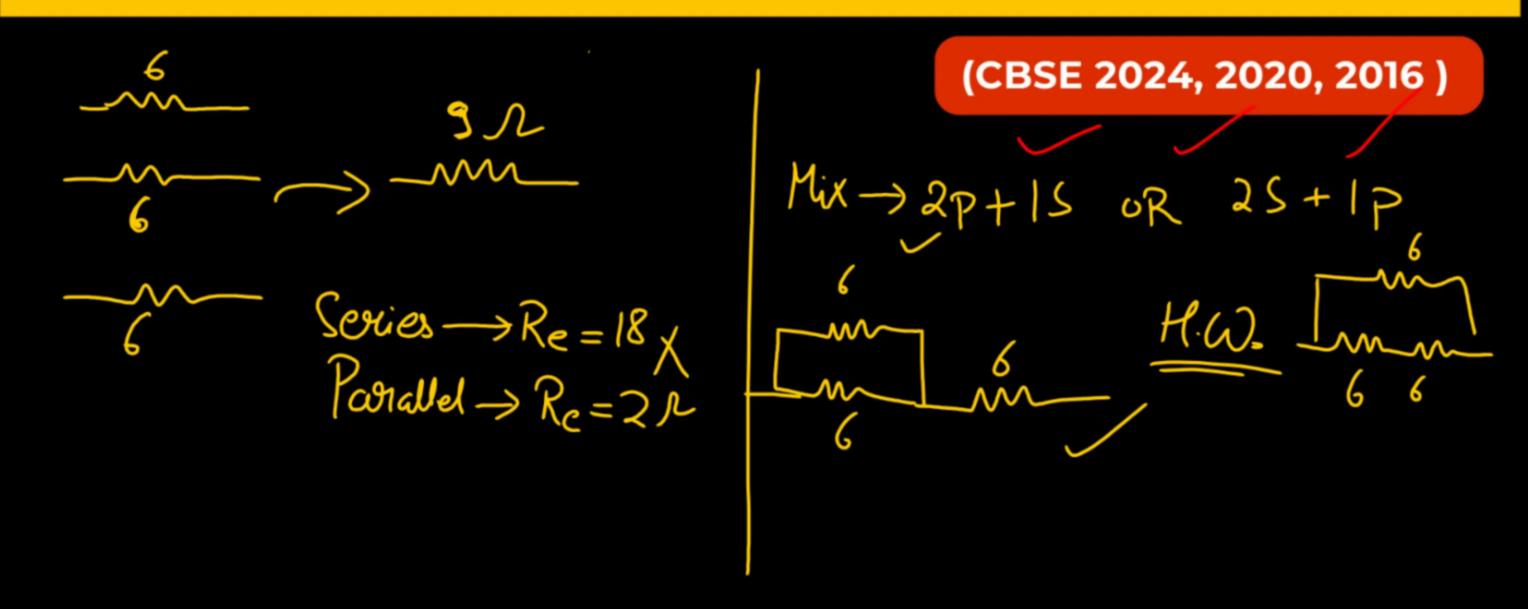20. Show how you would connect three resistors each of resistance  $6\Omega$ , so that the combination has a resistance of  $9\Omega$ . Also justify your answer.



21. Three  $2\Omega$  resistors A, B and C are connected in such a way that the total resistance of the combination is  $3\Omega$ . Show the arrangement of the three resistors and justify your answer.





HOMEWORK, COMMENT THE ANSWER

**CBSE Term II (2021-2022)** 

Correct


Rs -> Series Rp -> Parallel.

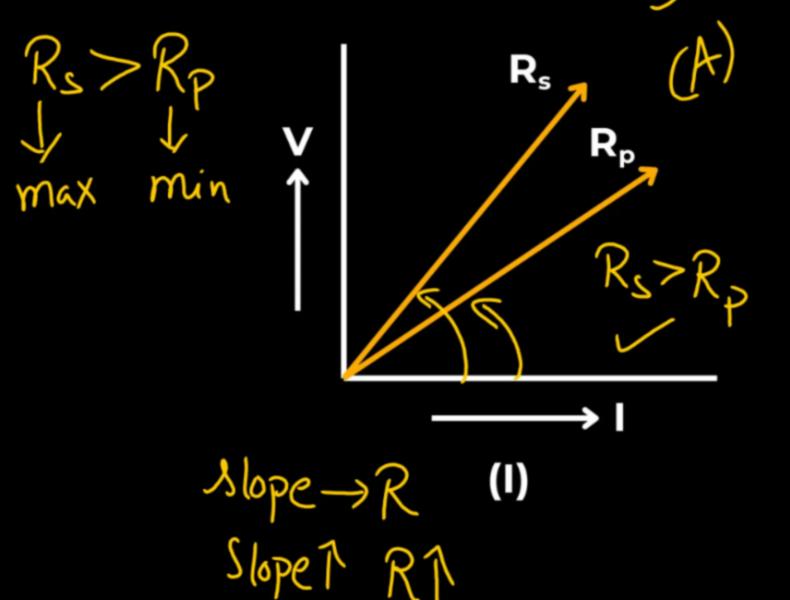

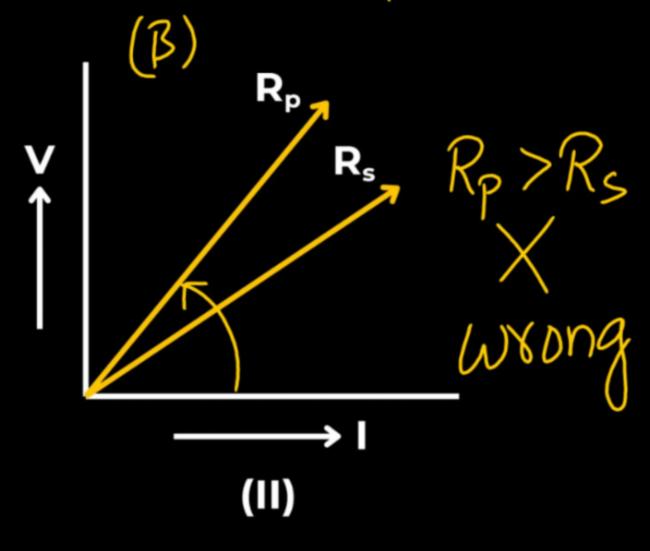
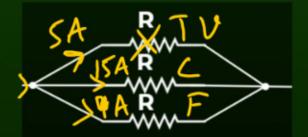
#### **Advantages of Parallel Over Series Combination**





#### 1. Independence of Appliances:

- If one appliance fails or there is a short circuit in one branch of the circuit, the other appliances continue to operate normally. This is because each appliance is on a separate branch of the circuit, ensuring that a fault in one does not affect the others.
- **2) Devices of different types need different current**, for example a Bulb & a Heater needs different current & can not be connected in series.

  This can be done with Parallel Combination.

#### 3. Reduced Equivalent Resistance:

- The equivalent resistance of a parallel circuit is less than the smallest resistance of any of the branches. This reduced resistance allows for a higher total current to flow through the circuit while maintaining the same voltage, which can lead to more efficient energy consumption.
- 22. Which type of circuits series or parallel should be used when you have to operate different electrical gadgets in your house?

  (CBSE 2024,CBSE 2020)

### **Circuit Diagram**



### **CIRCUIT** - Continuous & closed path of electric current.

S.No.	Components	Symbols
1	An electric cell	
2	A battery or a combination of cells	— <del>+</del>
3	Plug key or switch (open)	— OFF
4	Plug key or switch (closed)	— <b>(•)</b> — <i>○N</i>
5	A wire joint	
6	Wires crossing without joining	$\rightarrow$

S.No.	Components	Symbols
7	Electric bulb	
8	A resistor of resistance R	
9	Variable resistance or Rheostat	_^\^*\^_ or\\_
10	Ammeter	
11	Voltmeter /	


23. What do the symbols given below represent in an electric circuit? Write one function of each.








Req

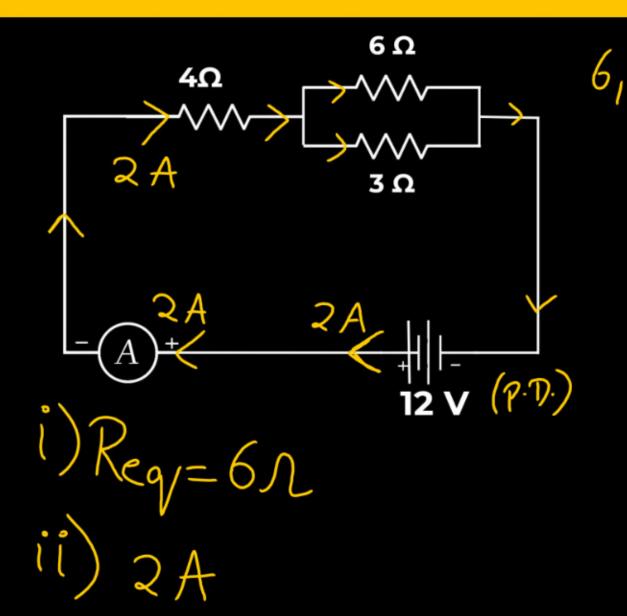


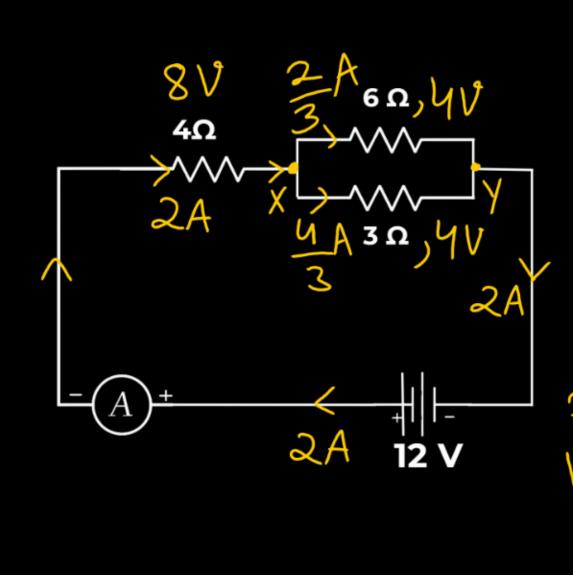


(heck

### 25. Calculate the values of the following:

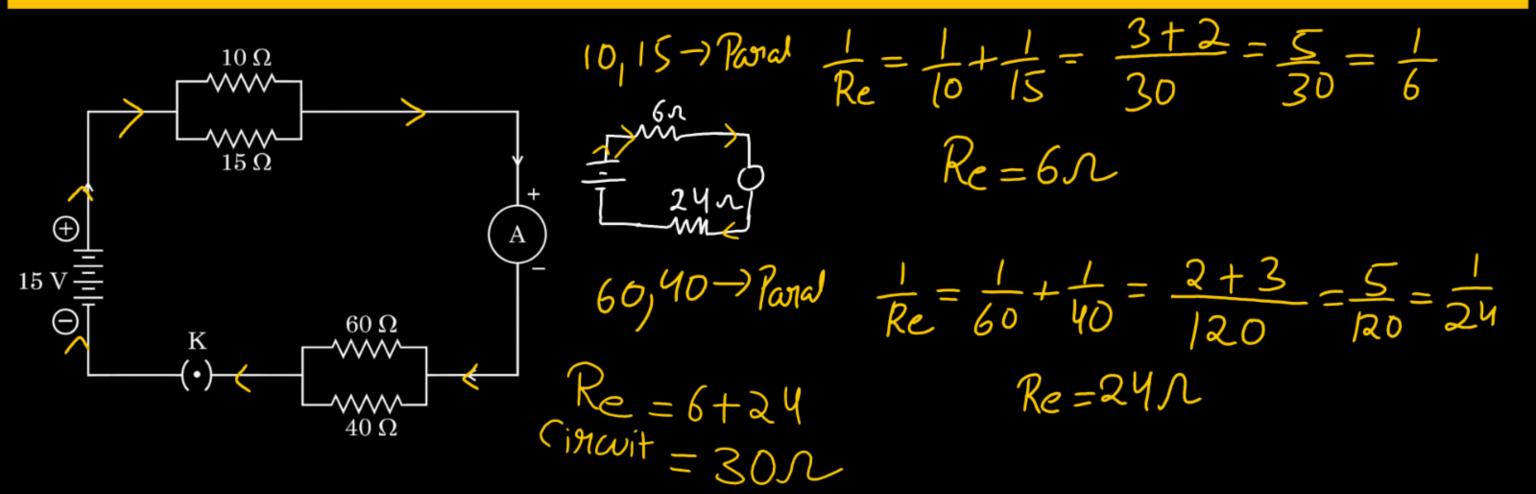
- (a) The total resistance of the circuit  $\Rightarrow 300$
- (CBSE 2025)
- (b) The total current drawn from the source O.SA
- (c) Potential difference across the parallel combination of 10  $\Omega$  and 15  $\Omega$  resistors  $\Rightarrow$   $2\sqrt{}$



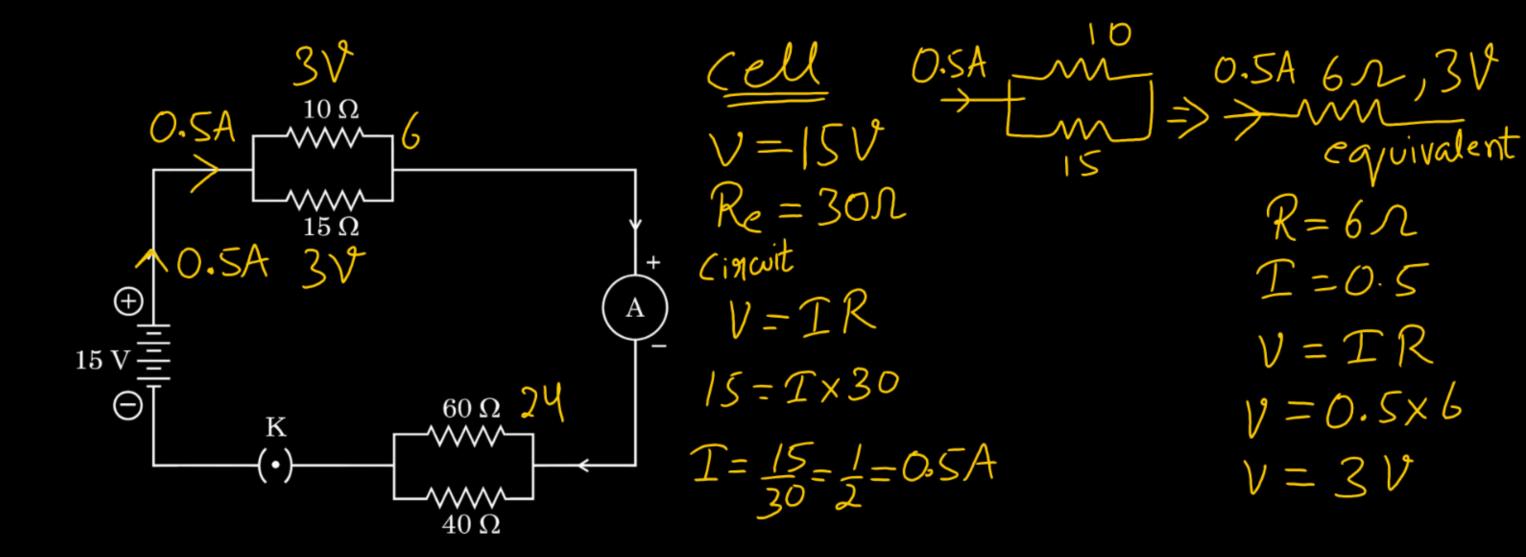

26. Draw a schematic diagram of a circuit consisting of a battery of four 1.5 V cells, a 5  $\Omega$  resistor, a 10  $\Omega$  resistor and a 15  $\Omega$  resistor and a plug key, all connected in series. Now find

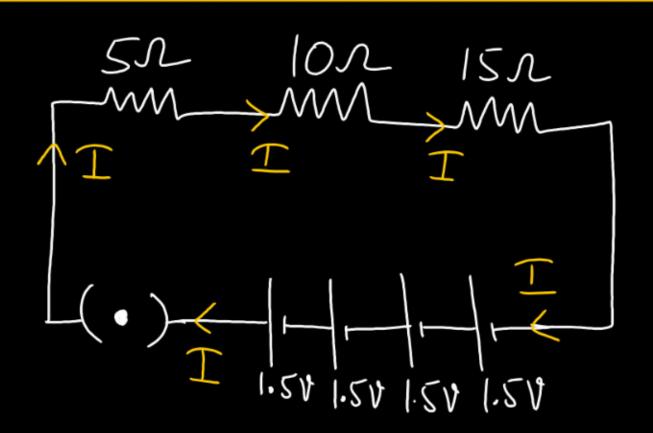(ii) Potential difference across the 10  $\Omega$  resistor when the plug key is closed. 2 \7



Cell
$$V = 1.5 + \dots$$

$$V = TR$$

$$V = 6V$$

$$V = 6V$$

$$V = 6 = 1 \times 30$$

$$V = 8 = 300$$

$$V = 6 = 300$$

$$V = 6$$

(CBSE 2024) = 30N

 $\begin{array}{c}
|OX| \\
|OX| \\
R = 10X \\
T = 0.2A \\
V = TR \\
= 0.2 \times 10 \\
= 2V
\end{array}$ 

### Electric Power (P)



### Rate at which Electric energy is consumed

$$P = I^2 R$$

$$P = rac{V^2}{R}$$

$$V = TR$$

P = Power , S.I Unit - Watt (W)/


V = Potential difference (Volt)

I = Current (Ampere)

28. Define electric power. Express it in terms of potential difference (V) and resistance (R).

(CBSE 2025, 2024)
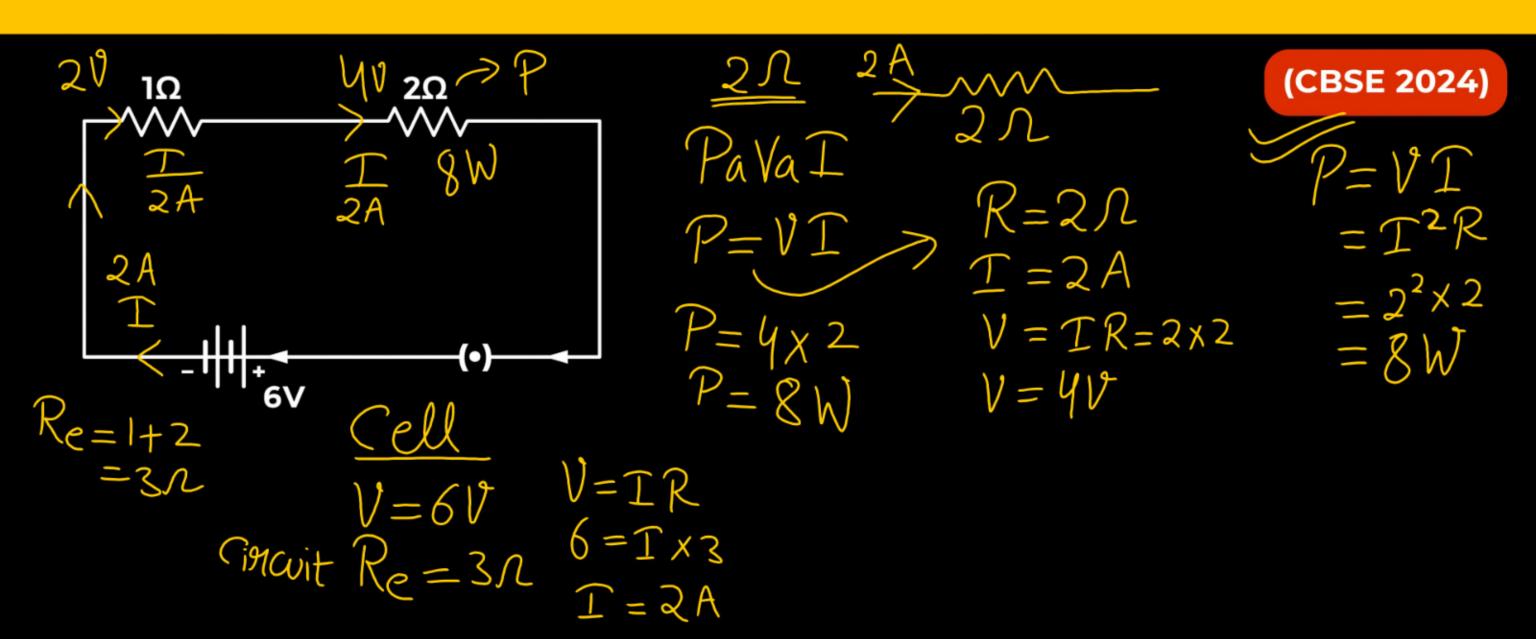
## 29. In the given circuit calculate the power consumed in watts in the resistor of $2\Omega$ .



### 30. An electric heater rated 1100W operates at 220V. Calculate (i) its resistance, and (ii) the current drawn by it.

Power Rating
$$P = 1100W$$

$$V = 220V$$

$$R = ?$$

$$T = 2$$

$$P = V T$$

$$||0\phi| = 22 \phi \times T$$

$$T = 40 10 = 5A$$

$$||2021-2022||$$

$$||200| = 5 \times R$$

V=IR 220=5xR 31. Consider two lamps A and B of rating 50 W; 220 V and 25 W; 220 V respectively. Find the ratio of the resistances of the two lamps (i.e.  $R_A$ :  $R_B$ ).

Rating
$$P = 50W$$

$$V = 220V$$

$$R = 7$$

$$R_A = \frac{V^2}{P} = \frac{(220)^2}{50}$$

$$R_{B} = \frac{(220)^{2}}{25}$$

$$T = \frac{1}{2}$$

$$T = \frac{1}{2}$$

$$RA = \frac{(220)^{2}}{1220}$$

$$= \frac{1}{2}$$

$$= \frac{25}{50}$$

$$= \frac{25}{50}$$

(CBSE 2025)
$$P = V I$$

$$P = V^{2}$$

$$R = V^{2}$$

32. An electric iron consumes energy at a rate of 880W when heating is at the maximum rate and 330W when the heating is at the minimum. If the source voltage is 220V, calculate the current and resistance in each case.

(omment maximum rate

$$P = 880W$$
 $V = 220V$ 
 $T = ?$ 
 $R = ?$ 

#### minimum rate

$$P = 330W$$
 $V = 220V$ 



33. Two LED bulbs of 10W and 5W are connected in series. If the current flowing through 5W bulb is 0.005A, the current flowing through 10W bub is:



(CBSE 2023, 2020)

B 001 A

O.005 A

0.0025 A

### Electrical Energy (E)



Energy = Po T

Electric energy --> Supplied by cell

$$E = P \times t$$

Wh

Watt

1 KWh =  $3.6 \times 10^6$  joule



Electric Meter → 1 Unit of Energy

1 Unit = 1 kWh

Bill = No. of units × Price of Unit




**Energy in kWh** 

- 34. For a heater, rated 4 kW and 220 V, calculate the following:
- (a) Energy consumed in 2 hours
- (b) If 1 kWh is prices at ₹4.50, then the cost of energy consumed.

(CBSE Term II | 2021-2022)

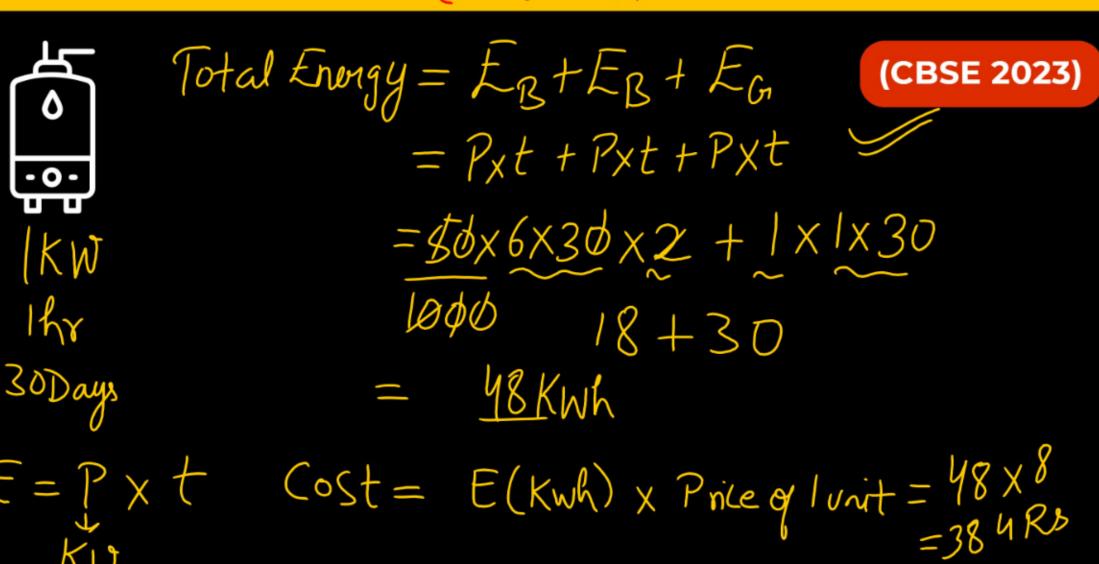35. In a house, 2 bulbs of 50 W each are used for 6 hours daily and an electric geyser of 1 kW is used for 1 hour daily. Calculate the total energy consumed in a month of 30 days and its cost at the rate of ₹8.00 per kWh.





- 36. The rated voltage of an air-conditioner is 220 V. This airconditioner consumes 22 units of electric energy in 10 hours, calculate:
  - (i) Power rating of the air-conditioner,
  - (ii) Current drawn by the air-conditioner, and
  - (iii) Resistance of the air-conditioner

# His Cond V=220V E = 22 unitst = 10hx

$$E = P_{X} + \frac{10h}{22KWh} = P_{X} + \frac{10h}{10}$$

$$P = \frac{22}{10} = 2.2KW$$

$$V = TR$$

$$220 = 10 \times R$$

$$R = 22 \Omega$$

### **Heating Effect of Electric Current**

When an electric current passes through a conductor or an electric device, the conductor becomes hot after some time and produces heat. This is called heating effect of Electric Current.

### Joule's Law of Heating


Heat (H) produces in a Pure resistor

$$1.H \propto I^2$$

$$2.H \propto R$$

$$3.H \propto t$$

Heat (H) is measured in Joules

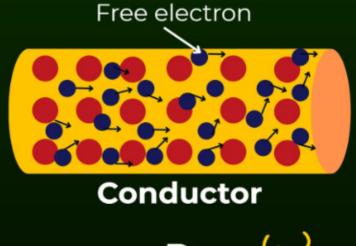

37. What is heating effect of electric current? Find an expression for the amount of heat produced when a current passes through a resistor for some tim (CBSE 2023 CBSE 2024)

A 5  $\Omega$  resistor is connected across a battery of 6 Volts. Calculate the energy that dissipates as heat in 10 s.

$$R = 51$$
  
 $V = 60$   
 $V = 10$ 

$$H = i^{2}Rt$$

$$= 6^{2}x 5 \times 10^{2}$$

$$= 36 \times 4 \times 10^{2}$$

$$= 725$$

(CBSE 2024, 2022, 2021)

### **Practical Application of Heating Effect of Electric Current**







#### Material used for making Heating Devices

Alloys: High Resistivity than metals

High melting point

(CBSE 2025, CBSE 2023)

### **Electric Bulb**

Filament-> Tungsten
Filament is heated & it emits light.
Tungsten has very high Melting point



Most of Energy consumed appears as heat, only small part as light Based on Heating Effect Of Current

### **Electric Fuse - Safety Device**



### **Based on Heating Effect Of Current**

Electrical fuse is used to prevent short circuit. Fuse has low melting point so when high current passes through, it melts due to Heat Produced given by Joule's Law (H =  $\frac{12}{12}$  and stop the flow of current.

Fuse wire is connected in series with the appliance



Fuse wire - Alloy of Al, cu, lead, Iron

Fuse wire hould have:

High resistivity and low melting point

#### Rating of Fuse Wire - Max Current

If high current flows (more than required)
Fuse wire gets heated & melts

Rating of Fuse - 1A, 2A, 3A, 4A, 5A, 10A, etc.

39. State Joule's law of heating. How is this effect useful in electric circuits where fuse is used as a safety device?

(CBSE 2024)

### Q) Current Rating of Fuse Wine FUSE Appliance X A) 4.5A V=220V B) 6 A P = 1100W c) 5.2 A P=VT D) 6.5A 1100 = 220x I $T = 110 \frac{10}{22} = 5A$

Define S.I unit Of Current 1 Ampere

$$Q = Tt \qquad T = 0 \rightarrow 10$$

$$4 \rightarrow 10$$

$$1A$$

If one coulomb of charge flows through a conductor in one second, the current flowing through the conductor is known as one ampere.

Define S.I unit Of Potential Difference 1 Volt

The potential difference between two points is said to be 1 volt if 1 Joule of work is done in moving a positive charge of 1 Coulomb from one point to the other.

**Define S.I unit Of Resistance 1 Ohm** 

$$IS = \frac{V \rightarrow IV}{T \rightarrow IA}$$

One ohm is defined as that resistance of an object when a current of 1 Ampere flows through an object on applying Potential difference of 1V.

**Define S.I unit Of Power 1 Watt** 

1 Watt is the Power Consumed in a circuit when 1 Ampere of Current Flows on applying a Potential difference 1 Volt.