

ELECTRONICS AND COMMUNICATION ENGINEERING

EXAM HELD ON

11th FEBRUARY 2024

MORNING SESSION

DETAILED SOLUTION BY TEAM



FOLLOW US:



MOBILE APP



YOUTUBE



TWITTER



FACEBOOK



TELEGRAM

[MCQ]

Q.1. P, Q, R, S and T have launched a new startup. Two of them are sibling. The office of the startup has just three rooms All of them agree that the sibling should not share the same room. If S and Q are single children and the room allocations shown below are acceptable.



Then which one of the given options is the sibling

- | | |
|-------------|-------------|
| (a) T and Q | (b) T and S |
| (c) T and R | (d) P and T |

Sol. (d)


Since S and Q are single children

RT is grouped together so there are not sibling.

Hence P and T are sibling.

[MCQ]

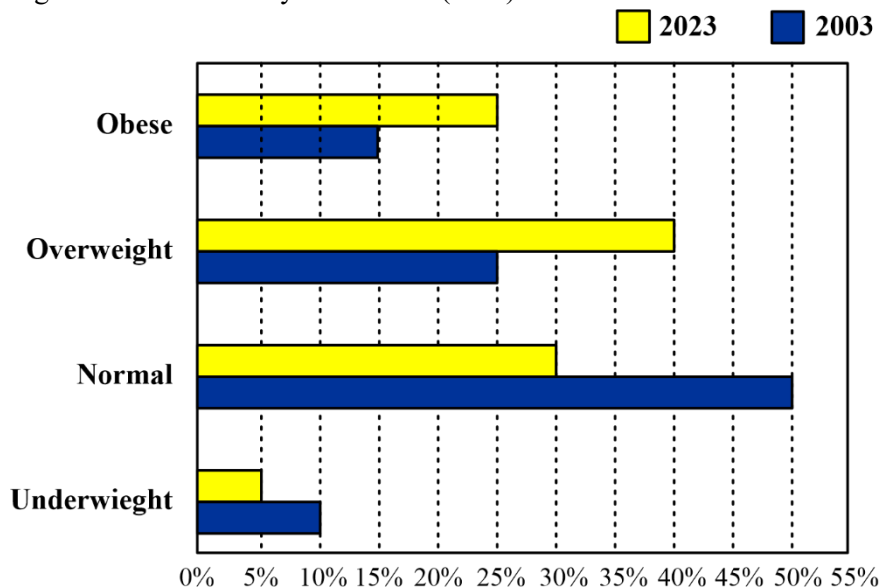Q.2. The bar chart shows the data for the percentage of population falling into different categories based on. Body mass index (BMI) in 2003 and 2023.



Based on the data provided which one of the following options is CORRECT?

- (a) The ratio of the percentage of population falling into overweight category to the percentage of population falling into normal category has increased in 20 years
- (b) The ratio of the percentage of population falling into obese category to the percentage of population falling into normal category has decreased in 20 years
- (c) The [percentage of population falling into normal category has decreased in 20 years
- (d) The ratio of the percentage of population falling into underweight category to the percentage of population falling into normal category has decreased in 20 years

Sol. (b)

The percentage of population falling into obese category in 2003 is 15%

The percentage of population falling into obese category in 2023 is 25%

Percentage of population falling into normal category in 2003 is 50%

Percentage of population falling into normal category in 2023 is 30%

The ratio of the percentage of population falling into obese category to the percentage of population falling into normal category has decreased in 20 years

[MCQ]

Q.3. Five years ago the ratio of Aman age to his father's age was 1:4 and five years from now, the ratio will be 2:5 what was his father's age when Aman was born?

(a) 35 years

(b) 32 years

(c) 30 years

(d) 28 years

Sol. (c)

$$A = x + 5$$

$$\text{After } A = x + 10$$

$$F = 4x + 5$$

$$F = 4x + 10$$

$$\frac{x+10}{4x+10} = \frac{2}{5}$$

$$5x + 50 = 8x + 20$$

$$5x = 30$$

$$x = 10$$

$$45 - 15 = 30$$

[MCQ]

Q.4. For a real number $x > 1$

$$\frac{1}{\log_2 x} = \frac{1}{\log_3 x} = \frac{1}{\log_4 x} = 1$$

The value of x is

(a) 4

(b) 12

(c) 36

(d) 24

Sol. (d)


$$\log_x 2 + \log_x 3 + \log_x 4 = 1$$

$$= \log_x 24 = 1$$

$$x = 24$$

[MCQ]

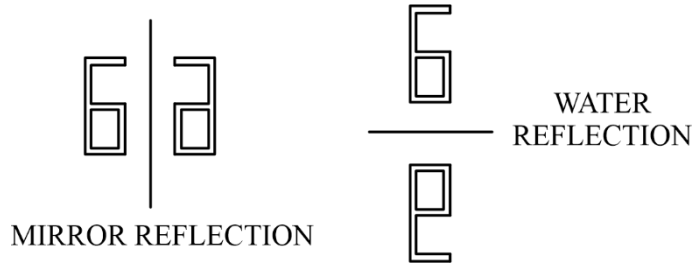- Q.7.** Examples of mirror and water reflections are shown in the figures below
An object appears as the following image after first reflecting in a mirror and then reflecting on water 5.24



Sol. ()

5.24

Reflecting on mirror image

5.24 | 4.25

Reflecting on water

4.25

5.24

[MSQ]

- Q.8.** For a causal discrete – time LTI system with transfer function $H(z) = \frac{2z^2 + 3}{\left(z + \frac{1}{3}\right)\left(z - \frac{1}{3}\right)}$

Which of the following statements is/are true?

- (a) The system is a minimum phase system
- (b) The system is stable
- (c) The initial value of the impulse response is 2
- (d) The final value of the impulse response is 0.

Sol. (b,c,d)

Since the system has a pole at $+1/3$, the system is not a minimum phase system

Since both the poles lies inside unit circle the system stable

Sol. (a)

Bode plot $\Rightarrow 40 \text{ dB/decad}$

$\Rightarrow \text{in dB/octave}$

$20 n \text{ dB/dec} = 6n \text{ dB/oct}$

$40 \text{ dB/dec} = 12 \text{ dB/oct}$

[MCQ]

Q.11. The general form of the complementary function of a differential equation is given by $y(t) = (At + B)e^{-2t}$, where A and B are real constants determined by the initial condition. The corresponding differential equation is _____.

(a) $\frac{d^2y}{dt^2} + 4\frac{dy}{dt} + 4y = f(t)$

(b) $\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = f(t)$

(c) $\frac{d^2y}{dt^2} + 4y = f(t)$

(d) $\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + 6y = f(t)$

Sol. (a)

$y(t) = (At + B)e^{-2t}$ complementary function

Taking Laplace transform of equation $\Rightarrow Y(s) = \frac{A}{(s+2)^2} + \frac{B}{(s+2)}$

Form option (a)

$y'' + 4y' + 4y = f(t)$

Taking Laplace transform

$\Rightarrow s^2Y(s) + 4sY(s) + 4Y(s) = F(s)$

$Y(s) = \frac{F(s)}{(s+2)^2}$

[MCQ]

Q.12. For the Boolean function $F(A, B, C, D) = \sum M(0, 2, 5, 7, 8, 10, 12, 13, 14, 15)$ The essential prime implicants are _____

(a) BD, AB

(b) AB, \overline{BD}

(c) BD, \overline{BD}

(d) BD, \overline{BD}, AB

Sol. (c)

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$	
$\overline{A}\overline{B}$	1 0	1	3	1 2	$\overline{B}\overline{D}, BD$
$\overline{A}B$	4	1 5	1 7	6	
AB	1 12	1 13	1 15	1 14	
$A\overline{B}$	1 8	9	11	1 10	

Essential prime implicants are BD, \overline{BD}

[NAT]

Q.13. A source transmits symbols from an alphabet of size 16. The achievable entropy (in bits) is _____.

Sol. (4)


There are 16 symbols, and for maximum entropy the symbols should be equiprobable

$$P = \frac{1}{16}$$

There for maximum entropy in bits is 4

[MSQ]

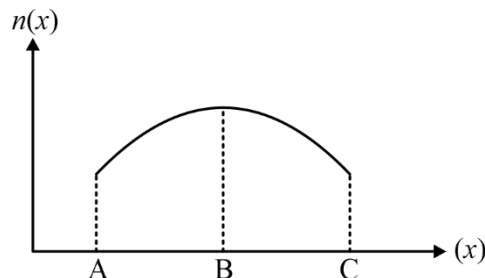Q.14. The free electron concentration profile $n(x)$ in a dope semiconductor at equilibrium is shown in the figure, where the points A , B and C mark three different position. Which of the following statements is/ are true?



- (a) For x between B and C the electric field is directed from B to C .
- (b) For x between B and A , the electric field is directed form A and B .
- (c) For x between B and C , the electron diffusion current is directed form C to B
- (d) For between B and A , the electron drift current is directed from B to A .

Sol. (a,c,d)


[MCQ]

Q.15. A white Gaussian $w(t)$ with zero mean and power spectral density $\frac{N_0}{2}$, when applied to a first- order RC low pass filter produces an output $n(t)$. At a particular time, $t = t_k$, the variance of the random variable $n(t_k)$ is _____.

- | | |
|-----------------------|-----------------------|
| (a) $\frac{N_0}{RC}$ | (b) $\frac{N_0}{4RC}$ |
| (c) $\frac{N_0}{2RC}$ | (d) $\frac{2N_0}{RC}$ |

Sol. (b)
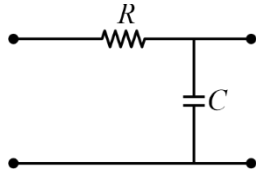
$$PSD = \frac{N_0}{2} \Rightarrow \text{applied to RC filter}$$



$$PSD_o = PSD_i \times |H(\omega)|^2$$

$$H(\omega) = \frac{1}{j\omega RC + 1}$$

$$|H(\omega)|^2 = \frac{1}{1 + \omega^2 R^2 C^2}$$

$$PSD_o = \frac{N_0}{2} \cdot \left(\frac{1}{1 + 4\pi^2 R^2 C^2 f^2} \right)$$

$$\text{Power of output} = \int_{-\infty}^{\infty} \frac{N_0}{2} \frac{1}{1 + 4\pi^2 f^2 R^2 C^2} df$$

$$\Rightarrow \frac{N_0}{2} \cdot \frac{1}{4\pi^2 R^2 C^2} \cdot \int_{-\infty}^{\infty} \frac{1}{\frac{1}{4\pi^2 R^2 C^2} + f^2} df$$

$$\Rightarrow \frac{N_0}{2} \cdot \frac{1}{4\pi^2 R^2 C^2} \cdot 2\pi RC \cdot \pi \Rightarrow \frac{N_0}{4RC}$$

[NAT]

Q.16. An amplitude modulator has output (in Volts)

$S(t) = A \cos(400\pi t) + B \cos(360\pi t) + B \cos(440\pi t)$ The carrier power normalized to 1Ω resistance is 50 Watts. The sideband power to the total power is $1/9$. The value of B in Volts (upto two decimal places) is _____.

Sol. (2.5)

$$S(t) = A \cos(400\pi t) + B \cos(360\pi t) + B \cos(440\pi t)$$

$$\text{Carrier power } P_C = A^2/2$$

$$\text{Side band power } P_{SB} = \frac{B^2}{2} + \frac{B^2}{2} = B^2$$

$$P_C = 50$$

$$A = 10$$

$$\frac{\text{Side band power}}{\text{Total power}} = \frac{1}{9}$$

$$\frac{\frac{B^2}{2}}{\frac{A^2}{2} + B^2} = \frac{1}{9}$$


$$B^2 = \frac{50}{8}$$

$$B = 2.5$$

[NAT]

Q.17. Suppose X and Y are independent and identically distributed random variables distributed uniformly in the interval $[0, 1]$. The probability is _____.


Sol. (0.5)

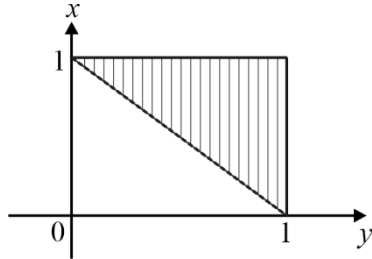

$$\text{Probability} = \iint_R \text{joint PDF} dx dy = \frac{1}{2}$$

[MCQ]

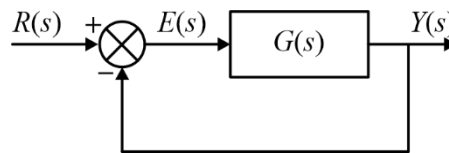Q.18. In the feedback control system shown in the figure below $\frac{6}{s(s+1)(s+2)}$



$R(s)$, $Y(s)$ and $E(s)$ are the Laplace transforms of $r(t)$, $y(t)$ and $e(t)$ respectively. If the input $r(t)$ is a unit step function then _____.

- (a) $\lim_{t \rightarrow \infty} e(t) = \frac{1}{4}$
- (b) $\lim_{t \rightarrow \infty} e(t) = 0$
- (c) $\lim_{t \rightarrow \infty} e(t)$ does not exist, $r(t)$ is oscillatory
- (d) $\lim_{t \rightarrow \infty} e(t) = \frac{1}{3}$

Sol. (b)

$$\frac{E(s)}{R(s)} = \frac{1}{1 + G(s)}$$

$$e(\infty) = \lim_{t \rightarrow \infty} \frac{S \cdot R(s)}{1 + G(s)}$$

$$e(\infty) = \lim_{s \rightarrow 0} \frac{S \cdot \frac{1}{s}}{1 + \frac{6}{s(s+1)(s+2)}} = 0$$

[NAT]

Q.19. In a number system of base r , the equation $x^2 - 12x + 37$ has $x = 8$ one of its solutions. The value of r is _____.

Sol. (11)

At $x = 8$,

$$8^2 - (12)_r (8)_r + (37)_r = 0$$

$$64 - (r + 2)8 + 3r + 7 = 0$$

$$64 - 8r - 16 + 3r + 7 = 0$$


$$5r = 64 - 16 + 7$$

$$5r = 55$$

$$r = 11$$


[NAT]

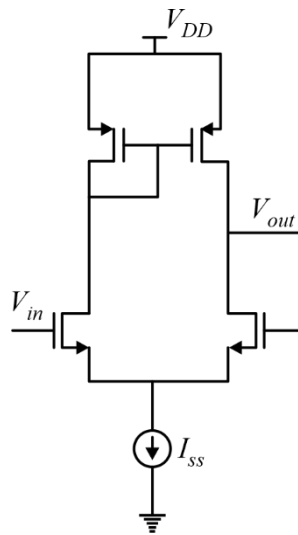Q.20. For the closed loop amplifier circuit shown below. The magnitude of open loop low frequency small signal Voltage gain is 40. All the transistors are biased in saturation. The correct source I_{ss} is ideal. Neglect body effect. Channel length modulation and intrinsic device capacitances. The closed loop low frequency small signal voltage gain (rounded off to three decimal places) is _____.




Sol. (0.975)

Open loop gain $A = 40$

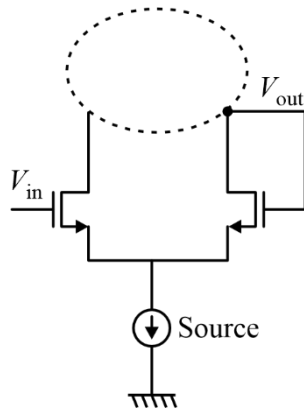

AC analysis of circuit

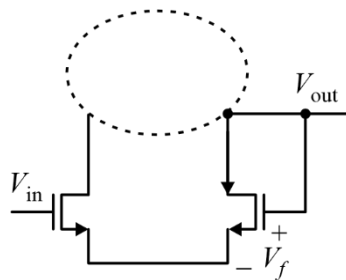

$$\Rightarrow V_f = V_0$$

$$\beta = \frac{V_f}{V_0} = 1$$

Negative feedback

$$\text{Closed loop gain} = \frac{A}{1 + A\beta} = \frac{40}{41}$$

[MSQ]

Q.21. Let $\rho(x, y, z, t)$ and $u(x, y, z, t)$ represent density and velocity respectively at a point (x, y, z) and time t , Assume $\frac{\partial \rho}{\partial t}$ is continuous Let V be an arbitrary volume in space enclosed by the closed surface S and n be the outward unit normal of S Which of the following equations is/are equivalent to $\frac{\partial \rho}{\partial t} + \nabla \cdot (\rho u) = 0$?

- (a) $\int_V \frac{\partial \rho}{\partial t} dv = - \int_V \nabla \cdot (\rho u) dv$ (b) $\int_S \frac{\partial \rho}{\partial t} dv = - \int_S (\rho u) \cdot n ds$
 (c) $\int_V \frac{\partial \rho}{\partial t} dv = - \int_S \rho u \cdot n ds$ (d) $\int_V \frac{\partial \rho}{\partial t} dv = - \int_S \nabla(\rho u) dv$

Sol. (a, c)

$$\frac{\partial \rho}{\partial t} + \nabla \cdot (\rho u) = 0$$

$$\int_V \frac{\partial \rho}{\partial t} dv = - \int_V \nabla \cdot (\rho u) dv$$

$$\int_V \frac{\partial \rho}{\partial t} dv = - \int_S \rho u \cdot n ds$$

[MSQ]

Q.22. Let \hat{i} and \hat{j} be the unit vectors along x and y axes, respectively and let A be a positive constant. Which one of the following statements is true for the fields

$$\vec{F}_1 = A(\hat{i}y + \hat{j}x) \text{ and } \vec{F}_2 = A(\hat{i}y - \hat{j}x)?$$

- (a) Only \vec{F}_2 is an electrostatic field
- (b) Neither \vec{F}_1 nor \vec{F}_2 is an electrostatic field
- (c) only \vec{F}_1 is an electrostatic field
- (d) Both \vec{F}_1 and \vec{F}_2 are electrostatic fields


Sol. (c)

$$\vec{\nabla} \times \vec{F}_1 = \begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ Ay & Ax & 0 \end{vmatrix} = 0$$

$$\vec{\nabla} \times \vec{F}_2 = \begin{vmatrix} \hat{a}_x & \hat{a}_y & \hat{a}_z \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ y & -x & 0 \end{vmatrix} = -2A\hat{a}_z + 0$$

[NAT]

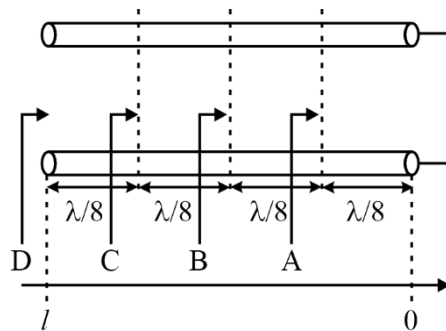Q.23. Consider a lossless transmission line terminated with a short as shown in the figure below, as one moves towards the generator from the load the normalized impedances Z_{inA} , Z_{inB} , Z_{inC} , Z_{inD} is



- (a) $Z_{inA} = j1\Omega$, $Z_{inB} = \infty$, $Z_{inC} = -j1\Omega$, $Z_{inD} = 0$
- (b) $Z_{inA} = j0.4\Omega$, $Z_{inB} = \infty$, $Z_{inC} = -j0.4\Omega$, $Z_{inD} = 0$
- (c) $Z_{inA} = \infty$, $Z_{inB} = j1\Omega$, $Z_{inC} = 0$, $Z_{inD} = -j1\Omega$
- (d) $Z_{inA} = \infty$, $Z_{inB} = j0.4\Omega$, $Z_{inC} = 0$, $Z_{inD} = -j0.4\Omega$

Sol. (a)

$$Z_L = 0$$

$$Z_{in} = jZ_0 \tan \beta l$$

$$\text{At A, } l = \frac{\lambda}{8}, \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{8} = \frac{\pi}{4}$$

$$Z_{in} = jZ_0$$

$$Z_{inA} = j1\Omega$$

$$\text{At B, } l = \frac{2\lambda}{8}, \beta l = \frac{2\pi}{\lambda} \cdot \frac{2\lambda}{8} = \frac{\pi}{2}$$

$$Z_{in} = jZ_0 \tan \frac{\pi}{2}$$

$$Z_{inB} = \infty$$

$$\text{At C, } l = \frac{3\lambda}{8}, \beta l = \frac{2\pi}{\lambda} \cdot \frac{3\lambda}{8} = \frac{3\pi}{4}$$

$$Z_{in} = -jZ_0$$

$$Z_{inC} = -j1\Omega$$

$$\text{At D, } l = \frac{4\lambda}{8}, \beta l = \frac{2\pi}{\lambda} \cdot \frac{4\lambda}{8} = \pi$$


$$Z_{in} = jZ_0 \tan \pi$$

$$Z_{inD} = 0\Omega$$


[MSQ]

Q.24. For non-degenerately doped n-type silicon when one of the following plots represents the temperature (T) dependence of free electron concentration (n)?


(a)

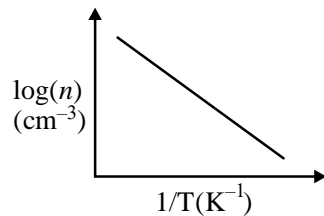

(b)

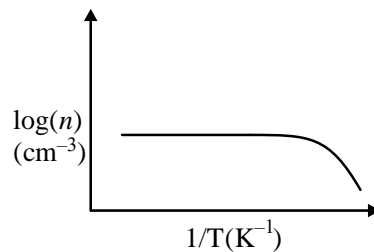


(c)

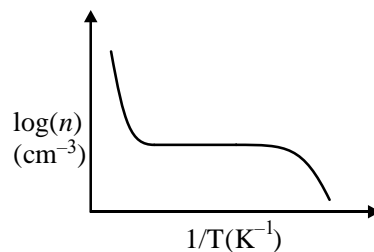


(d) None of these

Sol. (c)

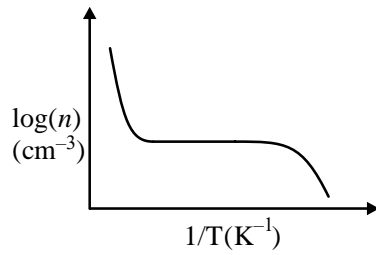

[MSQ]

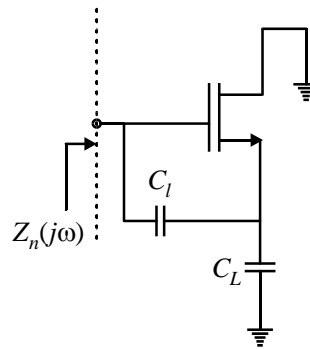Q.25. In the circuit below assume that the long channel NMOS transistor is biased in saturation. The small signal trans conductance of the transistor is g_m . Neglect body effect channel length modulation and intrinsic device capacitances. The small signal input impedance $Z(j\omega)$ is _____.




(a) $\frac{1}{j\omega C_i} + \frac{1}{j\omega C_L}$

(b) $\frac{-g_m}{C_i C_L \omega^2} + \frac{1}{j\omega C_i + j\omega C_L}$

(c) $\frac{-g_m}{C_i C_L \omega^2} + \frac{1}{j\omega C_i} + \frac{1}{j\omega C_L}$

(d) $\frac{g_m}{C_i C_L \omega^2} + \frac{1}{j\omega C_i} + \frac{1}{j\omega C_L}$

Sol. (c)

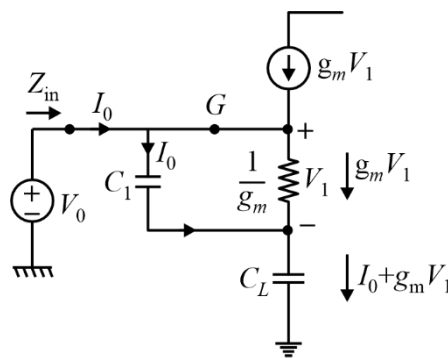

$$V_1 = Z_{C_i} \cdot I_0$$

$$-V_0 + I_0 Z_{C_i} + (I_0 + g_m V_1) Z_{C_L} = 0$$


$$-V_0 + I_0 Z_{C_i} + I_0 Z_{C_L} + g_m Z_{C_i} I_0 Z_{C_L} = 0$$

$$\frac{V_0}{I_0} = (Z_{C_i} + Z_{C_L} + g_m Z_{C_i} Z_{C_L})$$


$$\frac{V_0}{I_0} = \frac{1}{j\omega C_i} + \frac{1}{j\omega C_L} + \frac{g_m}{-\omega^2 C_i C_L}$$

[NAT]

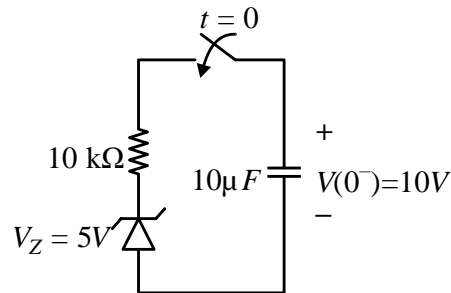- Q.26.** As shown in the circuit the initial voltage across the capacitor is 10 V. with the switch being open. The switch is then closed at $t = 0$. The total energy dissipated in the ideal Zener diode ($V_Z = 5V$) after the switch is closed (in mJ, rounded off to three decimal places) is _____.



Sol. (0.25)

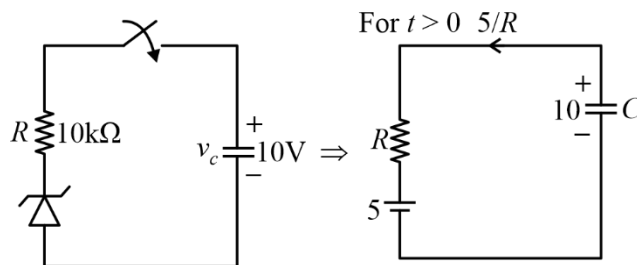

$$\Rightarrow i(t) = \frac{5}{R} e^{-t/RC}$$

$$P(t) = v \times i$$

$$P(t) = 5 \times \frac{5}{R} e^{-t/RC}$$

$$\text{Energy dissipated in Zener} \Rightarrow \int_0^{\infty} \frac{25}{R} e^{-t/RC} dt$$

$$\Rightarrow -\frac{25RC}{R} e^{-t/RC} \Big|_0^{\infty}$$

$$\Rightarrow 25 C$$

$$\text{Energy dissipated} \Rightarrow 25C$$


$$\Rightarrow 25 \times 10 \times 10^{-6}$$

$$\Rightarrow 250 \mu\text{J}$$


$$\Rightarrow 0.250 \text{ Milli Joule}$$

[NAT]

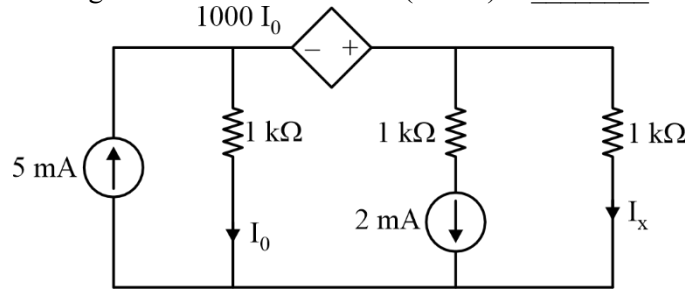Q.27. In the given circuit the current I_x (in mA) is _____



Sol. (2)

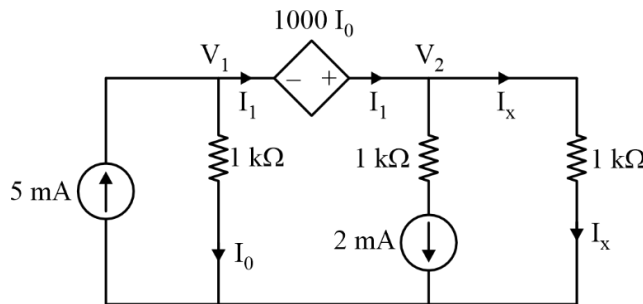

$$\frac{V_1 - 0}{1k} + I_1 = 5 \text{ mA} \Rightarrow V_1 + 1000 I_1 = 5$$

$$V_2 - V_1 = 1000 I_0 = 1000 \left(\frac{V_1}{1k} \right)$$

$$\Rightarrow V_1 = \frac{V_2}{2}$$

$$V_2 + 2 = 1000 I_1$$

$$V_1 + V_2 + 2 = 5$$


$$\frac{V_2}{2} + V_2 = 3 \Rightarrow V_2 = 2 \text{ V}$$

$$\frac{V_2 - 0}{1k} + 2 \text{ mA} = I_1$$


$$I_x = \frac{V_2}{1k} = 2 \text{ mA}$$

[NAT]

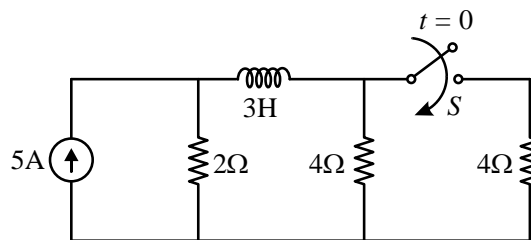Q.27. In the circuit given below the switch S was kept open for sufficiency long time and is closed at time $t = 0$, The time constant (in seconds) of the circuit for $t > 0$ is _____.



Sol. (0.75)

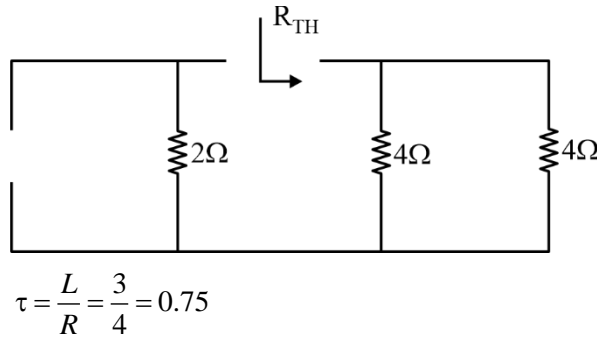

[NAT]

Q.29. Let R and R^2 denote the set of real number and the three-dimensional vector space over respectively. The value of a for which the set of vectors $\{[2 - 3 a], [3 - 1 3], [1 - 5 7]\}$ Does not form a basis of R^3 is _____

Sol. (5)

$\{[2 - 3 a], [3 - 1 3], [1 - 5 7]\}$

To form basis, all vectors should be independent

$$\begin{vmatrix} 2 & -3 & a \\ 3 & -1 & 3 \\ 1 & -5 & 7 \end{vmatrix} = 0$$

$$\Rightarrow 2\{8\} + 3\{18\} + a\{-14\} = 0$$

$$a = 5$$

[MSQ]

Q.30. A causal and stable LTI system with impulse response $h(t)$ produces an output $y(t)$ for an input signal $x(t)$. A signal $x(0.5t)$ is applied to another causal and stable LTI system with impulse response $h(0.5t)$ the resulting output is _____.

(a) $0.25 y(2t)$

(b) $0.25 y(0.25t)$


(c) $2y(0.5y)$

(d) $4y(0.5t)$

Sol. (c)

[MSQ]

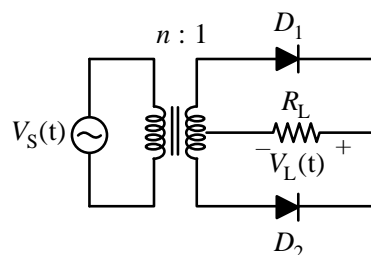Q.31. In the circuit shown the $n : 1$ step down transformer and the diodes are ideal. The diodes have no voltage drop forward condition. If the input Voltage (in Volts) is $V_s(t) = 10 \sin \omega t$ and the average value of load voltage $V_L(t_0)$ (in Volts) is $2.5/\pi$, the value of n is _____



Sol. (4)

$$V_s = 10 \sin \omega t$$

$$V_{\text{induced}} = \frac{10}{n} \sin \omega t$$

$$V_0 = \left| \frac{V_s}{2n} \right|$$

$$V_0 = \left| \frac{5 \sin \omega t}{n} \right|$$


$$V_{0\text{avg}} = \frac{2V_m}{\pi}$$

$$= 2 \times \frac{5}{n} \cdot \frac{1}{\pi} = \frac{10}{n\pi} \Rightarrow \frac{2.5}{\pi}$$

$$n = 4$$

[NAT]

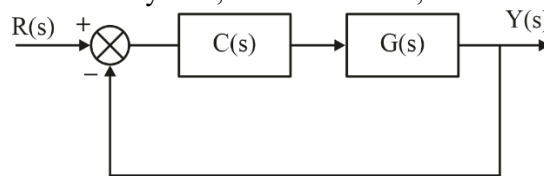Q.32. A satellite altitude control system, as shown below,



has a plant with transfer function $G(s) = \frac{1}{s^2}$ cascaded with a compensator

$$C(s) = \frac{K(s + \alpha)}{(s + 4)} \text{ where } K \text{ and } \alpha \text{ are positive real constant.}$$

In order for closed-loop system to have poles at $-1 + j\sqrt{3}$, the value of α must be _____.

Sol. (1)

$$OLTF = \frac{k(s + \alpha)}{s^2(s + 4)}$$

$$|G(s)|_{s=-1+j\sqrt{3}} = \frac{k(-1 + j\sqrt{3} + \alpha)}{(-1 + j\sqrt{3})^2(-1 + j\sqrt{3} + 4)}$$

$$= \frac{k(\alpha - 1 + j\sqrt{3})}{(-1 + j\sqrt{3})^2(3 + j\sqrt{3})}$$

If s_1 lie on Root Locus

$$\angle G(s) = (2q + 1)180$$

$$\angle G(s) = \tan^{-1} \frac{\sqrt{3}}{\alpha - 1} - \left[2 \tan^{-1} \frac{\sqrt{3}}{-1} - \tan^{-1} \frac{\sqrt{3}}{3} \right] = 180$$

$$= \tan^{-1} \frac{\sqrt{3}}{\alpha - 1} - \left[2(180 \tan^{-1} \sqrt{3}) - \tan^{-1} \frac{1}{\sqrt{3}} \right] = 180$$


$$= \tan^{-1} \frac{\sqrt{3}}{\alpha - 1} - [360 - 120 - 30] = 180$$

$$\tan^{-1} \frac{\sqrt{3}}{(\alpha - 1)} - [210] = 180$$

$$\alpha = 1$$

[MCQ]

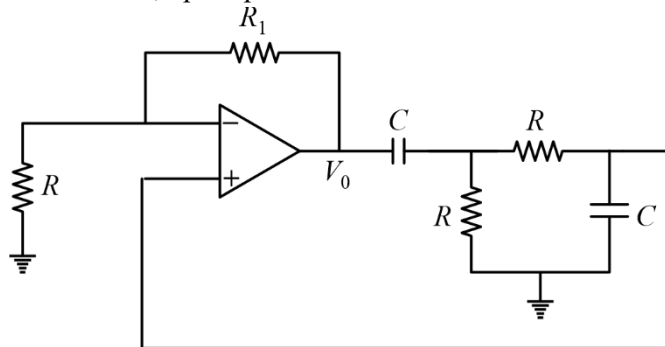Q.33. In circuit shown below, op-amp is ideal.



If the circuit is to show sustained oscillation, the respective value of R_1 and the corresponding frequency of oscillation are _____.

(a) $2R$ and $\frac{1}{(2\pi\sqrt{6}RC)}$


(b) $2R$ and $\frac{1}{(2\pi RC)}$

(c) $29R$ and $\frac{1}{(2\pi RC)}$

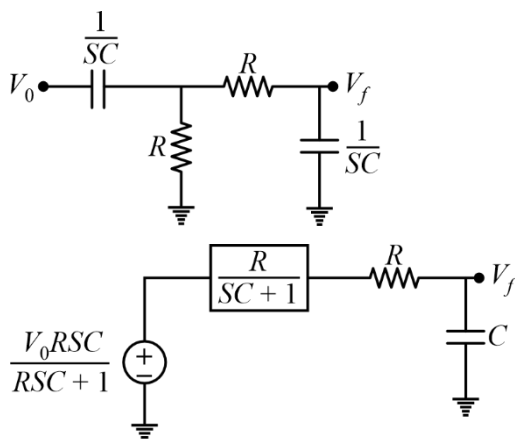(d) $29R$ and $\frac{1}{(2\pi\sqrt{6}RC)}$

Sol. (b)

$$\text{Gain } A = \left(1 + \frac{R_1}{R}\right)$$



$$V_f \Rightarrow \frac{V_0 RSC}{RSC+1} \cdot \frac{1/SC}{\frac{1}{SC} + R + \frac{R}{RSC+1}}$$

$$\beta = \frac{V_f}{V_0} = \frac{RSC}{(RSC+1) \left(RSC+1 + \frac{RSC}{RSC+1} \right)}$$

$$= \frac{RSC}{(RSC+1)^2 + RSC}$$

$$\beta \Rightarrow \frac{RSC}{(RSC)^2 + 3RSC + 1}$$

$$\beta = \frac{j\omega RC}{-\omega^2 R^2 C^2 + 1 + 3j\omega RC}$$

$$1 - \omega^2 R^2 C^2 = 0$$

$$\omega = \frac{1}{RC}$$

$$f = \frac{1}{2\pi RC}$$

$$\beta = \frac{1}{3}$$


So for oscillation $A = 3$

$$3 = 1 + \frac{R_i}{R}$$


$$R_i = 2R$$

[NAT]

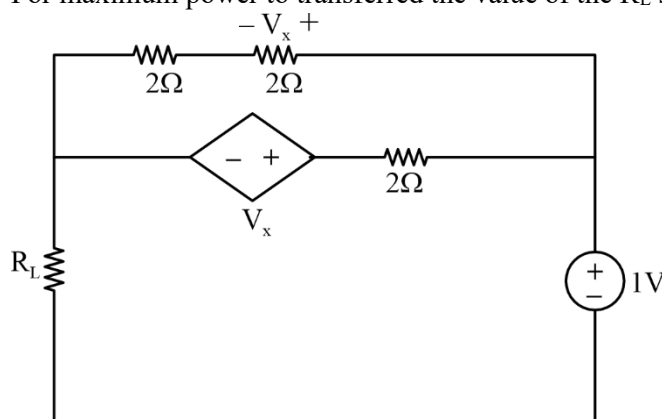Q.34. For maximum power to be transferred the value of the R_L should be



Sol. (2.5)

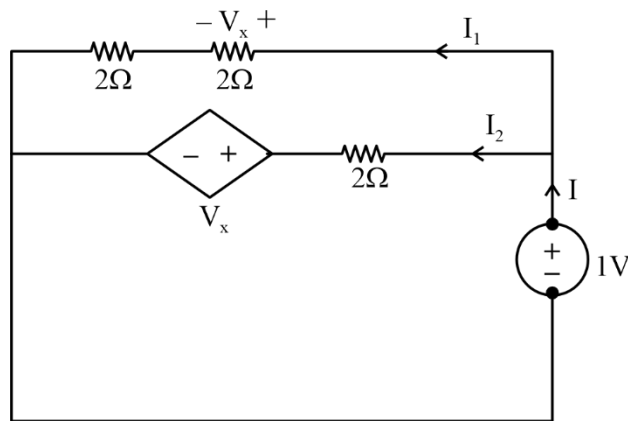

$$\frac{I}{2} = \frac{1 - V_x}{2}$$

$$= \frac{1 - 3/5}{2} = \frac{1}{5}$$

$$V_x = \frac{1}{5} \times 3 = \frac{3}{5}$$

$$R_L = ?$$

$$R_2$$

$$R_{th} = \frac{1}{I}$$

$$I = I_1 + I_2 = 2/5$$

$$R_{th} = \frac{5}{2} = 2.5\Omega$$

[NAT]

Q.35. A transmission line with $Z_0 = 50\Omega$, $|\Gamma| = 0.6$, is terminated with an unknown load. When seen from generator end to load the magnitude of maximum input impedance is.

Sol. (200)


$$Z_0 = 50\Omega, |\Gamma| = 0.6, Z_{\max} = ?$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1.6}{0.4} = 4$$

$$VSWR = \frac{Z_{\max}}{Z_0} = 4 \Rightarrow Z_{\max} = 4Z_0 = 200\Omega$$

[MCQ]

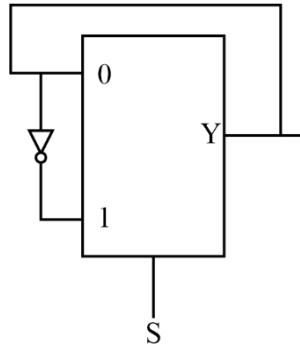Q.36. The propagation delay of the 2×1 MUX shown in the circuit is 10 ns. Consider the propagation delay of the inverter as 0 ns.




If S is set to 1 then output of Y is _____

- (a) Constant at '0'
- (b) Constant at '1'
- (c) A square wave of frequency 100 MHz
- (d) A square wave of frequency 50 MHz

Sol. (d)

At $S = 1$

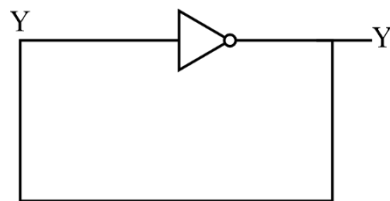

Output Y will be square waveform

$$T = 2 n t_{pd}$$

$$= 2(1) (10\text{ns})$$

$$= 20 \text{ ns}$$

$$f = \frac{1}{T} = 50 \text{ MHz}$$

[MCQ]

Q.37. A digital communication system transmits through a Noiseless band limited channel $[-W, W]$. The received signal $z(t)$ at output of receiving filter is given by $z(t) = \sum_a b(n)x(t - nT)$ where $b(n)$ are the symbols and $x(t)$ is the overall system response to single symbol. The received signal is sampled at $t = mT$ the fourier transform $x(t)$ is $x(f)$, the Nyquist condition that $x(f)$ must satisfy for zero inter symbol interference at the receiver is _____

(a) $\sum_{m=-\infty}^{\infty} X\left(f + \frac{m}{T}\right) = \frac{1}{T}$

(b) $\sum_{m=-\infty}^{\infty} X(f + mT) = \frac{1}{T}$

(c) $\sum_{m=-\infty}^{\infty} X\left(f + \frac{m}{T}\right) = T$

(d) $\sum_{m=-\infty}^{\infty} X(f + mT) = T$

Sol. (c)

Zero ISI

$x(t)$ is pulse

$$\Rightarrow x(t) \cdot \delta(t - nT) = \delta(t)$$


$$\frac{1}{2\pi} \left(X(\omega) * \sum_{n=-\infty}^{\infty} \frac{2\pi}{T} \delta(\omega - n\omega_s) \right) = 1$$

$$\Rightarrow \sum_{n=-\infty}^{\infty} X(\omega - n\omega_s) = T$$

$$\sum_{m=-\infty}^{\infty} X\left(f + \frac{m}{T}\right) = T$$

[MCQ]

Q.38.

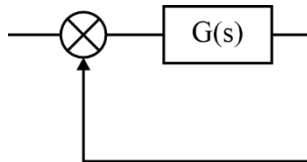


$$G(s) = \frac{k}{(s+1)(s+2)(s+3)}$$

The impulse response of close loop system de faster than e^{-1} if.

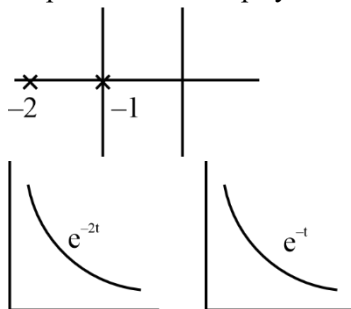- (a) $-24 \leq K \leq -6$
- (b) $-4 \leq K \leq -1$
- (c) $7 \leq K \leq 21$
- (d) $1 \leq K \leq 5$

Sol. (d)

So pole of close loop system should be lie L.H.S of $s = -1$ plane



$$s = (s - 1)$$

$$CE = 1 + (s) = 0$$

$$= 1 + \frac{K}{(s+1)(s+2)(s+3)}$$

$$(s+1)(s+2)(s+3) + K = 0$$

$$\text{Put } s = s - 1$$

$$s(s+1)(s+2) + K = 0$$

$$s(s^2 + 3s + 2) + K = 0$$

$$s^3 + 3s^2 + 2s + K = 0$$

Apply R.H.S

s^3	1	2
s^2	3	K
s	$\frac{6-K}{3}$	0
s^0	K	

$$\frac{6-K}{3} > 0$$

$$K < 6$$

$$K > 0$$

$$0 < K < 6$$

$$1 \leq K \leq 5$$

[MCQ]

Q.39. Which of the following is/are eigen vectors for matrix $\begin{bmatrix} 1 & k \\ 2 & 1 \end{bmatrix}; k \in R^+$

(a) $\begin{bmatrix} -1 \\ \sqrt{\frac{2}{k}} \end{bmatrix}$

(b) $\begin{bmatrix} \sqrt{2k} \\ -1 \end{bmatrix}$

(c) $\begin{bmatrix} \sqrt{2k} \\ 1 \end{bmatrix}$

(d) $\begin{bmatrix} 1 \\ \sqrt{\frac{2}{k}} \end{bmatrix}$

Sol. (a, d)

$$\begin{vmatrix} 1-\lambda & k \\ 2 & 1-\lambda \end{vmatrix} = 0 \Rightarrow (\lambda - 1)^2 = 2k$$

$$\Rightarrow \lambda = 1 \pm \sqrt{2k}$$

$$\begin{bmatrix} -1 \\ \sqrt{\frac{2}{k}} \end{bmatrix}, \begin{bmatrix} 1 \\ \sqrt{\frac{2}{k}} \end{bmatrix}$$

[MCQ]

Q.40. The radian frequency value (s) for which the discrete time sinusoidal signal

$$x(n) = A \cos\left(\Omega n + \frac{\pi}{3}\right) \text{ has a period of 40 is/are } \underline{\hspace{2cm}}.$$

(a) 0.15π

(b) 0.3π

(c) 0.45π

(d) 0.225π

Sol.
(a,b,c)

$$N = 40$$

$$\frac{\Omega}{2\pi} = \frac{K}{N}$$

$$\Omega = 2\pi \frac{K}{N}$$

$$\Omega = 2\pi \times \frac{K}{40}$$

$$\Omega = \frac{\pi}{20} \cdot K$$

$$K = 1 \Rightarrow \Omega = \frac{\pi}{20}$$

$$K = 2 \Rightarrow \Omega = \frac{\pi}{10}$$

$$K = 3 \Rightarrow \Omega = 0.15\pi$$

$$K = 4 \Rightarrow \Omega = 0.2\pi$$

$$K = 5 \Rightarrow \Omega = 0.25\pi$$

$$K = 6 \Rightarrow \Omega = 0.3\pi$$

$$K = 9 \Rightarrow \Omega = 0.45\pi$$

[NAT]

Q.41. 12. The relationship between any N-length sequence $x[n]$ and its corresponding point discrete Fourier transform $X[K]$ is defined as $X[K] = \sum_{n=0}^{N-1} x[n] e^{-j2\pi K n/N}$

If $y[n] = \sum_{k=0}^{N-1} X[k] e^{j2\pi k n/N}$

For the sequence $x[n] = \{1, 2, 1, 3\}$ the value of $Y[0]$ is _____.

Sol.
(112)

$$\text{DFT}(\text{DFT}(x(n))) = Nx(-n)$$

$$\text{DFT}(\text{DFT}(Nx(n))) = N^2x(n)$$

$$y(n) = 16x(n)$$

$$Y(0) = \sum y(n) = 16 \times (1 + 3 + 1 + 2) = 112$$



**GATE
WALLAH**

SOLDIERS

**THANK
YOU**